



香港中文大學(深圳)
The Chinese University of Hong Kong, Shenzhen

ECE2050 Digital Logic and Systems

Tutorial 8: Shift Registers



Yiyang Li

Contact: 222010039@link.cuhk.edu.cn

Office Hour: Tue. 11:00-12:00, ZXB107


Review: Two Basic Functions of Shift Registers

■ Data storage

 
 


Review: Two Basic Functions of Shift Registers



■ Data movement

 


(a) Serial in/shift right/serial out

  

(c) Parallel in/serial out

  


(d) Serial in/parallel out

 


Review: 8-Bit Serial In/Parallel Out Shift Register

 ■ 74HC164: Fixed-function IC shift register with serial in/parallel out




■ Two gated serial inputs: A and B, & an asynchronous clear (CLR) input


■ Parallel outputs : $Q_0 \sim Q_7$.

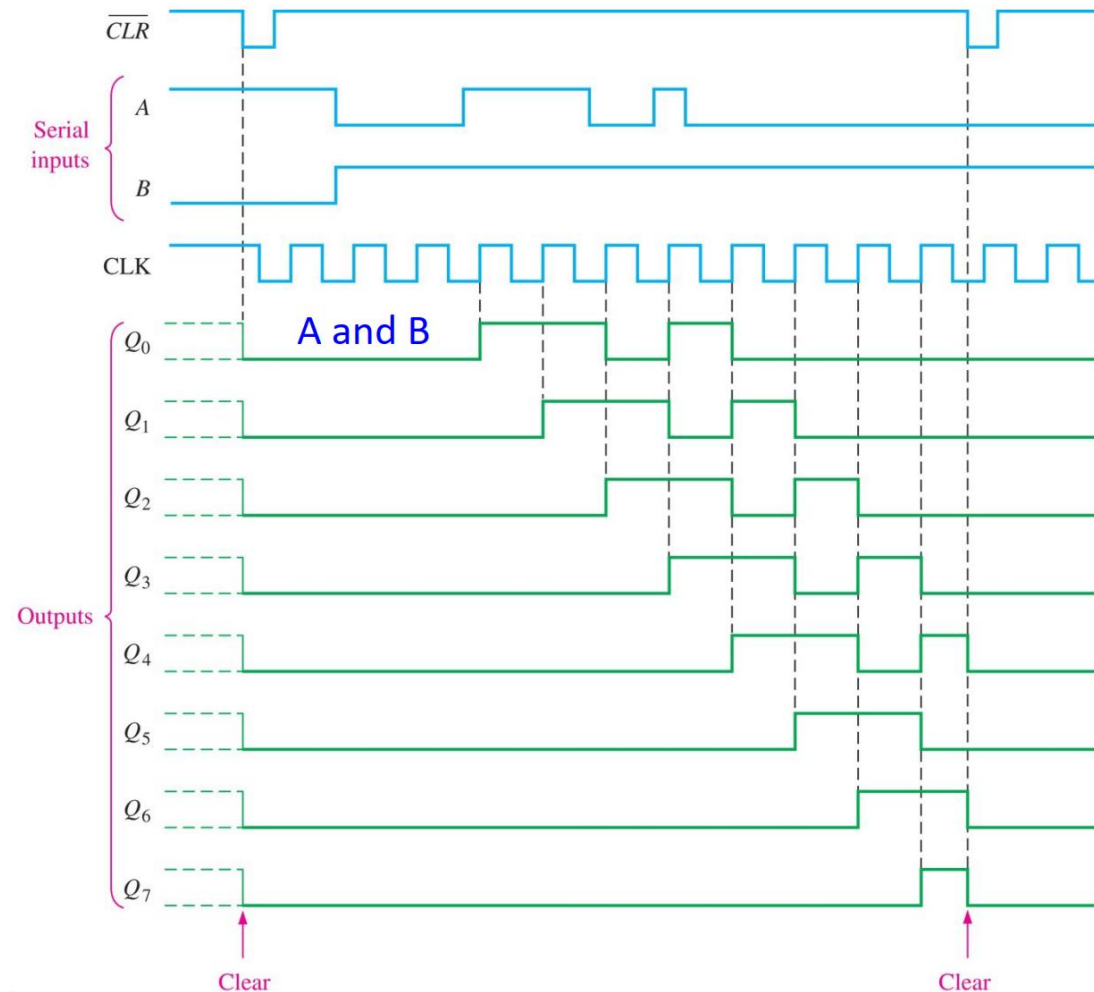

 Review: 4-Bit Bidirectional Universal Shift Register





S_0	S_1	Func.
HIGH	HIGH	Parallel Loading
HIGH	LOW	Shift right
LOW	HIGH	Shift left
LOW	LOW	Inhibit

 


Question 1: 8-Bit Bidirectional Shift Register

- Q1: Combine two 74HC194 to a Bidirectional Shift Register with 8 bit.

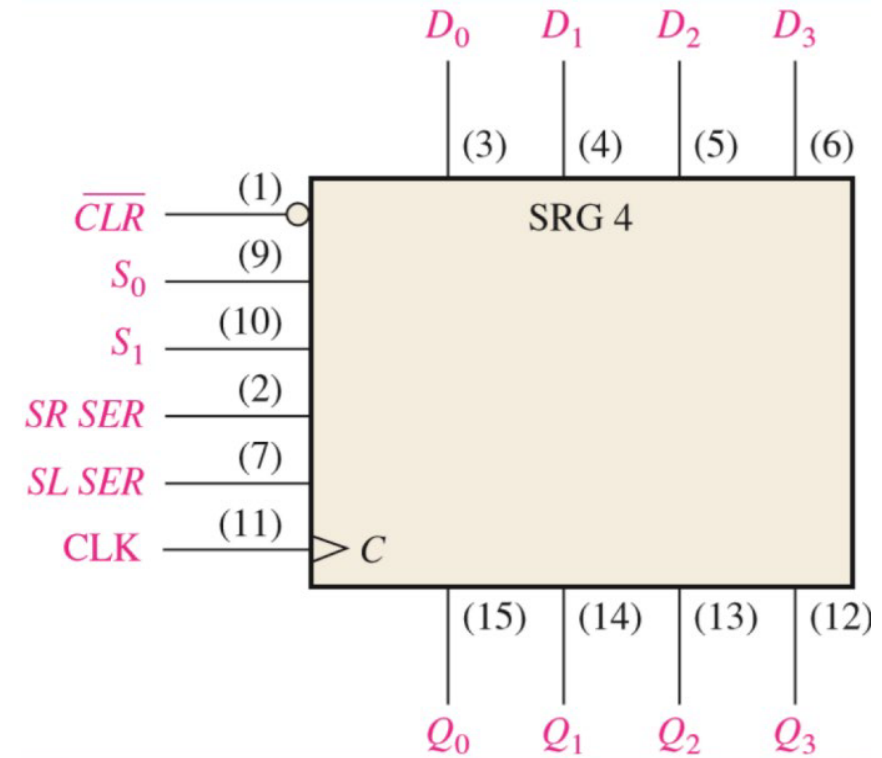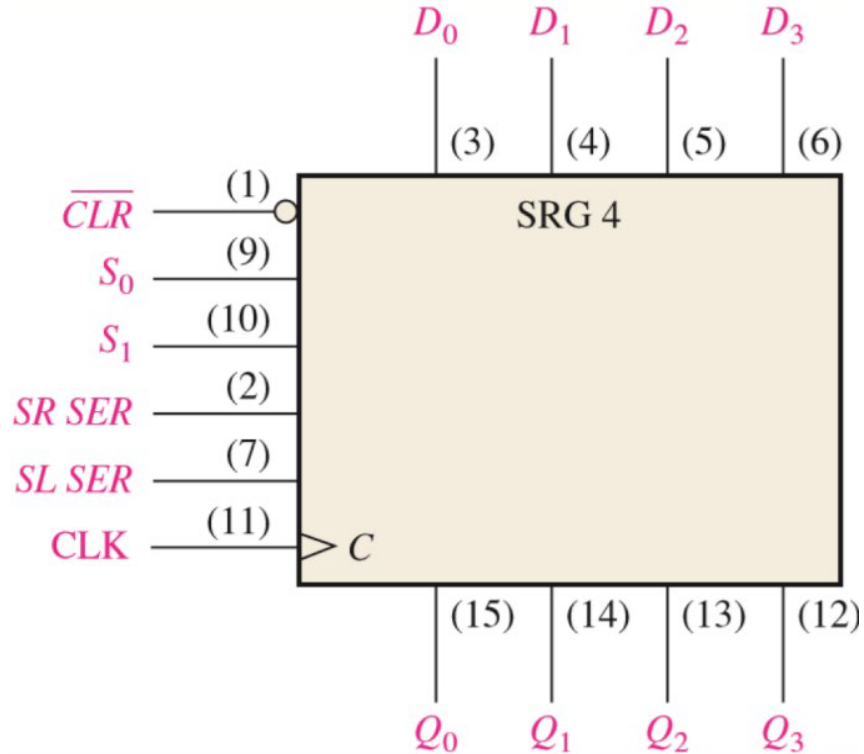

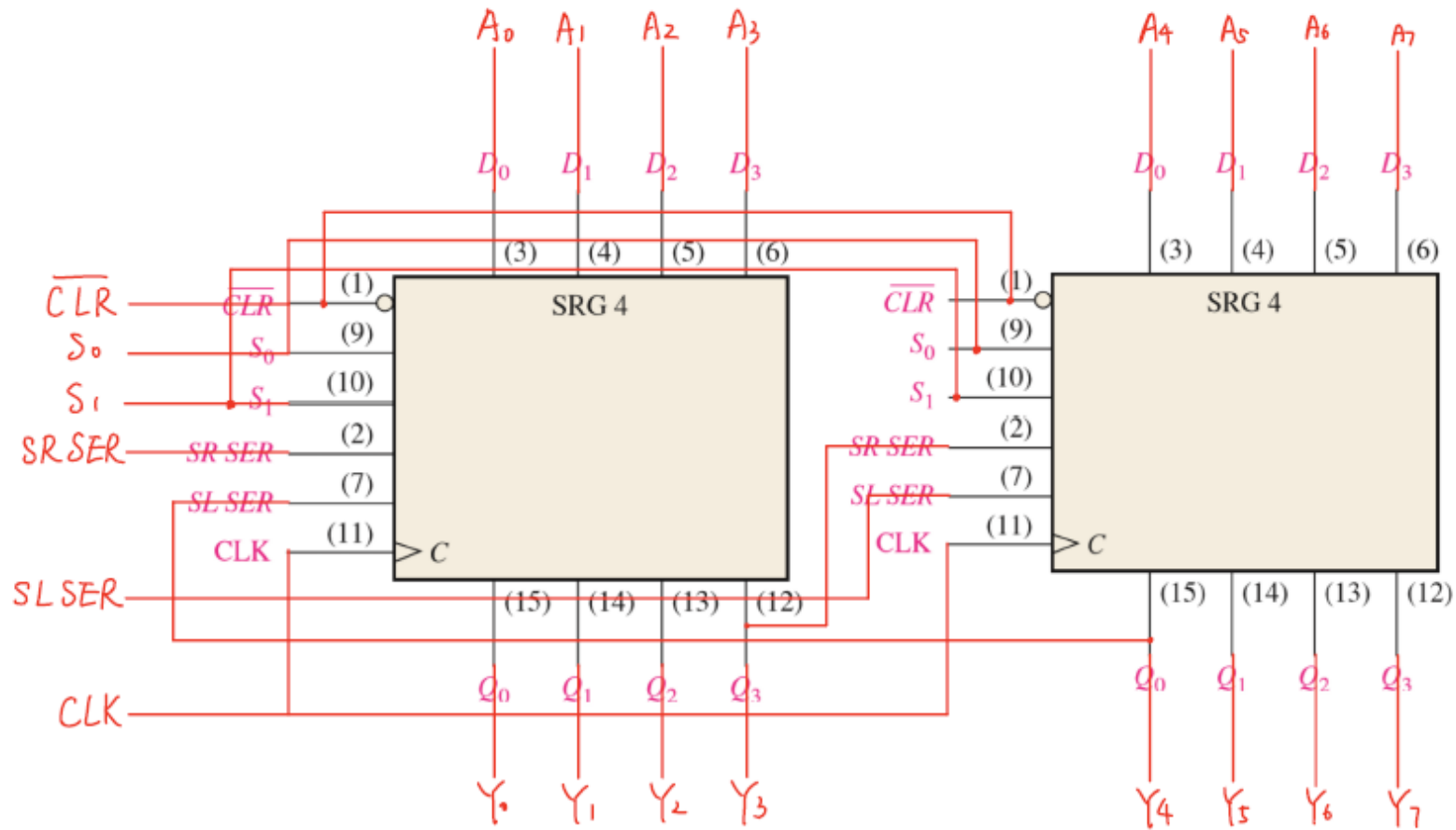Question 1: 8-Bit Bidirectional Shift Register





Parallel input: A0-A7
Parallel output: Y0-Y7
Shift right: new SR SER
Shift left: new SL SER



Question 2: Sequential Signal Generator


- Q2: Try to design a signal generator that can produce 00011101 sequentially, using one 74HC194 and one MUX.

 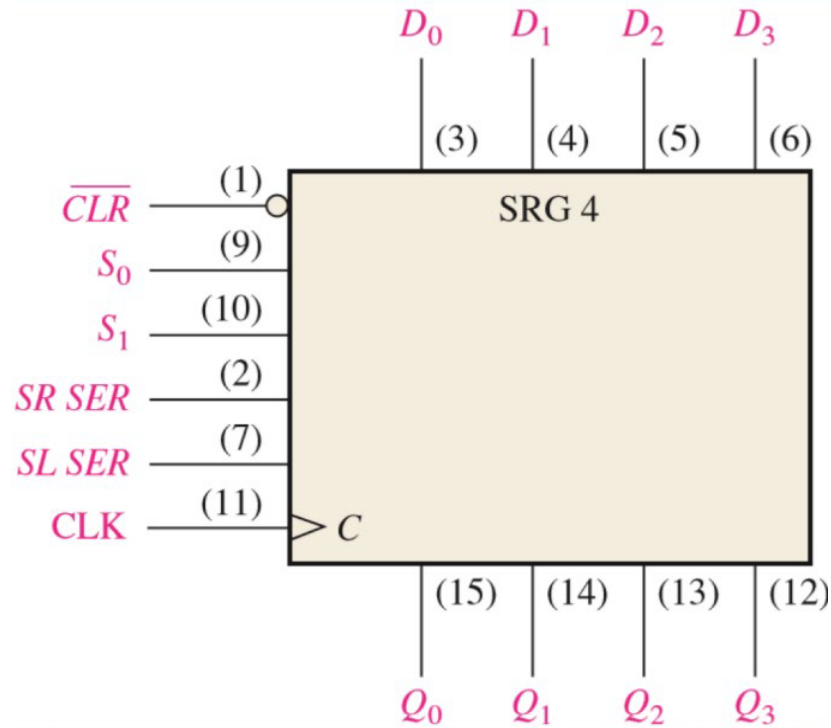

 Question 2: Sequential Signal Generator

Hints:

- Sequence length is 8, and it is possible to generate a serial sequence with a 3-bit shift register. Why?
- Use 74HC194, but three output ports will be enough.
- Use a MUX to help select input.



$$S_i = Q_2 Q_1 Q_0$$

$$S_1 = 000$$

$$S_2 = 100$$

$$S_3 = 110$$

$$S_4 = 111$$

$$S_5 = 011$$

$$S_6 = 101$$

$$S_7 = 010$$

$$S_8 = 001$$

$$S_1 = 000$$

Input \uparrow \uparrow Output

$Q_1 Q_2$	Q_0^n			
	00	01	11	10
0	1	0	1	0
1	1	0	0	1

$D_0=1$ $D_1=0$ $D_3=\overline{Q_0}$ $D_2=Q_0$


Q_0^n	Q_1^n	Q_2^n	Q_0^{n+1}	Q_1^{n+1}	Q_2^{n+1}	F (D_{SR})
0	0	0	1	0	0	1
1	0	0	1	1	0	1
1	1	0	1	1	1	1
1	1	1	0	1	1	0
0	1	1	1	0	1	1
1	0	1	0	1	0	0
0	1	0	0	0	1	0
0	0	1	0	0	0	0



Question 2: Sequential Signal Generator


$Q_1^n Q_2^n$ Q_0^n	00	01	11	10
0	1	0	1	0
1	1	0	0	1

$D_0=1$ $D_1=0$ $D_3=\overline{Q_0}$ $D_2=Q_0$

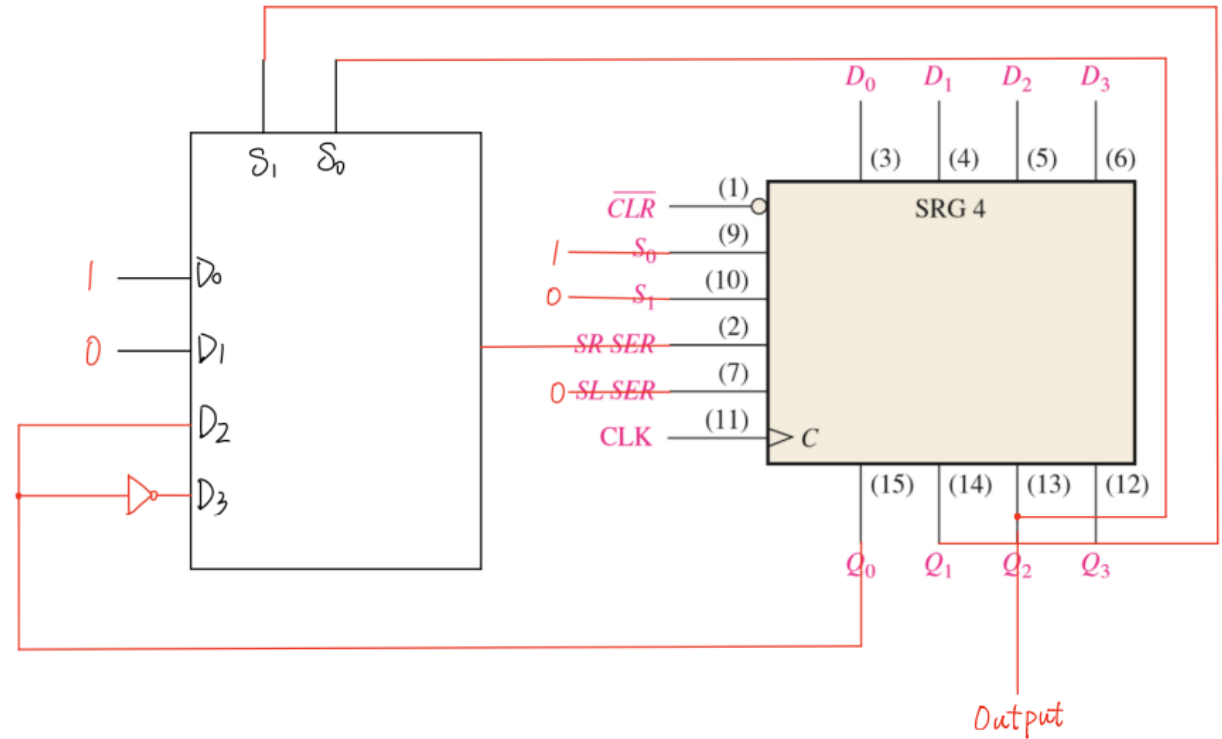

Question 3: Johnson counter

- Q3: Determine the output pulses for this counter circuit, known as a Johnson counter, assuming that all Q outputs begin in the low state.

 

Question 3: Johnson counter

 


TABLE 8-3

Four-bit Johnson sequence.

Clock Pulse	Q_0	Q_1	Q_2	Q_3
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1





香港中文大學(深圳)
The Chinese University of Hong Kong, Shenzhen

Thank You!