

ECE 2050 Digital Logic and Systems

Chapter 6 : Combinational Building Blocks

Instructor: Yue ZHENG, Ph.D.



Last Week

❑ Basic Combinational Logic Circuits

- ◆ AND-OR Logic
- ◆ AND-OR-Invert Logic
- ◆ Exclusive-OR Logic
- ◆ Exclusive-NOR Logic

❑ The Universal Property of NAND Gates

- ◆ Combinations of NAND gates can function as NOT, AND, OR, and NOR
- ◆ Combinations of NOR gates can function as NOT, AND, OR, and NAND.

❑ Dual Symbols :

$$\overline{AB} = \bar{A} + \bar{B} \quad \overline{A + B} = \bar{A}\bar{B}$$

- ◆ NAND Logic Diagrams Using Dual Symbols : NAND and Negative-OR;
- ◆ NOR Logic Diagrams Using Dual Symbols : NOR and Negative-AND


Adders




Half Adders

- Input: two binary digits
- Output: two binary digits — a sum bit & a carry bit

Logic symbol

 

Logic diagram

 

Half-adder truth table.

A	B	C_{out}	Σ
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Σ = sum


C_{out} = output carry

A and B = input variables (operands)


Full Adders

- Input: two binary digits & an input carry
- Output: two binary digits — a sum bit & a carry bit.

Logic symbol

 

Logic diagram

 



Two half-adders

Full-adder truth table.


A	B	C_{in}	C_{out}	Σ
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

C_{in} = input carry, sometimes designated as CI
 C_{out} = output carry, sometimes designated as CO
 Σ = sum
 A and B = input variables (operands)


Full-Adder Implemented with Half-adders.

  


Examples

 

(a)

 

(b)

 


(c)


Parallel Binary Adders

- Two or more full-adders are connected to form parallel binary adders.
- Example:
 
$$A_4A_3A_2A_1 = 1100 \text{ and } B_4B_3B_2B_1 = 1100$$




Block diagram

 

Logic symbol


Parallel Adders : 74HC283 / 74LS283

 - 74HC283/74LS283: 4-bit parallel adders
- Cascading two 4-bit parallel adders to handle the addition of two 8-bit numbers
- The carry input of the low-order adder is connected to ground
- The carry output of the low-order adder is connected to the carry input of the high-order adder



(a) Pin diagram

(b) Logic symbol

 


Low-order adder

High-order adder

Applications

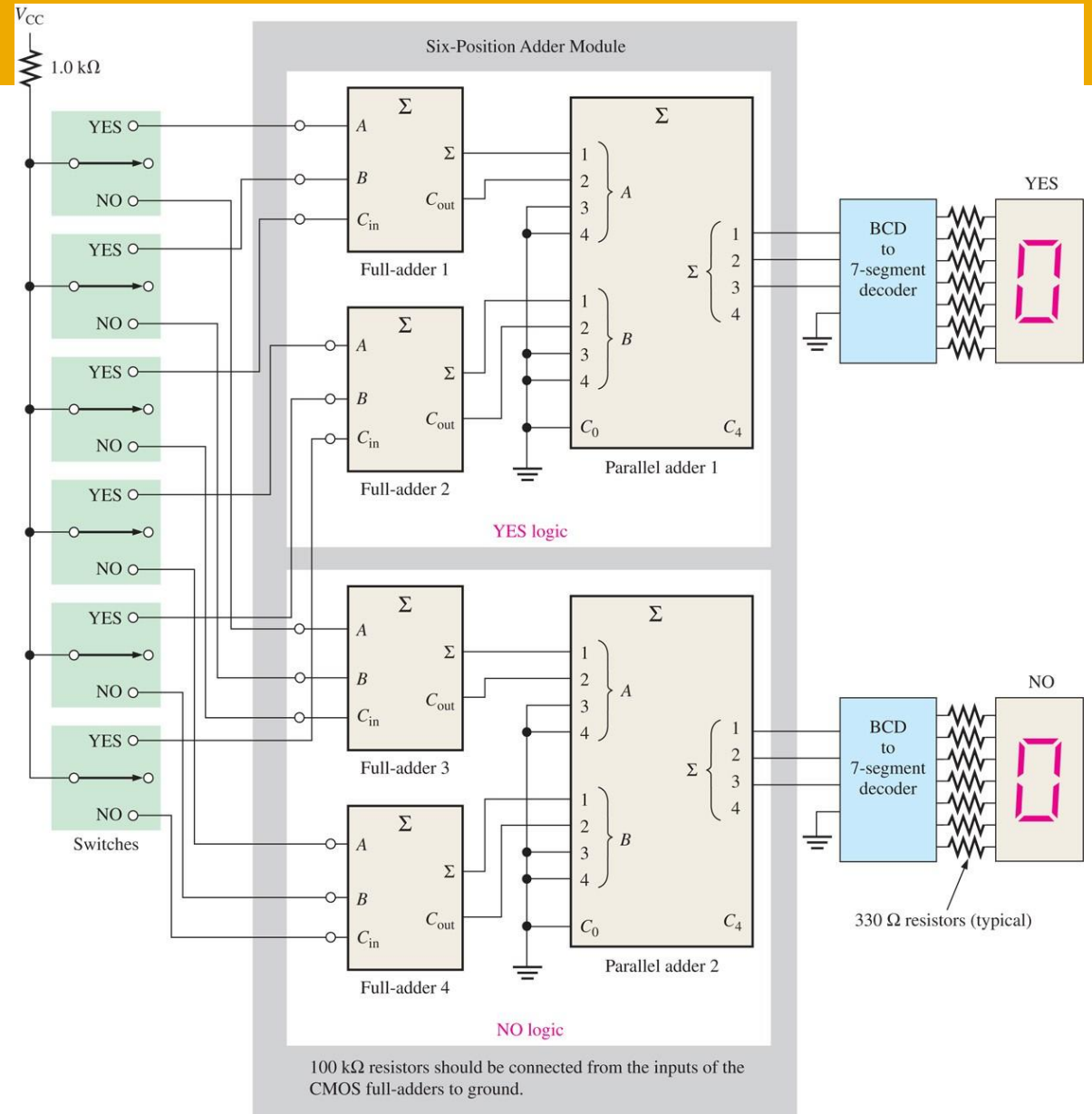
- A voting system that simultaneously counts # of “yes” and # of “no” votes.
- Assuming 6-position setup for simplicity
- Each input is LOW when the switch is in the neutral
- When a switch is moved to the “yes” or “no” position, a HIGH level (V_{CC}) is applied to the associated full adder input.



The Ripple Carry Adder

- The carry output of each full-adder is connected to the carry input of the next higher-order stage (a stage is one full-adder);
- The sum and the output carry of any stage cannot be produced until the input carry occurs, which causes a time delay in the addition process.

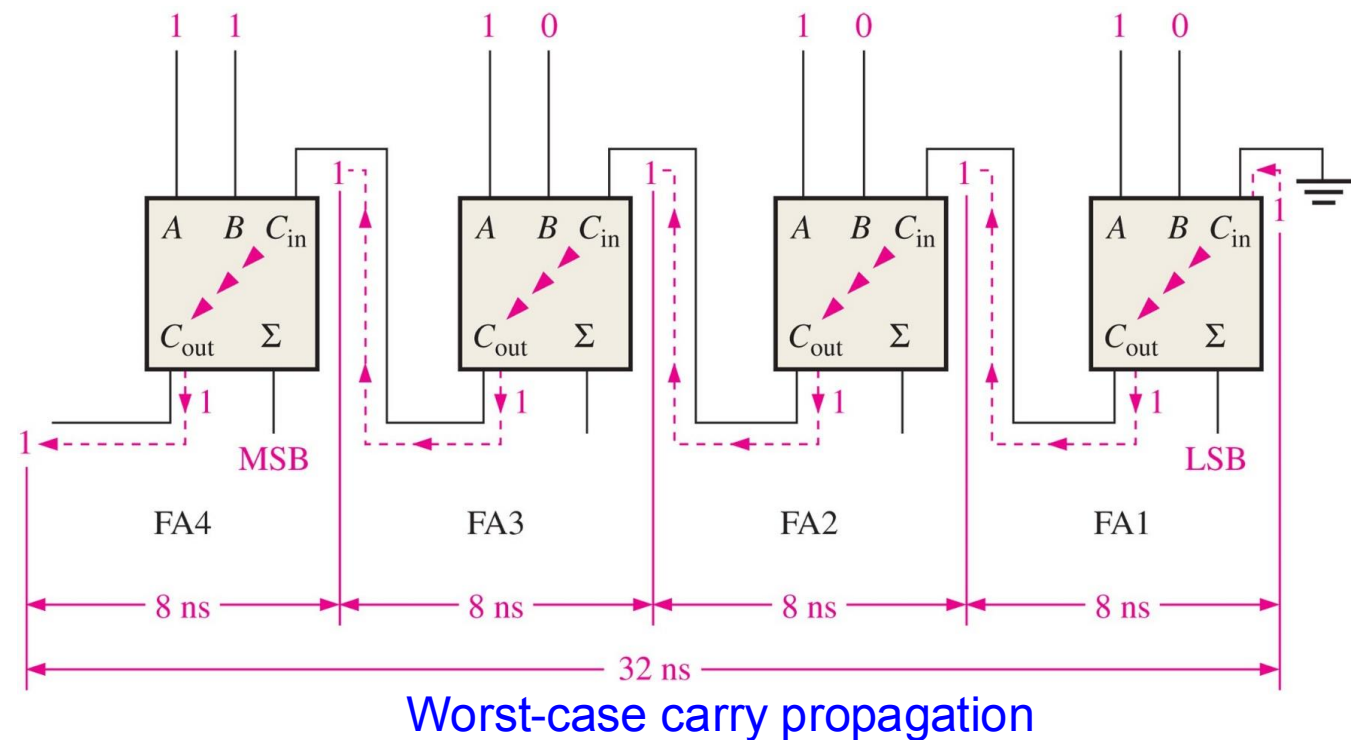The input carry to the least significant stage has to **ripple** through all the adders before a final sum is produced.



The Look-Ahead Carry Adder

- To speed up the addition process by eliminating the ripple carry delay


- Carry generation: $C_g = AB$

- Carry propagation:

Given the input carry is 1,


$$C_p = A + B$$

 - Thus, the output carry is given by $C_{out} = C_g + C_p C_{in}$



A 4-Bit Look-Ahead Carry Adder (I)

 - Adding $A_4A_3A_2A_1$ and $B_4B_3B_2B_1$



A 4-Bit Look-Ahead Carry Adder (II)

- Express C_{out} in terms of C_p , C_g and C_{in1}

Full-adder 1:

$$C_{out1} = C_{g1} + C_{p1}C_{in1}$$

Full-adder 2:


$$\begin{aligned} C_{in2} &= C_{out1} \\ C_{out2} &= C_{g2} + C_{p2}C_{in2} = C_{g2} + C_{p2}C_{out1} = C_{g2} + C_{p2}(C_{g1} + C_{p1}C_{in1}) \\ &= C_{g2} + C_{p2}C_{g1} + C_{p2}C_{p1}C_{in1} \end{aligned}$$

Full-adder 3:

$$\begin{aligned} C_{in3} &= C_{out2} \\ C_{out3} &= C_{g3} + C_{p3}C_{in3} = C_{g3} + C_{p3}C_{out2} = C_{g3} + C_{p3}(C_{g2} + C_{p2}C_{g1} + C_{p2}C_{p1}C_{in1}) \\ &= C_{g3} + C_{p3}C_{g2} + C_{p3}C_{p2}C_{g1} + C_{p3}C_{p2}C_{p1}C_{in1} \end{aligned}$$


Full-adder 4:
 
$$\begin{aligned} C_{in4} &= C_{out3} \\ C_{out4} &= C_{g4} + C_{p4}C_{in4} = C_{g4} + C_{p4}C_{out3} \\ &= C_{g4} + C_{p4}(C_{g3} + C_{p3}C_{g2} + C_{p3}C_{p2}C_{g1} + C_{p3}C_{p2}C_{p1}C_{in1}) \\ &= C_{g4} + C_{p4}C_{g3} + C_{p4}C_{p3}C_{g2} + C_{p4}C_{p3}C_{p2}C_{g1} + C_{p4}C_{p3}C_{p2}C_{p1}C_{in1} \end{aligned}$$



A 4-Bit Look-Ahead Carry Adder (III)

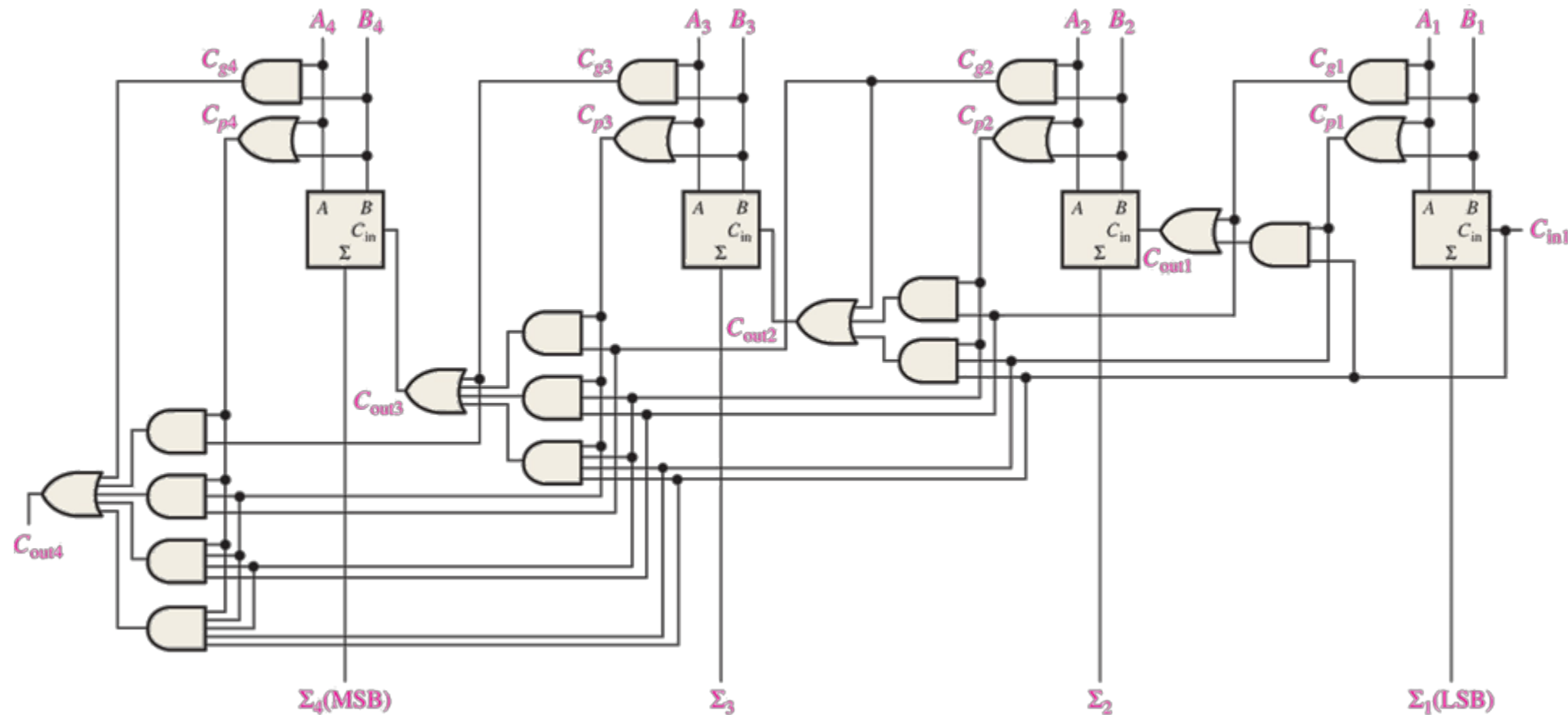- Logic diagram for a 4-stage look-ahead carry adder



Combine Look-Ahead and Ripple Carry Adders


- Cascading two look-ahead carry adders by connecting the output carry of one adder to the input carry of the next adder.

Comparators




Comparator: Equality

 - Exclusive-NOR gate can be used as a basic comparator



Comparator: Equality

 
- Equality comparison of two 2-bit numbers



General format: Binary number $A \rightarrow A_1A_0$
Binary number $B \rightarrow B_1B_0$


Comparator: Inequality

- Inequality comparison with three outputs indicating
 - Number A is greater than number B ($A > B$)
 - Number A is less than number B ($A < B$)
 - Number A is equal to number B ($A = B$).
- General procedures
 - To check for an inequality in a bit position, starting with the **highest**-order bits (MSBs).
 - When such an inequality is found, the relationship of the two numbers is established, and any other inequalities in lower-order bit positions must be ignored
- Using a 4-bit comparator as an example
 - If $A_3 = 1$ and $B_3 = 0$, number A is greater than number B.
 - If $A_3 = 0$ and $B_3 = 1$, number A is less than number B.
 - If $A_3 = B_3$, then examine the next lower bit position.

 


Comparators: 74HC85/74LS85

 - The 74HC85/74LS85 pin diagram and logic symbol



(a) Pin diagram

 

(b) Logic symbol


H = HIGH voltage level; L = LOW voltage level; X = don't care.

Comparing inputs				Cascading inputs			Outputs		
A3, B3	A2, B2	A1, B1	A0, B0	I _{A>B}	I _{A<B}	I _{A=B}	Q _{A>B}	Q _{A<B}	Q _{A=B}
A3 > B3	X	X	X	X	X	X	H	L	L
A3 < B3	X	X	X	X	X	X	L	H	L
A3 = B3	A2 > B2	X	X	X	X	X	H	L	L
A3 = B3	A2 < B2	X	X	X	X	X	L	H	L
A3 = B3	A2 = B2	A1 > B1	X	X	X	X	H	L	L
A3 = B3	A2 = B2	A1 < B1	X	X	X	X	L	H	L
A3 = B3	A2 = B2	A1 = B1	A0 > B0	X	X	X	H	L	L
A3 = B3	A2 = B2	A1 = B1	A0 < B0	X	X	X	L	H	L
A3 = B3	A2 = B2	A1 = B1	A0 = B0	H	L	L	H	L	L
A3 = B3	A2 = B2	A1 = B1	A0 = B0	L	H	L	L	H	L
A3 = B3	A2 = B2	A1 = B1	A0 = B0	L	L	H	L	L	H

Ref: https://assets.nexperia.com/documents/data-sheet/74HC_HCT85.pdf

Cascading of Comparators

 - Several comparators can be cascaded for number of more bits



Note the lowest-order comparator must have


- A HIGH on the $A = B$ input and
- LOWs on the $A > B$ and $A < B$ inputs.

Encoder & Decoder



Encoder

 - Input: Accepts an active level on one of its multiple input lines
- Output: multiple *output* lines
- Example: a 10-line-to-4-line encoder




Decimal-to-BCD **Priority** Encoder


- Produce a BCD output corresponding to the **highest-order decimal digit** input that is active and **will ignore any other lower-order active inputs**

 Example


- If LOW levels appear on pins, 1, 4, and 13 of the 74HC147 → Pin 4 is the highest-order decimal digit input having a LOW level and represents decimal 7. Therefore, the output levels indicate the BCD code for decimal 7



(a) Pin diagram

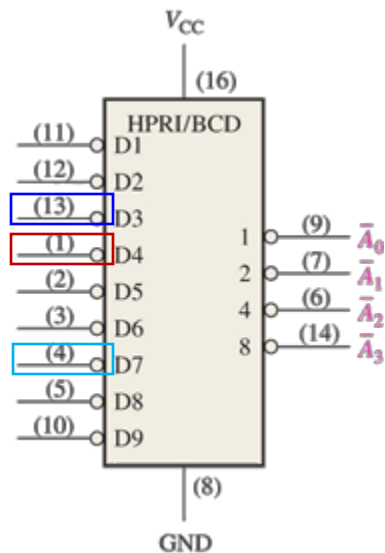

(b) Logic diagram

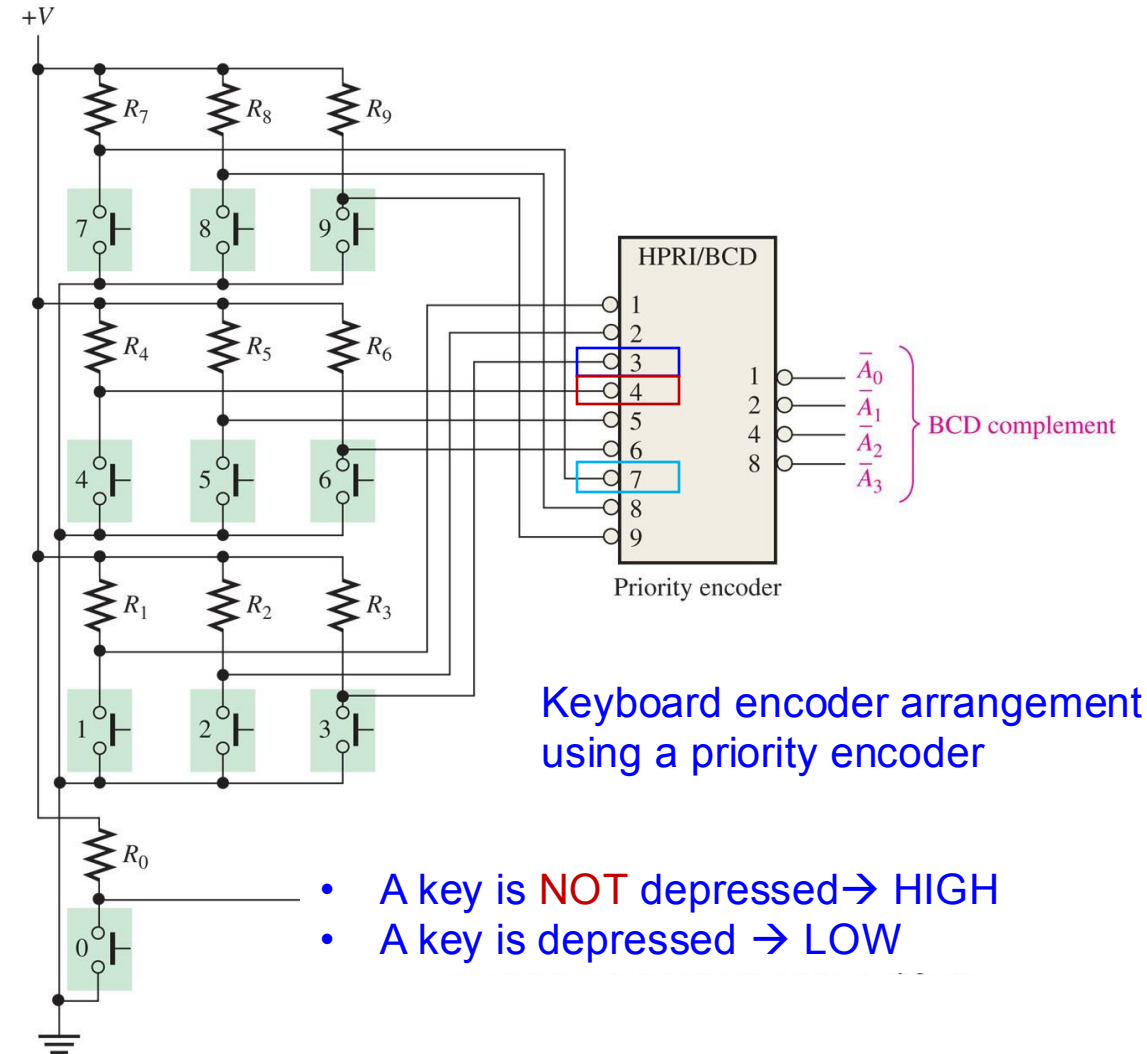


Keyboard encoder arrangement using a priority encoder

- A key is **NOT** depressed → HIGH
- A key is depressed → LOW

Priority Encoder

 - Use “Don’t Care” to indicate priority by design




Inputs								Outputs		
D_7	D_6	D_5	D_4	D_3	D_2	D_1	D_0	Q_2	Q_1	Q_0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	x	0	0	1
0	0	0	0	0	1	x	x	0	1	0
0	0	0	0	1	x	x	x	0	1	1
0	0	0	1	x	x	x	x	1	0	0
0	0	1	x	x	x	x	x	1	0	1
0	1	x	x	x	x	x	x	1	1	0
1	x	x	x	x	x	x	x	1	1	1

X = dont care


Decoders

 - N inputs, 2^N outputs
- **One-hot outputs:** only one output **Active** at once




A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

Decoder Implementation

 

Logic Using Decoders

- OR the minterms:

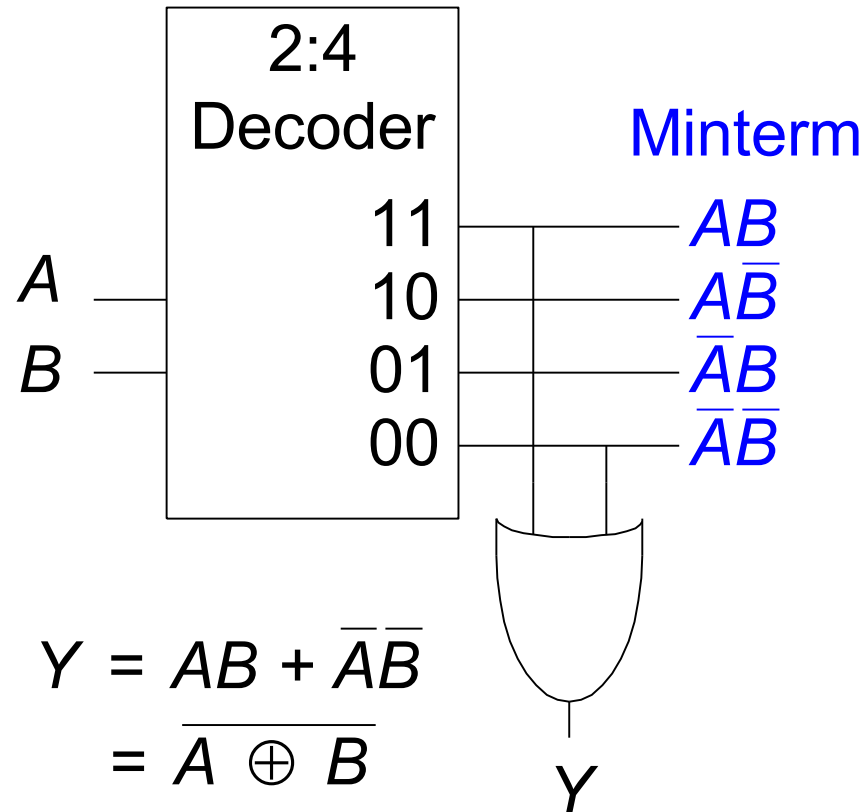


Example: 4-bit Decoder

Decoding functions and truth table for a 4-line-to-16-line (1-of-16) decoder with active-LOW outputs.


Decimal Digit	Binary Inputs				Decoding Function	Outputs															
	A ₃	A ₂	A ₁	A ₀		0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
0	0	0	0	0	$\overline{A_3}\overline{A_2}\overline{A_1}\overline{A_0}$	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1
1	0	0	0	1	$\overline{A_3}\overline{A_2}\overline{A_1}A_0$	1	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1
2	0	0	1	0	$\overline{A_3}\overline{A_2}A_1\overline{A_0}$	1	1	0	1	1	1	1	1	1	1	1	1	1	1	1	1
3	0	0	1	1	$\overline{A_3}\overline{A_2}A_1A_0$	1	1	1	0	1	1	1	1	1	1	1	1	1	1	1	1
4	0	1	0	0	$\overline{A_3}A_2\overline{A_1}\overline{A_0}$	1	1	1	1	0	1	1	1	1	1	1	1	1	1	1	1
5	0	1	0	1	$\overline{A_3}A_2\overline{A_1}A_0$	1	1	1	1	1	0	1	1	1	1	1	1	1	1	1	1
6	0	1	1	0	$\overline{A_3}A_2A_1\overline{A_0}$	1	1	1	1	1	1	0	1	1	1	1	1	1	1	1	1
7	0	1	1	1	$\overline{A_3}A_2A_1A_0$	1	1	1	1	1	1	1	0	1	1	1	1	1	1	1	1
8	1	0	0	0	$A_3\overline{A_2}\overline{A_1}\overline{A_0}$	1	1	1	1	1	1	1	1	0	1	1	1	1	1	1	1
9	1	0	0	1	$A_3\overline{A_2}\overline{A_1}A_0$	1	1	1	1	1	1	1	1	1	0	1	1	1	1	1	1
10	1	0	1	0	$A_3\overline{A_2}A_1\overline{A_0}$	1	1	1	1	1	1	1	1	1	1	0	1	1	1	1	1
11	1	0	1	1	$A_3\overline{A_2}A_1A_0$	1	1	1	1	1	1	1	1	1	1	1	0	1	1	1	1
12	1	1	0	0	$A_3A_2\overline{A_1}\overline{A_0}$	1	1	1	1	1	1	1	1	1	1	1	1	0	1	1	1
13	1	1	0	1	$A_3A_2\overline{A_1}A_0$	1	1	1	1	1	1	1	1	1	1	1	1	1	0	1	1
14	1	1	1	0	$A_3A_2A_1\overline{A_0}$	1	1	1	1	1	1	1	1	1	1	1	1	1	1	0	1
15	1	1	1	1	$A_3A_2A_1A_0$	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	0

16 NAND Gates

 


Decoders: 74HC154

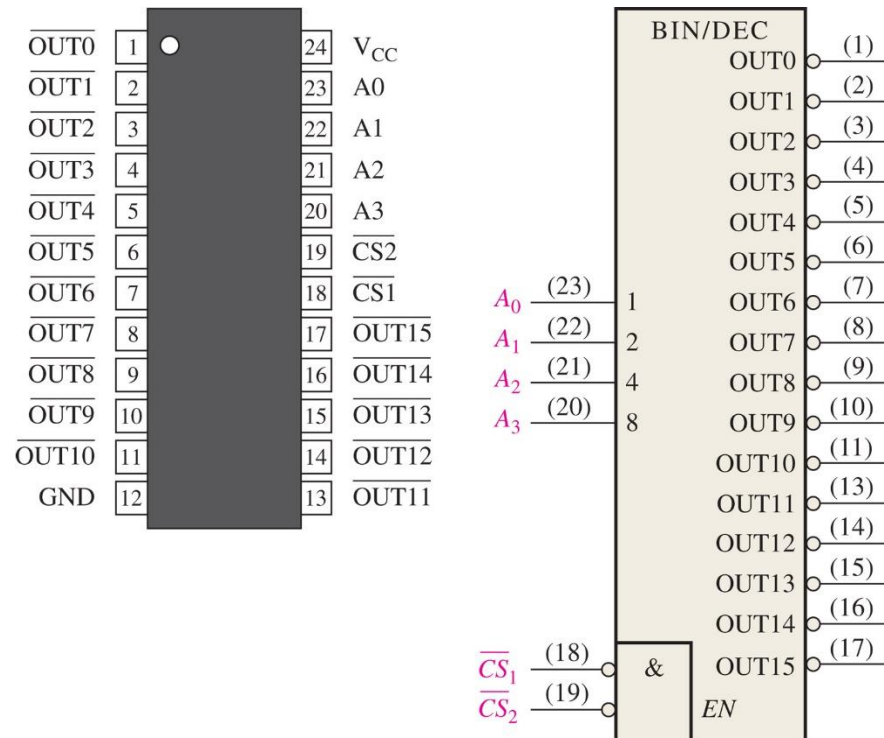- EN: \overline{CS}_1 and \overline{CS}_2 both LOW \rightarrow Output HIGH
- EN is connected to an input of each NAND
- EN: HIGH to enable the decoder; otherwise all decoder outputs will be HIGH



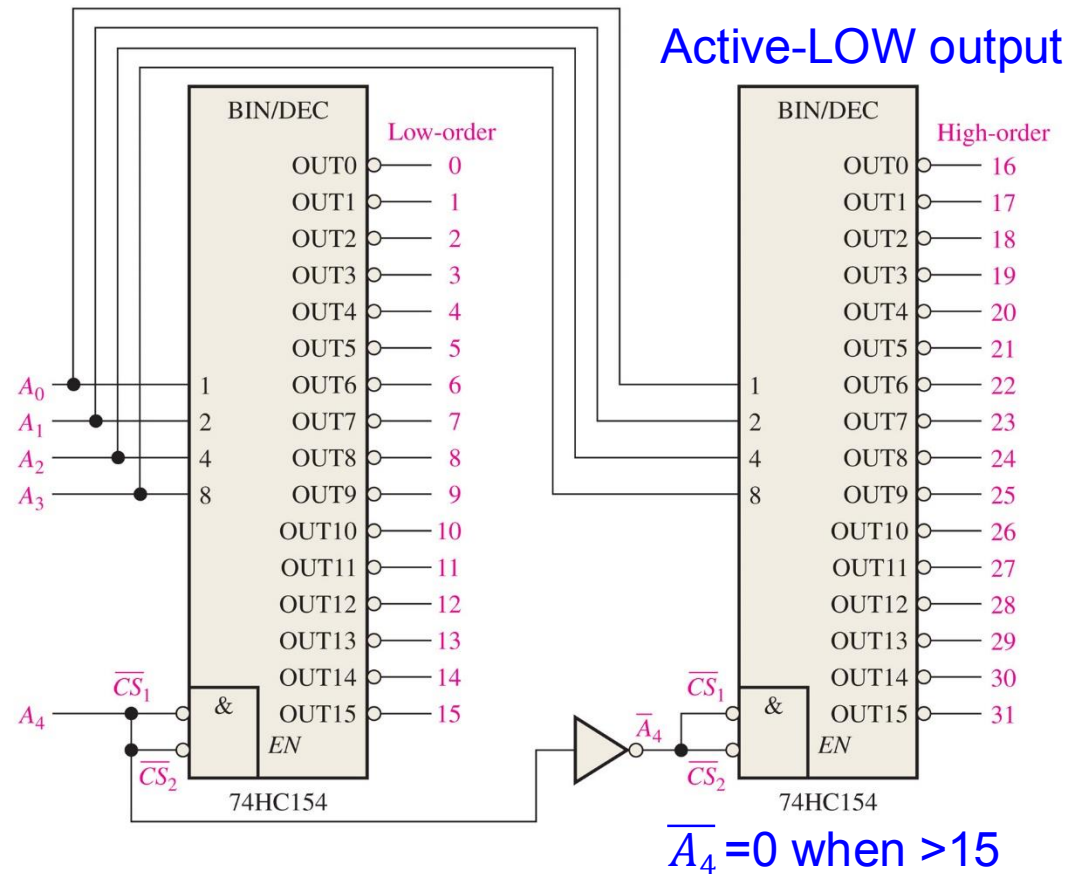
Example

- Implement a 5-bit decoder using two 4-bit decoders (74HC154)
- EN is connected to an input of each NAND
- EN: HIGH to enable the decoder; otherwise all decoder outputs will be HIGH




Decoders: BCD-to-Decimal Decoder

 - 4-line-to-10-line decoder: only the ten decimal digits 0 through 9.






BCD decoding functions.

Decimal Digit	A_3	A_2	A_1	A_0	Decoding Function
0	0	0	0	0	$\overline{A_3}\overline{A_2}\overline{A_1}\overline{A_0}$
1	0	0	0	1	$\overline{A_3}\overline{A_2}\overline{A_1}A_0$
2	0	0	1	0	$\overline{A_3}\overline{A_2}A_1\overline{A_0}$
3	0	0	1	1	$\overline{A_3}\overline{A_2}A_1A_0$
4	0	1	0	0	$\overline{A_3}A_2\overline{A_1}\overline{A_0}$
5	0	1	0	1	$\overline{A_3}A_2\overline{A_1}A_0$
6	0	1	1	0	$\overline{A_3}A_2A_1\overline{A_0}$
7	0	1	1	1	$\overline{A_3}A_2A_1A_0$
8	1	0	0	0	$A_3\overline{A_2}\overline{A_1}\overline{A_0}$
9	1	0	0	1	$A_3\overline{A_2}\overline{A_1}A_0$

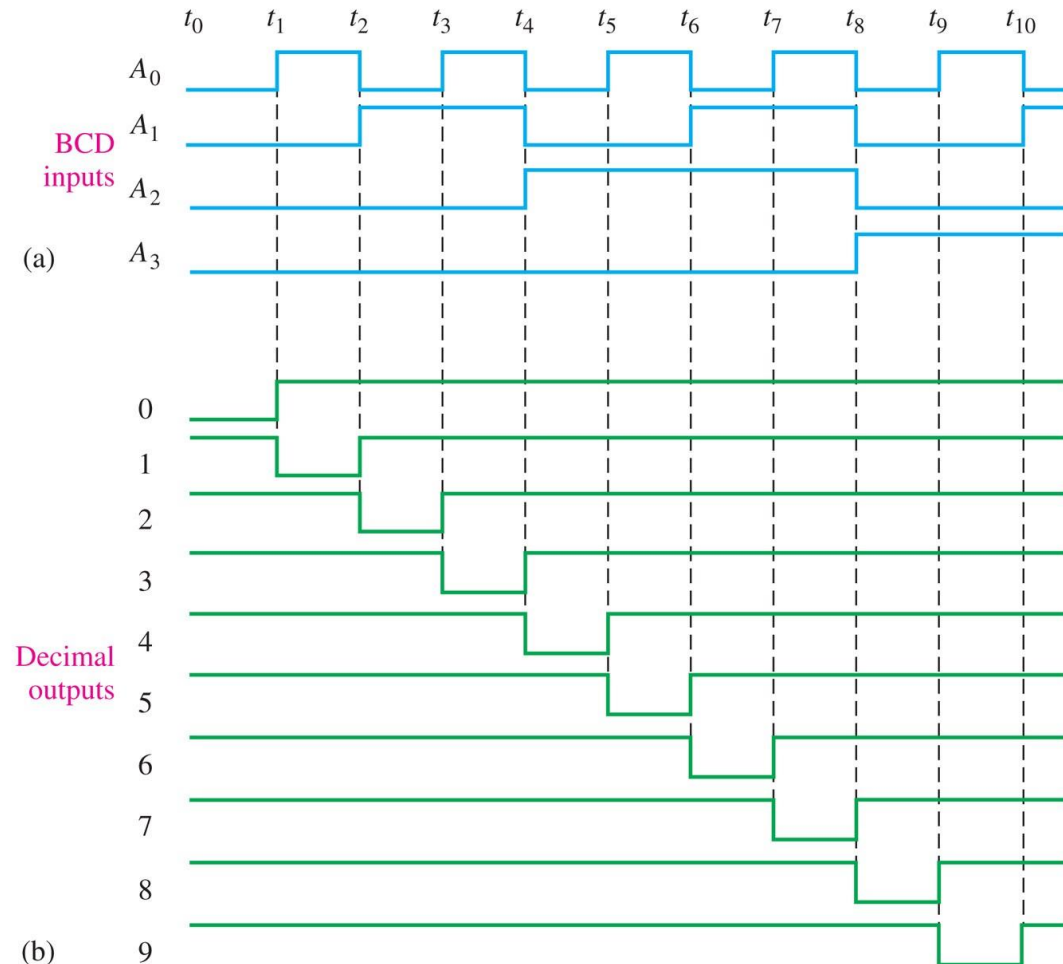


Decoders: The BCD-to-7-Segment Decoder

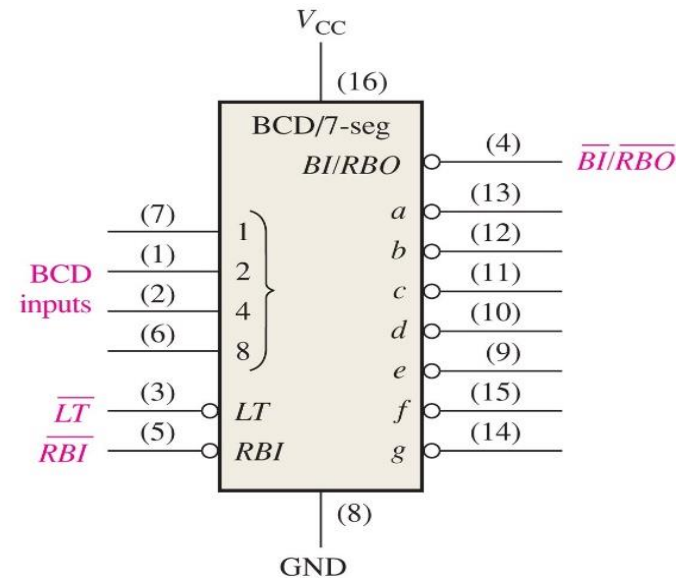  - Inequality comparison with three outputs indicating
 - LT : Lamp test
 - RBI : Ripple blanking input
 - BI /RBO : either **Blanking input** or **Ripple blanking output**
- Lamp test: \overline{LT} : LOW, and $\overline{BI} / \overline{RBO}$: HIGH, all segments are turned on



Decoders: The BCD-to-7-Segment Decoder

 - BCD inputs = 0000 and \overline{RBI} is LOW, \rightarrow decoder outputs HIGH, display blanked & \overline{RBO} LOW
- Zero suppression:**
0030.0800 will be displayed as 30.08




Multiplexers



Multiplexer (Mux): Data Selector

- Selects between one of N inputs to connect to output
- **Select** input is $\log_2 N$ bits – control input
- **Example:**

2:1 Mux

 

S	D_1	D_0	Y	S	Y
0	0	0	0	0	D_0
0	0	1	1	1	D_1
0	1	0	0		
0	1	1	1		
1	0	0	0		
1	0	1	0		
1	1	0	1		
1	1	1	1		


2:1 Multiplexer Implementations

- **Logic gates**

- Sum-of-products form


$D_0 D_1$		S			
		00	01	11	10
Y	0	0	0	1	1
	1	0	1	1	0

$$Y = D_0 \bar{S} + D_1 S$$

 


- **Tristates**

 - Two tristates
- Turn on exactly one to select the appropriate input




Example: 4:1 Mux

 


Data selection for a 1-of-4-multiplexer.

Data-Select Inputs		Input Selected
S_1	S_0	
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

 


4:1 Multiplexer Implementations


2-Level Logic

 

Tristates

 

4:1 Mux Symbol

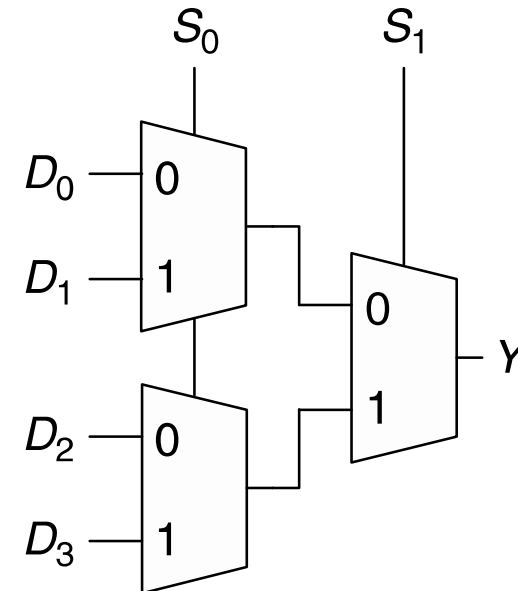


Logic using Multiplexers

- Using MUX as a **lookup table**

<i>A</i>	<i>B</i>	<i>Y</i>
0	0	0
0	1	1
1	0	0
1	1	0


$$Y = \overline{A}B$$

 

Logic using Multiplexers



- Using MUX as a **logic function generator**

Inputs			Output
A_2	A_1	A_0	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

 

Demultiplexer: data distributor

 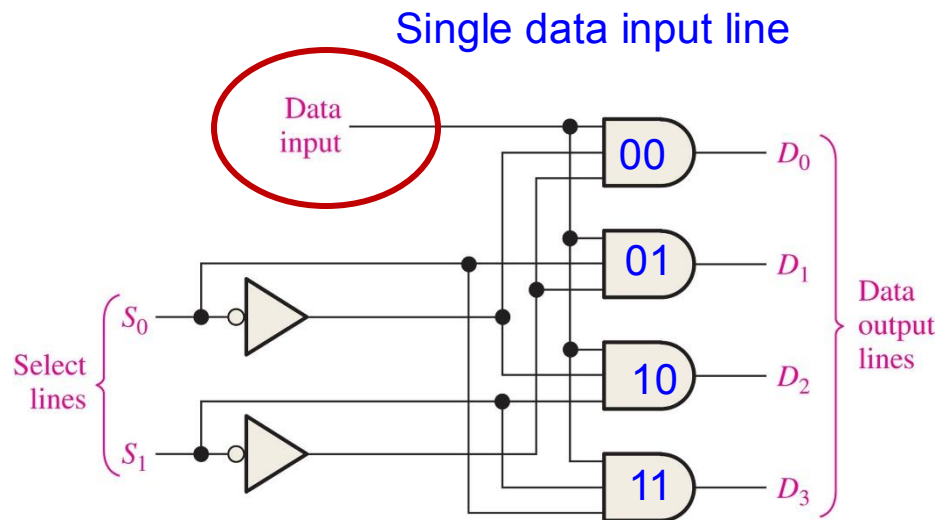- Aka. a data distributor that reverses the multiplexing function




Timing




Timing

 - **Delay**: time between input change and output changing
- How to build fast circuits?



Propagation & Contamination Delay

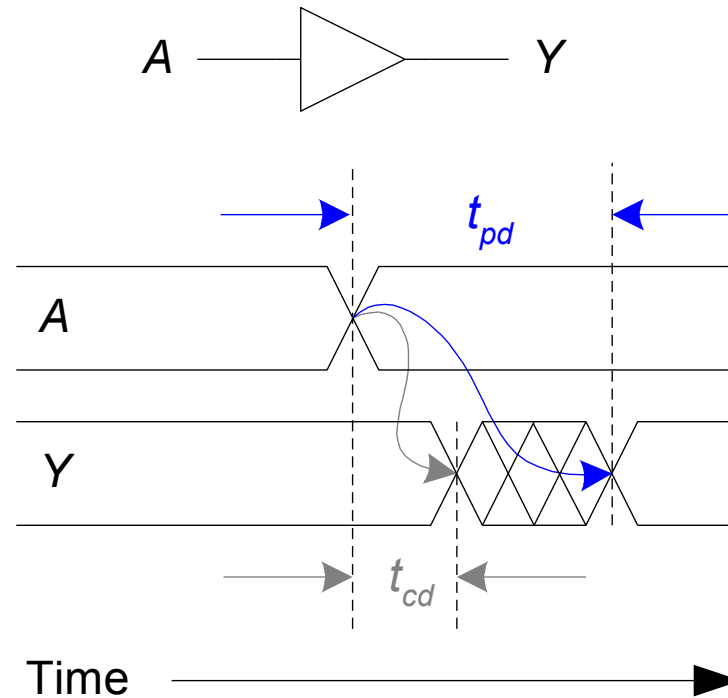
- **Propagation delay:** $t_{pd} = \mathbf{max}$ delay from input to output
- **Contamination delay:** $t_{cd} = \mathbf{min}$ delay from input to output



Propagation & Contamination Delay

- **Delay is caused by**
 - Capacitance and resistance in a circuit
 - Speed of light limitation
- **Reasons why t_{pd} and t_{cd} may be different:**
 - Different rising and falling delays
 - Multiple inputs and outputs, some of which are faster than others
 - Circuits slow down when hot and speed up when cold

Critical (Long) & Short Paths

 

Critical (Long) Path: $t_{pd} = 2t_{pd_AND} + t_{pd_OR}$ (max delay)

Short Path: $t_{cd} = t_{cd_AND}$ (min delay)


Glitches

- When a single input change causes an output to change multiple times





Glitch Example

 - What happens when $A = 0$, $C = 1$, B falls?



		AB			
C	AB	00	01	11	10
	0	1	0	0	0
1	0	1	1	1	0

$Y = \bar{A}\bar{B} + BC$

 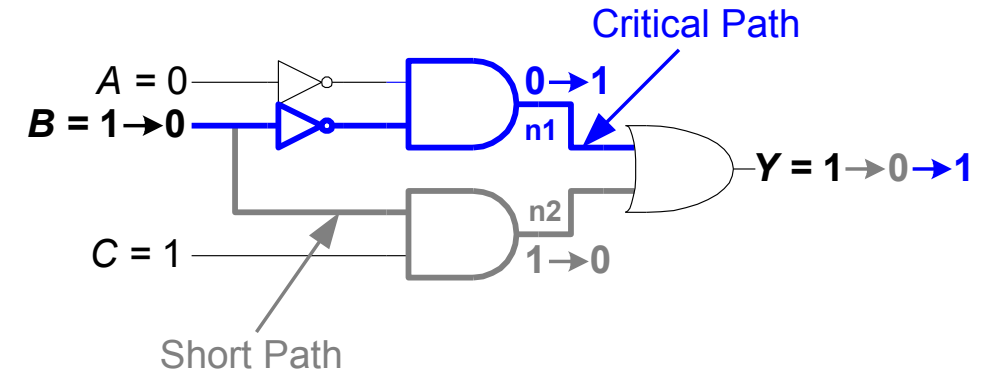


Fixing the Glitch

Y		AB			
		00	01	11	10
C	0	1	0	0	0
	1	1	1	1	0

$\bar{A}C$ (points to the cell where C=1 and AB=00)

$Y = \bar{A}\bar{B} + BC + \bar{A}C$

 


Why Understand Glitches?


- Because of **synchronous design** conventions (see Chapter 3), glitches don't cause problems.
- It's important to **recognize** a glitch: in simulations or on oscilloscope.
- We **can't get rid of all glitches** – simultaneous transitions on multiple inputs can also cause glitches.

Chapter Review

 - ❑ Half and Full Adders
- ❑ Parallel Binary Adders
- ❑ Ripple Carry and Look-Ahead Carry Adders
- ❑ Comparators
- ❑ Decoders (n input lines \rightarrow max. 2^n output lines)
- ❑ Encoders (e.g. Decimal-to-BCD **Priority** Encoder)
- ❑ Code Converters (e.g. BCD-to-Binary Conversion)
- ❑ Multiplexers (To route several inputs onto a single output line)
- ❑ Demultiplexers
- ❑ Timing



How to design a multiplier by FA/HA?

 

True/False Quiz



A half-adder adds two binary bits.



A half-adder has a carry output only.



A full adder adds two bits and produces two outputs.



A full-adder can be realized only by using 2-input XOR gates.



When the input bits are both 1 and the input carry bit is 1, the sum output of a full adder is 1.



The output of a comparator is 0 when the two binary inputs given are equal.



A decoder detects the presence of a specified combination of input bits.



The 4-line-to-10-line decoder and the 1-of-10 decoder are two different types.



An encoder essentially performs a reverse decoder function.



A multiplexer is a logic circuit that allows digital information from a single source to be routed onto several lines.

