 



# ECE2050 Homework 6

**Due:** March 29, 2025

**Q1** Given the input waveforms shown below, sketch the output,  $Q$ , of an SR latch.




 
**Q2** Determine the output of a D Latch for the inputs below.





*Q* Low

  **Q3** Construct the following flip-flops:


- Construct a JK flip-flop, using a D flip-flop and some combinational logic.
- Construct a D flip-flop, using a JK flip-flop and some combinational logic.



  **Q4** Design a circuit to generate a very short-duration negative spike on the negative-going transition of the clock pulse. (You are not allowed to use more than two inverters.)





 **Q5** Design a synchronous resettable D flip-flop, using basic logic gates. (You are not allowed to use off-the-shelf D flip-flop.)



**Q6** Determine the output  $Q$  of a **synchronous** resettable D flip-flop for the inputs below. (The input  $\overline{Reset}$  is **active-low**.)

Symbols

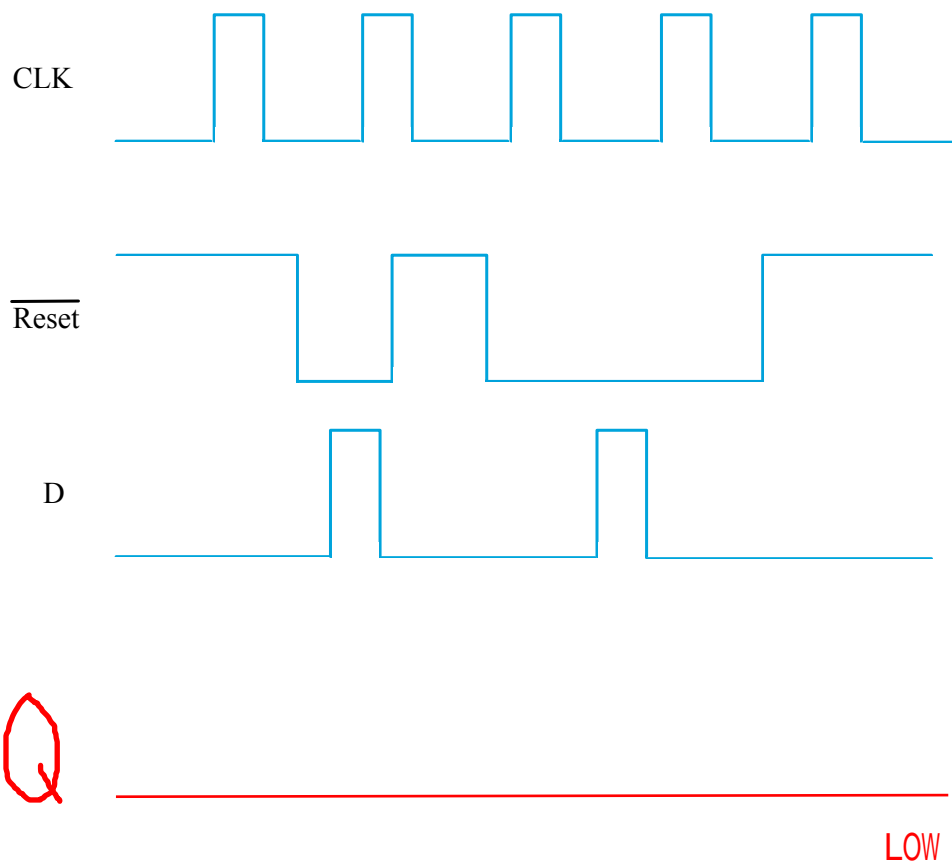 

**Q7** Determine the output  $Q$  of an **asynchronous** resettable D flip-flop for the inputs below. (The input Reset is **active-high**.)

### Symbols

