

Midterm Test

(Time allowed: 90 minutes)

November 7, 2021

NOTE: Answer ALL 9 questions. Show all intermediate steps, except Question 1.

1. (10 points) Are the following statements necessarily true (Y) or not (N)?

- (1) The dual symbol for a NAND gate is a negative-AND symbol.
- (2) Any Boolean function can be implemented using only NOR gates.
- (3) A demultiplexer is a logic circuit that allows digital information from a single source to be routed onto several lines.
- (4) Addition in Boolean algebra is equivalent to the NOR function.
- (5) A truth table illustrates how the input level of a gate responds to all the possible output level combinations.
- (6) A NOR gate output is LOW if any of its inputs is LOW.
- (7) Good troubleshooting is done by looking at the input signal and how it interacts with the circuits.
- (8) A NAND gate output is LOW only if all the inputs are HIGH.
- (9) An exclusive-NOR gate output is HIGH when the inputs are unequal.
- (10) A full-adder has three inputs and two outputs.

Solution:

- (1) N
- (2) Y
- (3) Y
- (4) N
- (5) N
- (6) N
- (7) N
- (8) Y
- (9) N
- (10) Y

2. (15 points)

- (1) Convert the binary number 110011.11 into **Octal**;
- (2) Perform the subtraction of the **signed** numbers :

$$00110011 - 01101010, \quad (1)$$

i.e. subtract 01101010 from 00110011. Express your result in the 2's complement form.

- (3) Divide 01111010 by 00101000 using the 2's complement addition. Find the quotient and remainder in the binary form. Please show each calculation step.

Solution:

- (1) $(110011.11)_2 = (63.6)_8$;
- (2) 11001001

$$\begin{array}{r} 00110011 \\ + 10010110 \\ \hline 11001001 \end{array}$$

- (3) The quotient is $(0000011)_2 = 3$ whereas remainder is $(00000010)_2 = 2$.

Step 1:	$\begin{array}{r} 01111010 \\ + 11011000 \\ \hline 01010010 \end{array}$	Quotient: 00000001
Step:2:	$\begin{array}{r} 01010010 \\ + 11011000 \\ \hline 00101010 \end{array}$	Quotient: 00000010
Step:3:	$\begin{array}{r} 00101010 \\ + 11011000 \\ \hline 00000010 \end{array}$	Quotient: 00000011
Remainder: 00000010		

3. (10 points)

- (1) Multiply 01101010 by 11110001 in the 2's complement form. Note the resulting product may have more than eight bits.
- (2) Apply CRC to the data bits 10110010 using the generator code 1010 to produce the transmitted CRC code.

Solution:

- (1) The 2's complement form of 11110001 is 00001111. Thus, we have

$$\begin{array}{r}
 01101010 \\
 \times 00001111 \\
 \hline
 01101010 \\
 01101010 \\
 \hline
 100111110 \\
 01101010 \\
 \hline
 1011100110 \\
 01101010 \\
 \hline
 11000110110
 \end{array}$$

Finally, changing to 2's complement with sign, we have 100111001010.

- (2) The remainder can be found as follows:

$$\begin{array}{r}
 101100100000 \\
 \underline{1010} \downarrow \downarrow \downarrow \downarrow \downarrow \\
 1001 \downarrow \downarrow \downarrow \downarrow \downarrow \\
 \underline{1010} \downarrow \downarrow \downarrow \downarrow \downarrow \\
 1100 \downarrow \downarrow \downarrow \downarrow \downarrow \\
 \underline{1010} \downarrow \downarrow \downarrow \downarrow \downarrow \\
 1100 \downarrow \downarrow \downarrow \downarrow \downarrow \\
 \underline{1010} \downarrow \downarrow \downarrow \downarrow \downarrow \\
 1100 \downarrow \downarrow \downarrow \downarrow \downarrow \\
 \underline{1010} \downarrow \downarrow \downarrow \downarrow \downarrow \\
 1100 \downarrow \downarrow \downarrow \downarrow \downarrow \\
 \underline{1010} \\
 \text{Remainder} = 0110
 \end{array}$$

CRC is 101100100110.

4. (10 points)

(1) Design a one-bit basic comparator that implements the following truth table

Inputs		Output
A	B	$A = B$
0	0	1
0	1	0
1	0	0
1	1	1

Table 1: one-bit comparator

 


Figure 1: One-bit basic comparator

(2) Design a one-bit *inequality* comparator with the following truth table by using the one-bit basic comparator constructed in (1) and any necessary basic logic gates:

Inputs		Output		
A	B	$A < B$	$A = B$	$A > B$
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

Table 2: one-bit inequality comparator

 


Figure 2: One-bit inequality comparator

(3) Implement a two-bit inequality comparator using two one-bit inequality comparators designed in (2) and any necessary basic logic gates, assuming that A_1 and B_1 are the most significant bits.

 


Figure 3: The two-bit inequality comparator

Solution:

(1) One-bit basic comparator

 


Figure 4: One-bit basic comparator

(2) One-bit inequality comparator

 


Figure 5: One-bit inequality comparator

(3) Two-bit inequality comparator

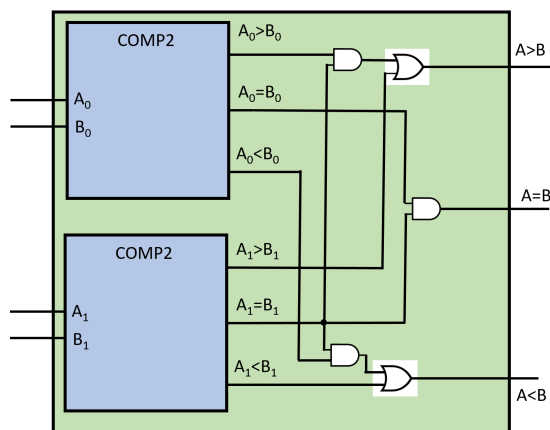


Figure 6: Two-bit inequality comparator

5. (10 points) The following figure shows a BCD-to-binary converter consisting of 4-bit adders.

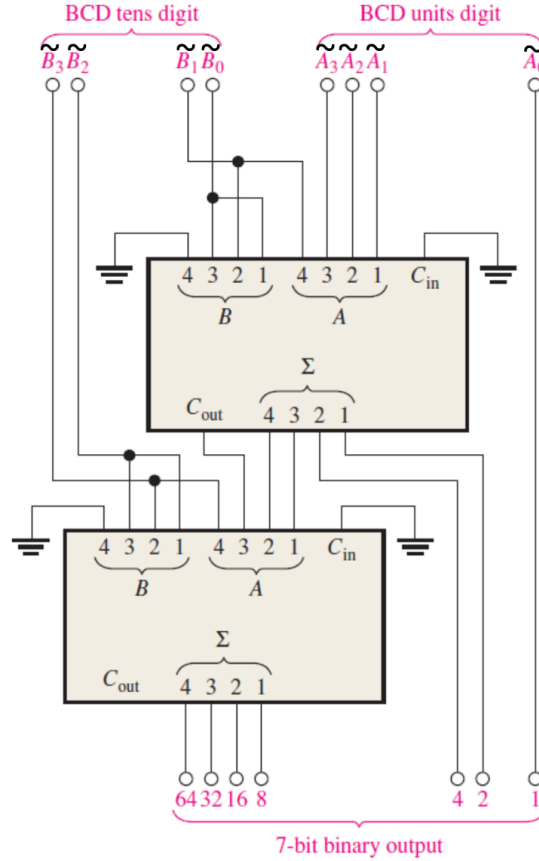


Figure 7: BCD-to-binary converter

- (1) Express the final binary output into *decimal* in terms of input $\tilde{B}_3, \tilde{B}_2, \tilde{B}_1, \tilde{B}_0, \tilde{A}_3, \tilde{A}_2, \tilde{A}_1, \tilde{A}_0$;
- (2) Given input $\tilde{B}_3\tilde{B}_2\tilde{B}_1\tilde{B}_0 = 0011$ and $\tilde{A}_3\tilde{A}_2\tilde{A}_1\tilde{A}_0 = 0101$, calculate the output C_{out} and $\Sigma_4\Sigma_3\Sigma_2\Sigma_1$ for both the top and bottom adders;
- (3) Explain why such a configuration of $B_3B_2B_1B_0$ can correctly convert BCD to binary.

Solution:

- (1) $Z = \tilde{B}_3 * 80 + \tilde{B}_2 * 40 + \tilde{B}_1 * 20 + \tilde{B}_0 * 10 + \tilde{A}_3 * 8 + \tilde{A}_2 * 4 + \tilde{A}_1 * 2 + \tilde{A}_0$
- (2) The top adder: $C_{\text{out}}^t = 1$ and $\Sigma_4^t\Sigma_3^t\Sigma_2^t\Sigma_1^t = 0001$.
The bottom adder: $C_{\text{out}}^b = 0$ and $\Sigma_4^b\Sigma_3^b\Sigma_2^b\Sigma_1^b = 0100$.
- (3) For input $\tilde{B}_0 = 1$, 10 can be represented as $8 + 2$. Similarly, input $\tilde{B}_1 = 1$, i.e. 20 can be represented by $16 + 4$. Since the least significant bit input \tilde{A}_0 is directly connected to the output, A_4, A_3, A_2 and A_1 of the top adder are actually weighted by 16, 8, 4 and 2, respectively. The same weighting configuration is also true for B_4, B_3, B_2 and B_1 . Therefore, input \tilde{B}_0 is connected to the B_1 and B_3 of the top adder whereas \tilde{B}_1 to A_4 and B_2 .
For the bottom adder, A_4, A_3, A_2 and A_1 are weighted by 64, 32, 16 and 8. By representing $80 = 64 + 16$ and $40 = 32 + 8$, we can connect input \tilde{B}_2 to B_1 and B_3 of the top adder whereas \tilde{B}_3 to A_4 and B_2 .

6. (10 points) Design a circuit with four input, namely A , B , C and D and one output Y . The output is 1 when there are at least three consecutive 1's or 0's in the inputs, e.g. 1110.

- (1) Develop the truth table for Y with four inputs A, B, C and D ;
- (2) Use a Karnaugh map to find the minimum **product of sums** (POS) form of Y ;

Solution:

- (1) The truth table for Y with four inputs A, B, C and D is given as follows:

Inputs				Output
A	B	C	D	Y
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

- (2) Use a Karnaugh map to find the minimum **product of sums** (POS) form of Y ;

$$Y = (\overline{B} + C) (\overline{A} + C + \overline{D}) (A + B + \overline{C}) (A + \overline{C} + D) (\overline{A} + B + \overline{C}) \quad (2)$$

CD		00	01	11	10
AB	00	1	1	0	0
	01	0	0	1	0
	11	0	0	1	1
	10	1	0	0	0

Figure 8: Karnaugh Map for Q.6.

7. (10 points) Given the circuit and input waveforms as shown below


 



Figure 9: Logic circuit and input waveforms for Q.4.

 - (1) Write the Boolean expression of X ;
- (2) Sketch the output waveform X in proper relation to the inputs.



Solution:

 - (1) $X = ABC + D\overline{E}$;
- (2) The output timing diagram is as follows:



8. (10 points) Implement the logic function specified in the following truth table by using a 4-input data selector and all necessary basic logic gates.

Inputs				Output
A_3	A_2	A_1	A_0	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

Table 3: The desired logic function table


 


Figure 10: The 4-input Logic Symbol


Solution:

Inputs		Output
A_3	A_2	Y
0	0	$A_1 A_0$
0	1	A_1
1	0	$A_1 + \overline{A_0}$
1	1	A_0

Table 4: The equivalent logic function table

 

 
9. (15 points) We implement a 1-bit full subtractor that performs the binary subtraction as shown below.



P and Q are 1-bit variables and B_{in} is the borrow input from the previous stage. It produces two outputs: the difference D and the borrow output B_{out} . The truth table describing the function of this 1-bit full subtractor is shown in the following table.

B_{in}	P	Q	D	B_{out}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	0
0	1	1	0	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	0
1	1	1	1	1

 
- (1) Derive the Boolean expressions for D and B_{out} using K-maps;
- (2) Implement D and B_{out} using all necessary basic logic gates;
- (3) Alternatively, we can design the 1-bit full subtractor above using a 3×8 decoder whose truth table is as shown below. Show your implementation with all necessary basic logic gates.



X	Y	Z	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Solution:

 
- (1) The logic expressions for D and B_{out} can be found as



$$D = \overline{B_{in}} \overline{P \oplus Q} + B_{in} (P \oplus Q) \quad (3)$$

$$B_{out} = \overline{P}Q + B_{in}Q + B_{in}\overline{P} \quad (4)$$

 (2) The subtractor can be implemented with basic logic gates as follows:



(3) Set X , Y and Z as B_{in} , P and Q respectively, we can use two four-input OR gates and the decoder to implement the full subtractor.

$$D = D_1 + D_2 + D_4 + D_7 \quad (5)$$

$$B_{out} = D_1 + D_4 + D_5 + D_7 \quad (6)$$