

ECE 2050 Digital Logic and Systems


# **Chapter 7 : Sequential Logic Design**

Instructor: Yue ZHENG, Ph.D.



 
# Last Week

- ❑ Half and Full Adders
- ❑ Parallel Binary Adders
- ❑ Ripple Carry and Look-Ahead Carry Adders
- ❑ Comparators
- ❑ Decoders ( $n$  input lines  $\rightarrow$  max.  $2^n$  output lines)
- ❑ Encoders (e.g. Decimal-to-BCD **Priority** Encoder)
- ❑ Code Converters (e.g. BCD-to-Binary Conversion)
- ❑ Multiplexers (To route several inputs onto a single output line)
- ❑ Demultiplexers
- ❑ Timing



*How to design a multiplier by FA/HA?*

 

# State Elements



# Introduction

- Outputs of sequential logic depend on current *and* prior input values – it has **memory**.
- Some definitions:
  - **State**: all the information about a circuit necessary to explain its future behavior
  - **Latches and flip-flops**: state elements that store one bit of state
  - **Synchronous sequential circuits**: Sequential circuits using flip-flops sharing a common clock



# Sequential Circuits

- Give sequence to events
- Have memory (short-term)
- Use feedback from output to input to store information



# State Elements

- **State:** everything about the prior inputs to the circuit necessary to predict its future behavior
  - Usually just 1 bit, the last value captured
- State elements store state
  - Bistable circuit
  - SR Latch
  - D Latch
  - D Flip-flop




# Bistable Circuit




# Bistable Circuit

- Fundamental building block of other state elements
- Two outputs:  $Q$ ,  $\overline{Q}$
- No inputs

**Same circuit!**

 

**Back-to-back inverters**


 


**Cross-coupled inverters**


  
# Bistable Circuit Analysis

- Consider the two possible cases:
  - **$Q = 0$ :**  
then  $\bar{Q} = 1$ ,  $Q = 0$  (consistent)
  - **$Q = 1$ :**  
then  $\bar{Q} = 0$ ,  $Q = 1$  (consistent)
- Stores 1 bit of state in the state variable,  $Q$  (or  $\bar{Q}$ )
- But there are **no inputs to control the state**




# SR Latch



# SR (Set/Reset) Latch

- **SR Latch**

 


- Consider the four possible cases:
  - **$S = 1, R = 0$**
  - **$S = 0, R = 1$**
  - **$S = 0, R = 0$**
  - **$S = 1, R = 1$**

# SR Latch Analysis


–  **$S = 1$** ,  $R = 0$ :  
then  **$Q = 1$**  and  **$\bar{Q} = 0$**

**Set the output**

 

–  $S = 0$ ,  **$R = 1$** :  
then  **$Q = 0$**  and  **$\bar{Q} = 1$**

**Reset the output**

 


# SR Latch Analysis

–  $S = 0, R = 0$ :

then  $Q = Q_{prev}$

**Memory!**

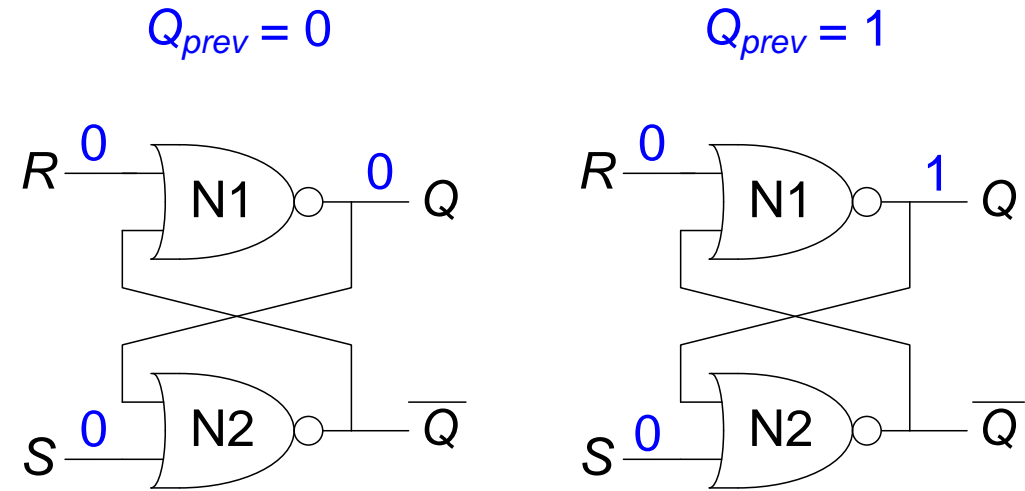


–  $S = 1, R = 1$ :

then  $Q = 0, \overline{Q} = 0$

**Invalid State**


$\overline{Q} \neq \text{NOT } Q$

 

# SR Latch

- **SR** stands for **S**et/**R**eset Latch
  - Stores one bit of state ( $Q$ )
- Control what value is being stored with  $S$ ,  $R$  inputs
  - **Set**: Make the output 1
    - $S = 1$ ,  $R = 0$ ,  $Q = 1$
  - **Reset**: Make the output 0
    - $S = 0$ ,  $R = 1$ ,  $Q = 0$
  - **Memory**: Retain value
    - $S = 0$ ,  $R = 0$ ,  $Q = Q_{prev}$
- **Must do something to avoid invalid state (when  $S = R = 1$ )**

SR Latch symbol

 


# D Latch



# D Latch


- **Two inputs:  $CLK$ ,  $D$** 
  - **$CLK$** : controls *when* the output changes
  - **$D$**  (the data input): controls *what* the output changes to
- **Function**
  - When  **$CLK = 1$** ,
    - $D$  passes through to  $Q$  (*transparent*)
  - When  **$CLK = 0$** ,
    - $Q$  holds its previous value (*opaque*)

D Latch  
Symbol

 



# D Latch Internal Circuit

 

$CLK$	$D$	$\overline{D}$	$S$	$R$	$Q$	$\overline{Q}$
0	X					
1	0					
1	1					

# D Flip Flop



# D Flip-Flop

- Inputs:  $CLK$ ,  $D$

- Truth Table:



Truth table for a positive edge-triggered D flip-flop.

Inputs		Outputs		Comments
$D$	$CLK$	$Q$	$\overline{Q}$	
0	↑	0	1	RESET
1	↑	1	0	SET

↑ = clock transition LOW to HIGH


- Called **edge-triggered**
  - Activated on the *clock edge*

D Flip-Flop Symbols

  

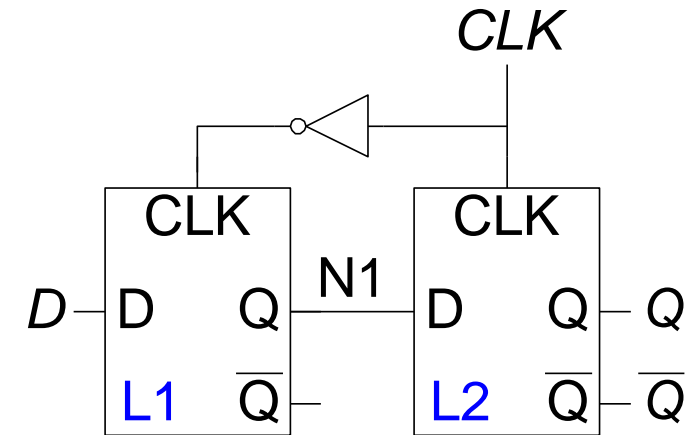
# D Flip-Flop Internal Circuit

- **Two back-to-back D latches** (L1 and L2) controlled by complementary clocks
- When **CLK = 0**
  - L1 is transparent
  - L2 is opaque
  - **D** passes through to **N1**
- When **CLK = 1**
  - L2 is transparent
  - L1 is opaque
  - **N1** passes through to **Q**
- Thus, on the edge of the clock (when **CLK rises from 0 → 1**)
  - **D** passes through to **Q**



 
# Edge-Triggered Operation

- By exploiting a small delay through the inverter on one input to the NAND gate, generate a very short-duration spike on the positive-going transition of the clock pulse.




A type of pulse transition detector


# D Latch vs. D Flip-Flop

 

D Latch

 

D Flip-flop

 

# J-K Flip Flop



# J-K Flip Flop

- Inputs:  $CLK$ ,  $J$ ,  $K$

- Truth Table:

Truth table for a positive edge-triggered J-K flip-flop.

Inputs			Outputs		Comments
$J$	$K$	$CLK$	$Q$	$\overline{Q}$	
0	0	↑	$Q_0$	$\overline{Q}_0$	No change
0	1	↑	0	1	RESET
1	0	↑	1	0	SET
1	1	↑	$\overline{Q}_0$	$Q_0$	Toggle


↑ = clock transition LOW to HIGH

$Q_0$  = output level prior to clock transition

- Toggle State**



# J-K Flip-Flop Internal Circuit

 


J	K	$Q_N$	$Q_{N+1}$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0


# Variations on a Flop



# Registers: One or More Flip-Flops

 


4-bit Register

 

4-bit Register
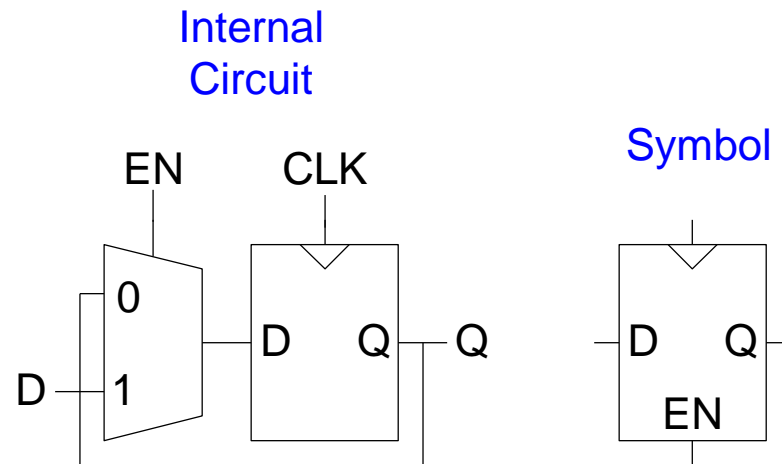
# Enabled Flip-Flops


- **Inputs:**  $CLK$ ,  $D$ ,  $EN$ 
  - The enable input ( $EN$ ) controls when new data ( $D$ ) is stored
- **Function**
  - $EN = 1$ :  $D$  passes through to  $Q$  on the clock edge
  - $EN = 0$ : the flip-flop retains its previous state



# Resettable Flip-Flops


- **Inputs:** *CLK*, *D*, *Reset*
- **Function:**
  - **Reset = 1:** Q is forced to 0
  - **Reset = 0:** flip-flop behaves

## Symbols

 
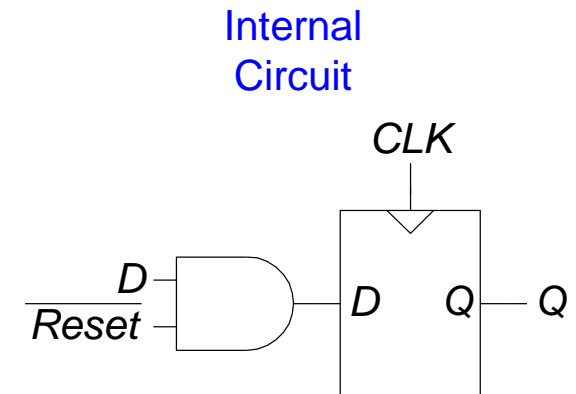
# Resettable Flip-Flops


- Two types:
  - **Synchronous:** resets at the clock edge only
  - **Asynchronous:** resets immediately when  $Reset = 1$
- **Asynchronously** resettable flip-flop requires changing the internal circuitry of the flip-flop
- **Synchronously** resettable flip-flop?



# Settable Flip-Flops

- **Inputs:** *CLK*, *D*, *Set*
- **Function:**
  - **Set = 1:** Q is set to 1
  - **Set = 0:** the flip-flop behaves as ordinary D flip-flop

## Symbols

 

# Chapter Review

- ☐ State Elements
- ☐ Bistable Circuit
- ☐ D Latch
- ☐ D Flip Flop
- ☐ J-K Flip Flop
- ☐ Variations on a Flop
  - ☐ Registers
  - ☐ Enabled Flip-Flops
  - ☐ Resettable Flip-Flops
  - ☐ Settable Flip-Flops





# True/False Quiz



A latch has one stable state.



A latch is considered to be in the RESET state when the Q output is low.



A gated D latch cannot be used to change state.



Flip-flops and latches are both bistable devices.



An edge-triggered D flip-flop changes state whenever the D input changes.



A clock input is necessary for an edge-triggered flip-flop.



When both the J and K inputs are HIGH, an edge-triggered J-K flip-flop changes state on each clock pulse.

