

ECE 2050 Digital Logic and Systems

# Chapter 10 : Counters

Instructor: Tinghuan CHEN, Ph.D.



# Last Week


- ❑ (Synchronous) Sequential Logic Counters
- ❑ Finite State Machine
  - ❑ Moore FSM
  - ❑ Mealy FSM
- ❑ Timing
  - ❑ Setup time
  - ❑ Hold time
  - ❑ Aperture time
  - ❑ Propagation delay
  - ❑ Contamination delay
  - ❑ Dynamic Discipline

# Counters

- Increments on each clock edge
- Used to cycle through numbers. For example,
  - 000, 001, 010, 011, 100, 101, 110, 111, 000, 001...
- **Example uses:**
  - Digital clock displays
  - Program counter: keeps track of current instruction executing

**Symbol**

**Implementation**

 


# Asynchronous Counters


 
# Asynchronous Counters


- An asynchronous counter is one in which the flip-flops (FF) within the counter do not have a common clock;



- The 2-bit asynchronous counter counts # of clock pulses up to 3, and on the 4<sup>th</sup> pulse, it recycles to its original state ( $Q_0 = Q_1 = 0$ ).

Binary state sequence for the counter in Figure 9–4.

Clock Pulse	$Q_1$	$Q_0$
Initially	0	0
1	0	1
2	1	0
3	1	1
4 (recycles)	0	0

 

# A 3-Bit Asynchronous Binary Counter

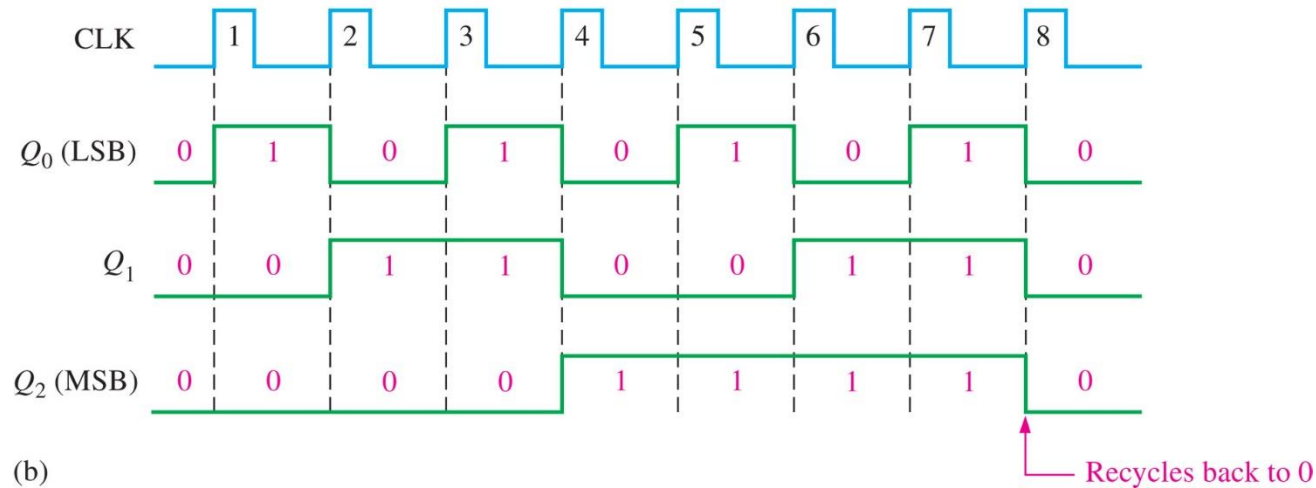
 



TABLE 9-2

State sequence for a 3-bit binary counter.

Clock Pulse	$Q_2$	$Q_1$	$Q_0$
Initially	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8 (recycles)	0	0	0

- ❑ Commonly referred to as **ripple** counters;
- ❑ The **cumulative delay** of asynchronous counters is a major drawback.

# Propagation Delay

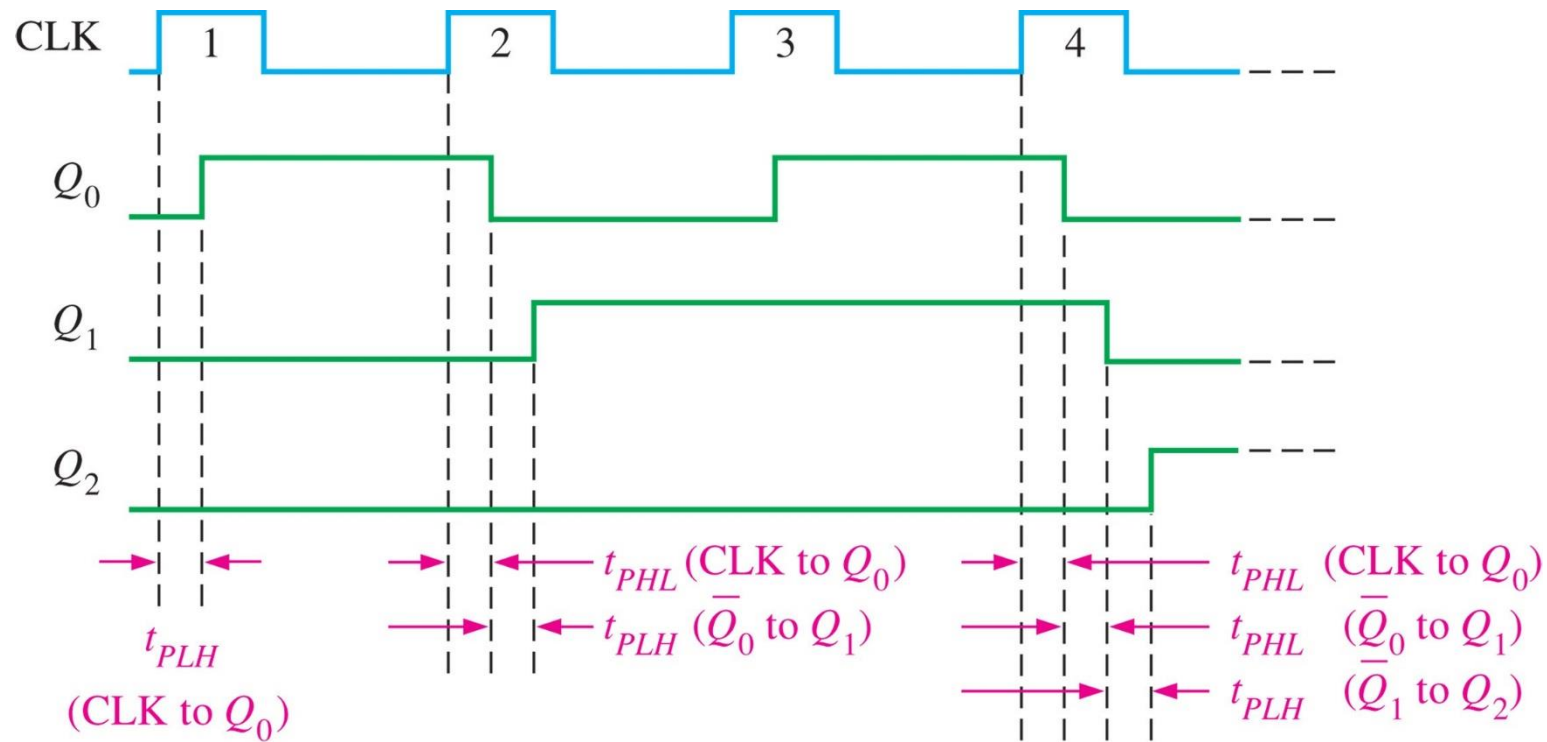


- If each D flip-flop has a propagation delay for  $t$  second, then
- The total delay time:  $t_{p(tot)} = t * \# \text{ of D flip-flops}$
- The maximum clock frequency:  $f_{max} = 1 / t_{p(tot)}$

# Asynchronous Decade Counters

- ❑ Modulus: # of unique states through which the counter will sequence.
- ❑ Maximum modulus:  $2^n$  for a counter of  $n$  flip-flops.
- ❑ Counters can have less than  $2^n$  states, called a truncated sequence.
- ❑ Example: A **decade** counter with four flip-flops counts a truncated sequence from 0000 through 1001

1010 ↔ 0000

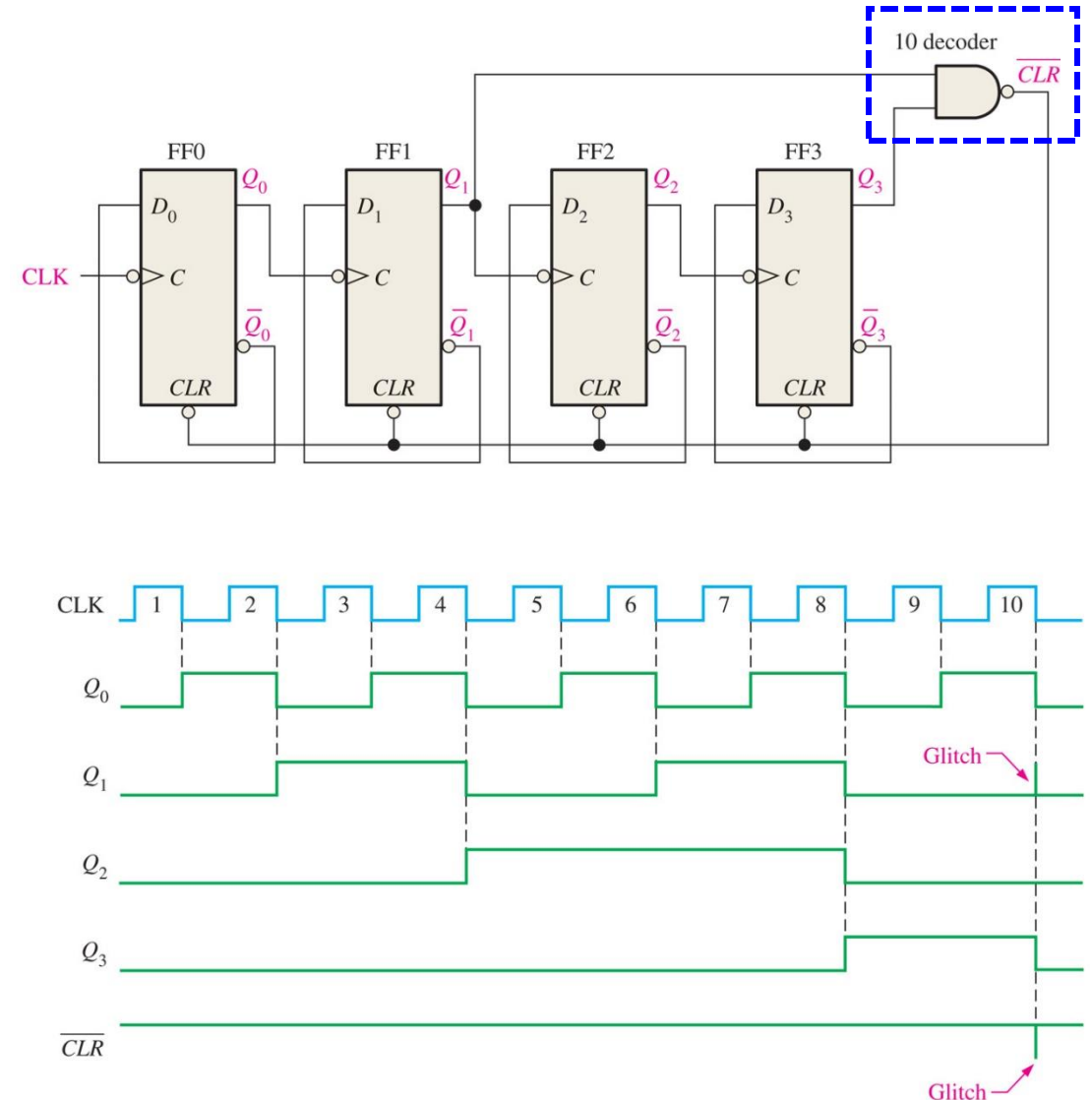**Glitch:** the counter is in the 1010 state for a short time before it is reset to 0000







# Example 9–2 with J-K Flip-Flops

- J and K inputs are both HIGH  $\rightarrow$  Flip-flops toggle between S/R states

1100  $\leftrightarrow$  0000

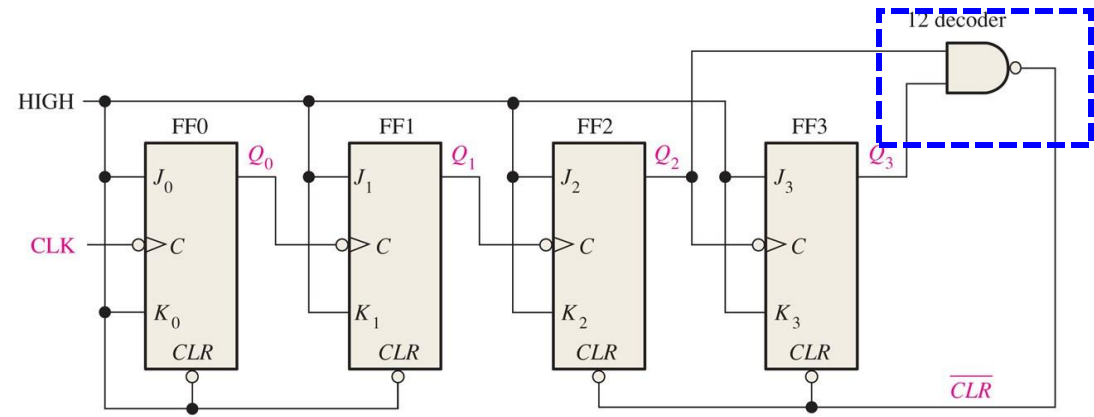

(a)

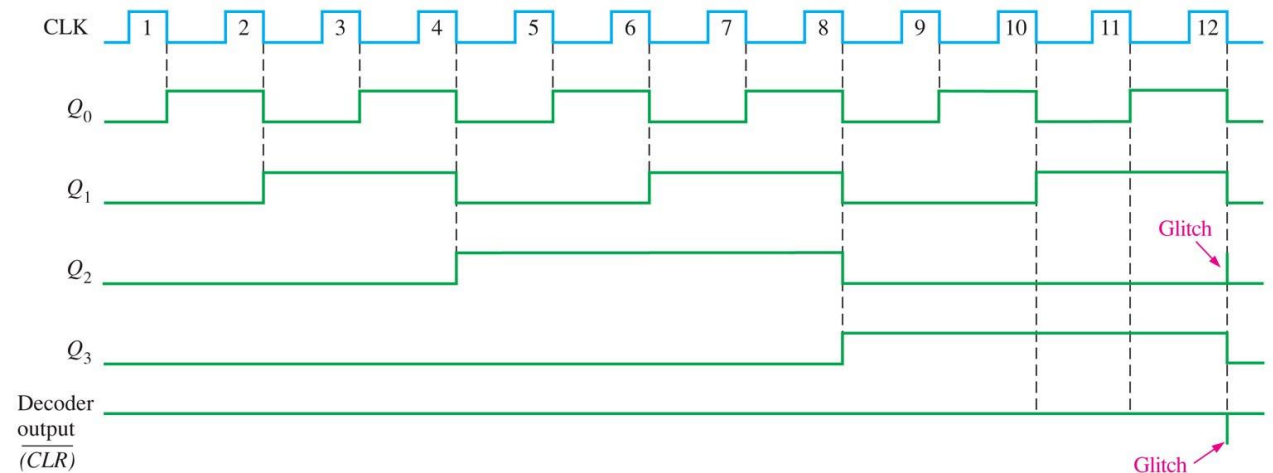



(b)

# Synchronous Counters



  
# Synchronous Counters

- Synchronous: All flip-flops are controlled by the same clock
- Both J and K inputs are connected to HIGH
- Example: A **synchronous** counter with two flip-flops counts a sequence from 00 through 11 in four clock pulses



# A 3-Bit Synchronous Binary Counter

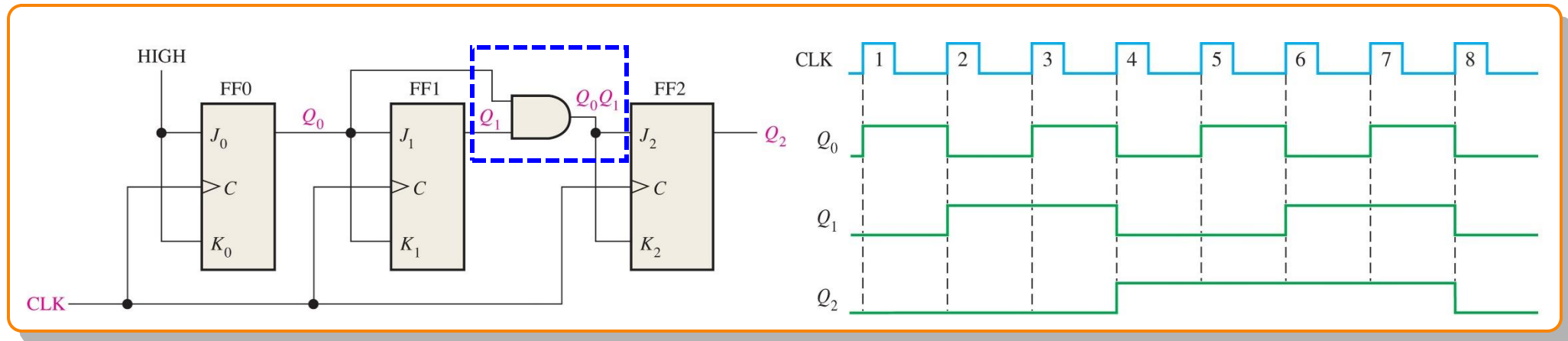



Summary of the analysis of the counter in Figure 9–15.

Clock Pulse	Outputs			J-K Inputs						At the Next Clock Pulse		
	$Q_2$	$Q_1$	$Q_0$	$J_2$	$K_2$	$J_1$	$K_1$	$J_0$	$K_0$	FF2	FF1	FF0
Initially	0	0	0	0	0	0	0	1	1	NC*	NC	Toggle
1	0	0	1	0	0	1	1	1	1	NC	Toggle	Toggle
2	0	1	0	0	0	0	0	1	1	NC	NC	Toggle
3	0	1	1	1	1	1	1	1	1	Toggle	Toggle	Toggle
4	1	0	0	0	0	0	0	1	1	NC	NC	Toggle
5	1	0	1	0	0	1	1	1	1	NC	Toggle	Toggle
6	1	1	0	0	0	0	0	1	1	NC	NC	Toggle
7	1	1	1	1	1	1	1	1	1	Toggle	Toggle	Toggle

Counter recycles back to 000.

NC: No Change

# A 4-Bit Synchronous **Decade** Counter

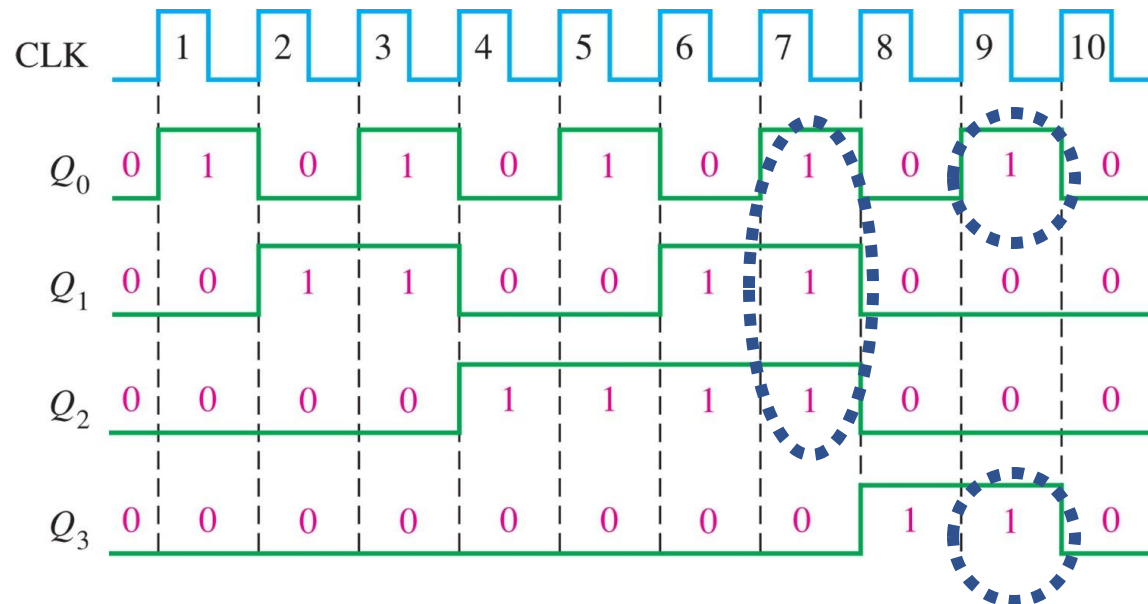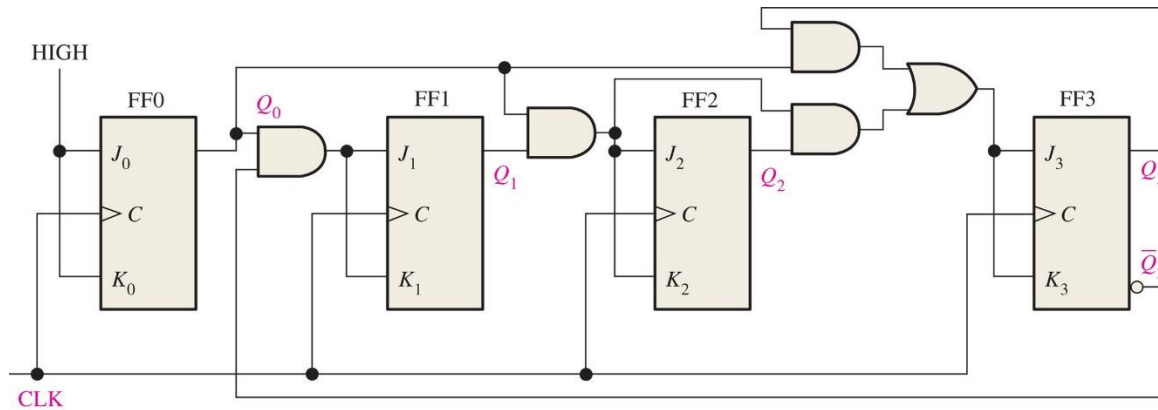

**TABLE 9-5**

States of a BCD decade counter.

Clock Pulse	$Q_3$	$Q_2$	$Q_1$	$Q_0$
Initially	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10 (recycles)	0	0	0	0

$$J_1 = K_1 = Q_0 \bar{Q}_3$$


$$J_2 = K_2 = Q_0 Q_1$$

$$J_3 = K_3 = Q_0 Q_1 Q_2 + Q_0 Q_3$$


The derivation of the expressions above will be discussed in detail later.
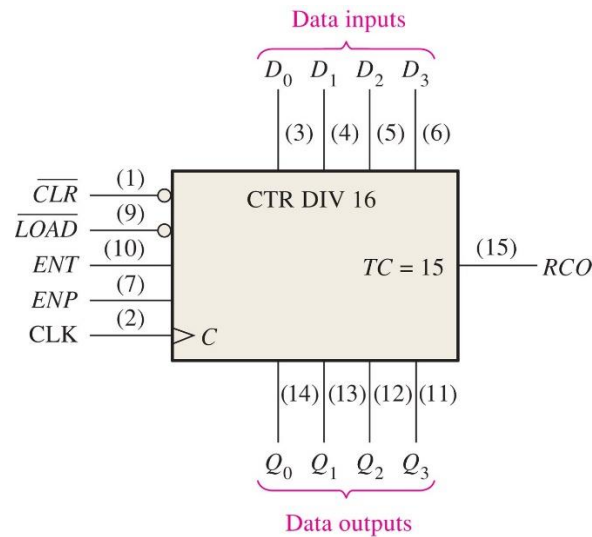
# 4-Bit Synchronous Binary Counter

74HC163 4-bit  
synchronous  
binary counter.



- When  $\overline{LOAD}$  is LOW, the counter will load  $D_3D_2D_1D_0$  on the next clock pulse  $\rightarrow$  the counter sequence can be started with any 4-bit binary number.
- The ripple clock output (RCO) goes HIGH when the counter reaches the last state in its sequence of fifteen, called the terminal count (TC = 15).
- 2 enable inputs,  $ENP$  and  $ENT$ , must both be HIGH for the CTR to sequence through its binary states

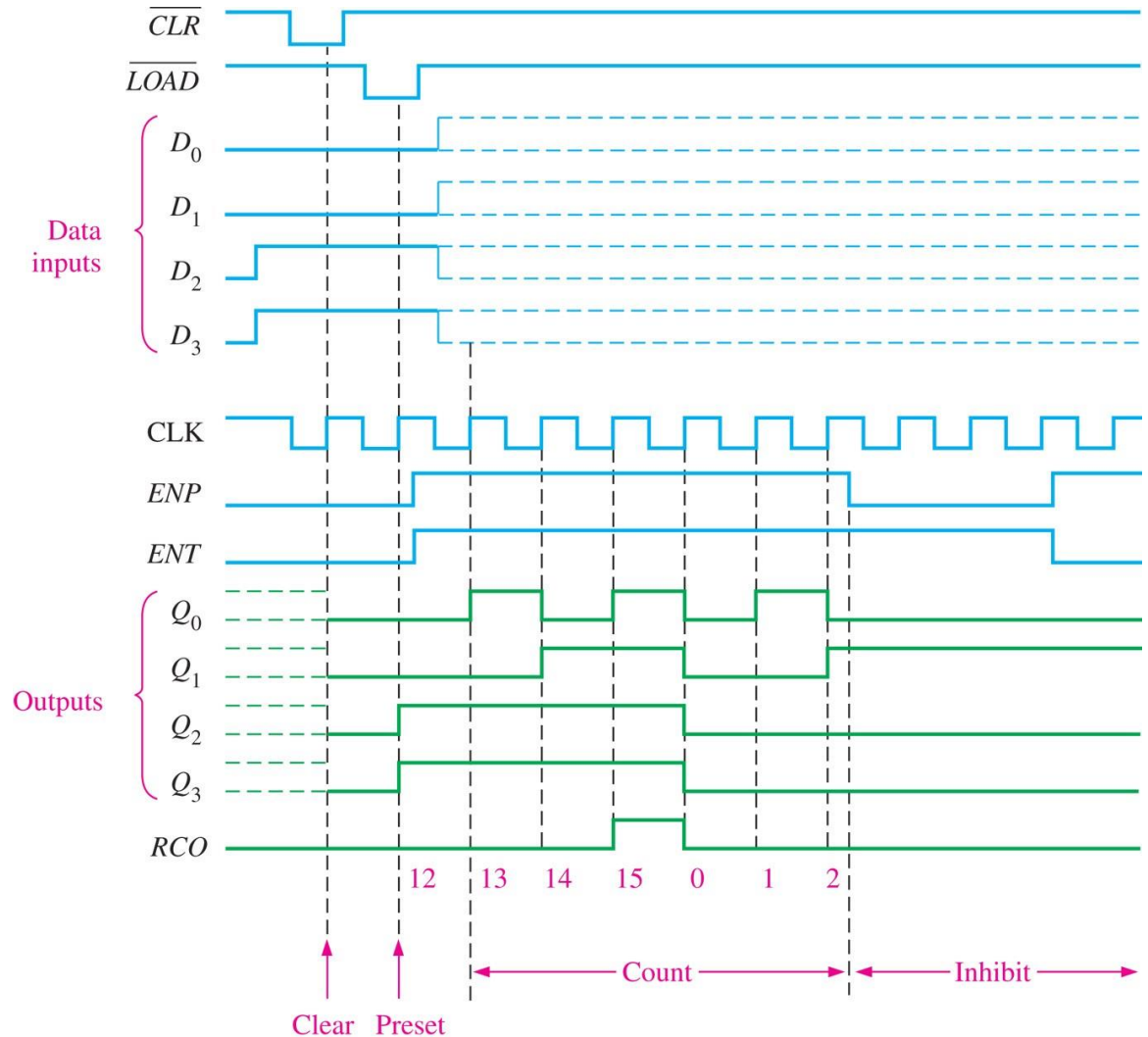

# Up/Down Synchronous Counters



# Up/Down Synchronous Counters


Up/Down sequence for a 3-bit binary counter.

Clock Pulse	Up	$Q_2$	$Q_1$	$Q_0$	Down
0	↶	0	0	0	↷
1	↶	0	0	1	↷
2	↶	0	1	0	↷
3	↶	0	1	1	↷
4	↶	1	0	0	↷
5	↶	1	0	1	↷
6	↶	1	1	0	↷
7	↶	1	1	1	↷

$$J_0 = K_0 = 1$$

$$J_1 = K_1 = (Q_0 \cdot \text{UP}) + (\bar{Q}_0 \cdot \text{DOWN})$$
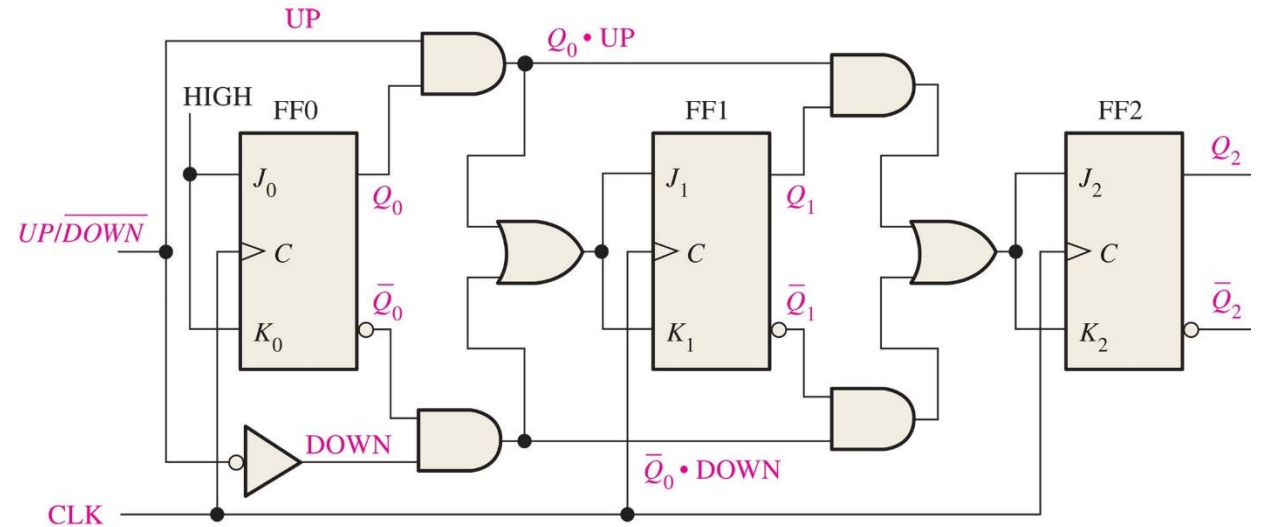
$$J_2 = K_2 = (Q_0 \cdot Q_1 \cdot \text{UP}) + (\bar{Q}_0 \cdot \bar{Q}_1 \cdot \text{DOWN})$$



Again, the derivation of the expressions above will be discussed in detail later.

- Also known as the **bidirectional counter** that can progress in either direction
- In general, an UP/Down counter can be reversed at any point in its sequence



# Up/Down Synchronous Counters


Up/Down sequence for a 3-bit binary counter.

Clock Pulse	Up	$Q_2$	$Q_1$	$Q_0$	Down
0	↶	0	0	0	↷
1	↶	0	0	1	↷
2	↶	0	1	0	↷
3	↶	0	1	1	↷
4	↶	1	0	0	↷
5	↶	1	0	1	↷
6	↶	1	1	0	↷
7	↶	1	1	1	↷

$$J_0 = K_0 = 1$$

$$J_1 = K_1 = (Q_0 \cdot \text{UP}) + (\bar{Q}_0 \cdot \text{DOWN})$$
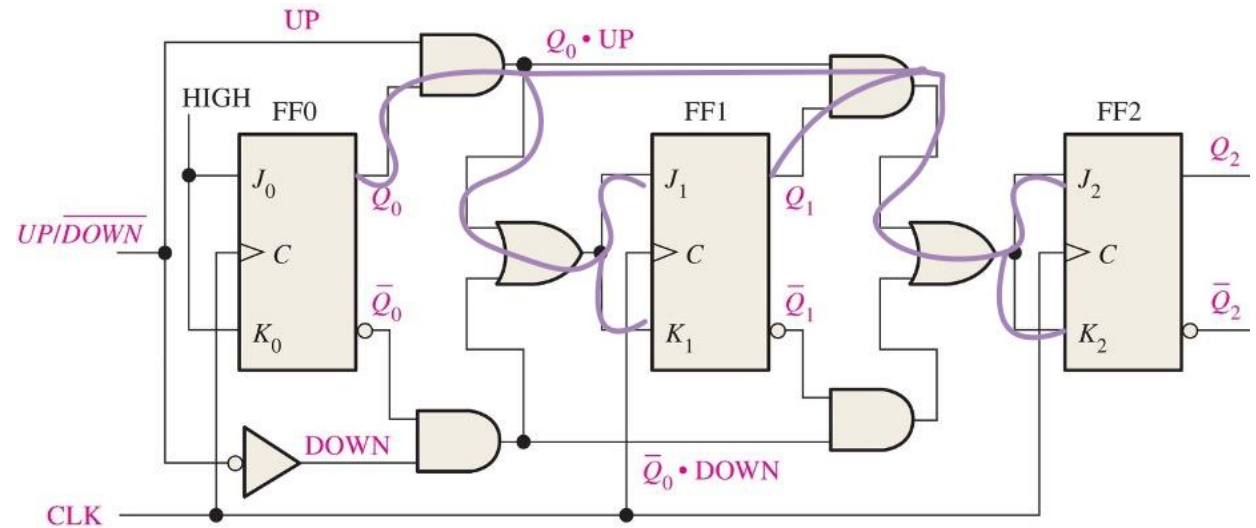
$$J_2 = K_2 = (Q_0 \cdot Q_1 \cdot \text{UP}) + (\bar{Q}_0 \cdot \bar{Q}_1 \cdot \text{DOWN})$$



Again, the derivation of the expressions above will be discussed in detail later.

- Also known as the **bidirectional counter** that can progress in either direction
- In general, an UP/Down counter can be reversed at any point in its sequence

# Up/Down Synchronous Counters


Up/Down sequence for a 3-bit binary counter.

Clock Pulse	Up	$Q_2$	$Q_1$	$Q_0$	Down
0	↶	0	0	0	↷
1	↶	0	0	1	↷
2	↶	0	1	0	↷
3	↶	0	1	1	↷
4	↶	1	0	0	↷
5	↶	1	0	1	↷
6	↶	1	1	0	↷
7	↶	1	1	1	↷

$$J_0 = K_0 = 1$$

$$J_1 = K_1 = (Q_0 \cdot \text{UP}) + (\bar{Q}_0 \cdot \text{DOWN})$$
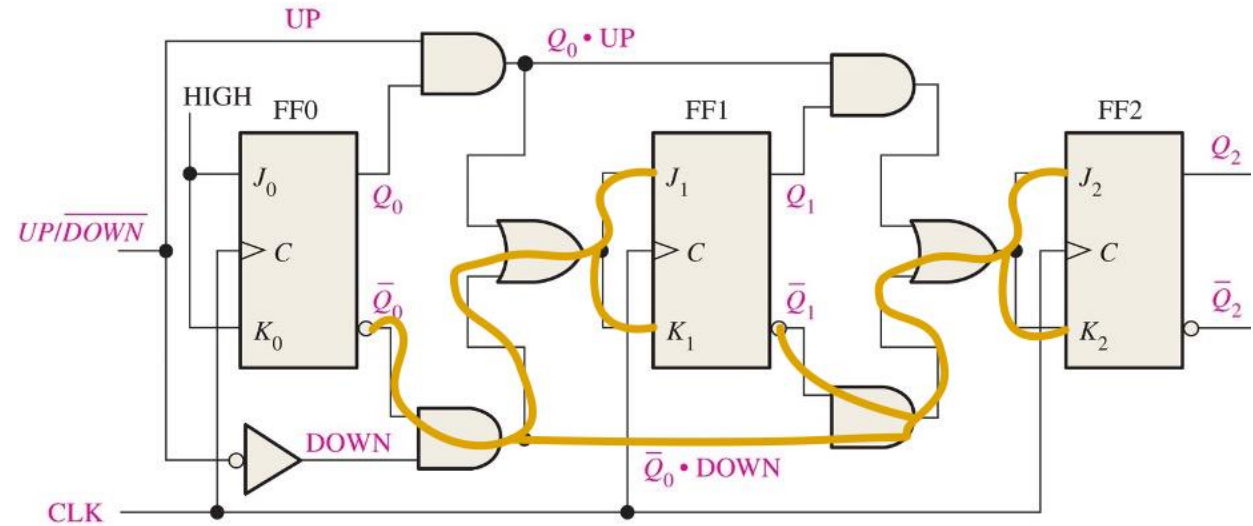
$$J_2 = K_2 = (Q_0 \cdot Q_1 \cdot \text{UP}) + (\bar{Q}_0 \cdot \bar{Q}_1 \cdot \text{DOWN})$$




Again, the derivation of the expressions above will be discussed in detail later.


- Also known as the **bidirectional counter** that can progress in either direction
- In general, an UP/Down counter can be reversed at any point in its sequence
 
# Example

- The direction of the count is determined by the level of the up/down input ( $D/\bar{U}$ ). When this input is HIGH, the counter counts down; when it is LOW, the counter counts up.



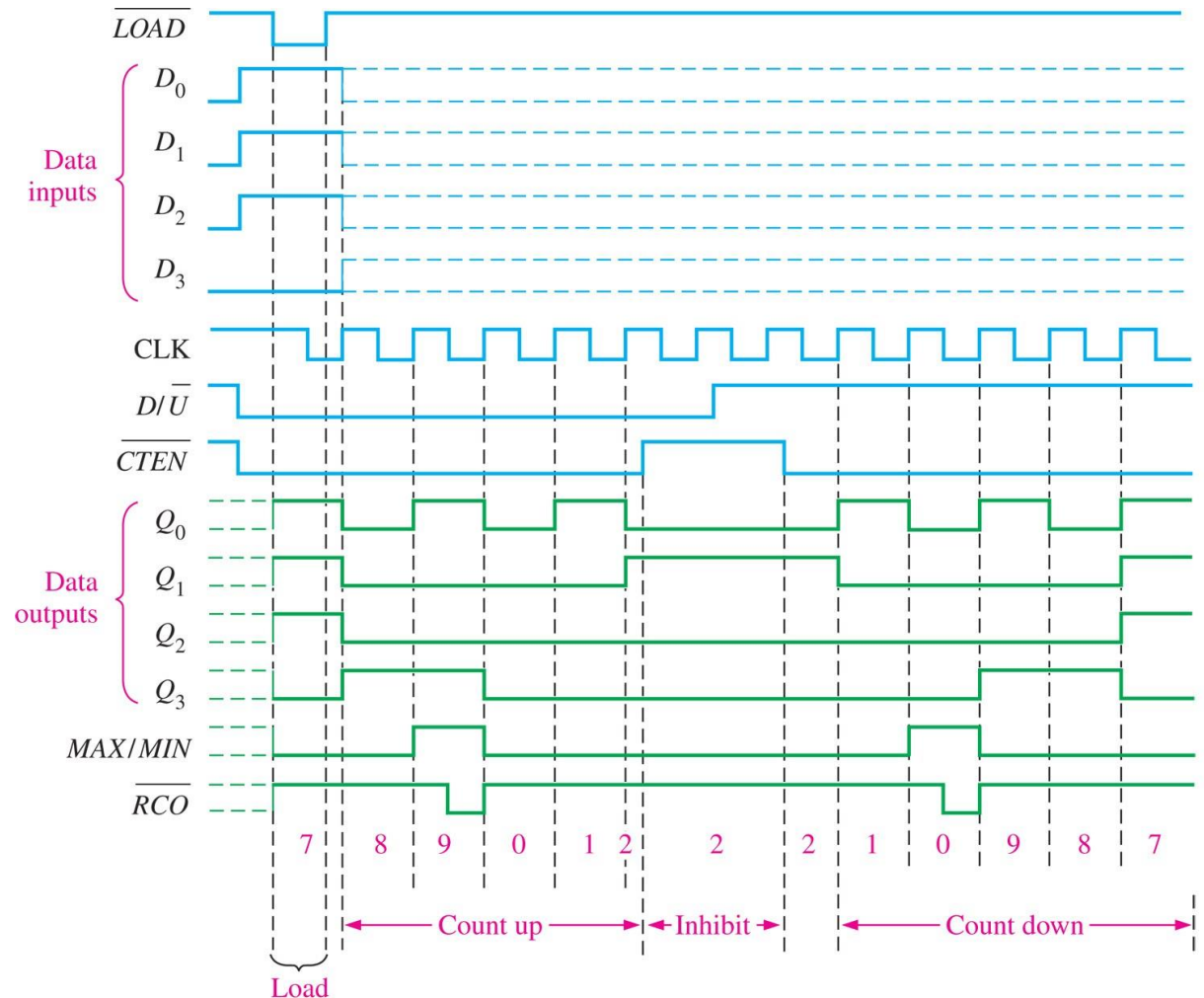74HC190 : a U/D synchronous decade counter



# Design of Synchronous Counters




# Design of Synchronous Counters (I)

- Step 1: State Diagram
- Step 2: Next-State Table
- Step 3: Flip-Flop Transition Table
- Step 4: Karnaugh Maps
- Step 5: Logic Expressions for Flip-Flop Inputs
- Step 6: Counter Implementation

# Example

- Step 1: State Diagram

 

- Step 2: Next-State Table

Next-state table for 3-bit Gray code counter.

Present State			Next State		
$Q_2$	$Q_1$	$Q_0$	$Q_2$	$Q_1$	$Q_0$
0	0	0	0	0	1
0	0	1	0	1	1
0	1	1	0	1	0
0	1	0	1	1	0
1	1	0	1	1	1
1	1	1	1	0	1
1	0	1	1	0	0
1	0	0	0	0	0

- Step 3: Flip-Flop Transition Table

Transition table for a J-K flip-flop.

Output Transitions		Flip-Flop Inputs	
$Q_N$	$Q_{N+1}$	$J$	$K$
0	→ 0	0	X
0	→ 1	1	X
1	→ 0	X	1
1	→ 1	X	0


# Example: Cont'd

- Step 4: Karnaugh Maps

Next-state table for 3-bit Gray code counter.

Present State			Next State		
$Q_2$	$Q_1$	$Q_0$	$Q_2$	$Q_1$	$Q_0$
0	0	0	0	0	1
0	0	1	0	1	1
0	1	1	0	1	0
0	1	0	1	1	0
1	1	0	1	1	1
1	1	1	1	0	1
1	0	1	1	0	0
1	0	0	0	0	0

$J_0$	$K_0$
1	X
X	0
X	1
0	X
1	X
X	0
X	1
0	X

 

# Example: Cont'd

- Step 5: Logic Expressions for Flip-Flop Inputs

$Q_2Q_1 \backslash Q_0$		0	1
00		0	0
01		1	0
11		X	X
10		X	X

$J_2$  map

$Q_2Q_1 \backslash Q_0$		0	1
00		0	1
01		X	X
11		X	X
10		0	0

$J_1$  map

$Q_2Q_1 \backslash Q_0$		0	1
00		1	X
01		0	X
11		1	X
10		0	X

$J_0$  map

$Q_2Q_1 \backslash Q_0$		0	1
00		X	X
01		X	X
11		0	0
10		1	0

$K_2$  map

$Q_2Q_1 \backslash Q_0$		0	1
00		X	X
01		0	0
11		0	1
10		X	X

$K_1$  map

$Q_2Q_1 \backslash Q_0$		0	1
00		X	0
01		X	1
11		X	0
10		X	1

$K_0$  map

$$J_0 = Q_2Q_1 + \bar{Q}_2\bar{Q}_1 = \overline{Q_2 \oplus Q_1}$$

$$K_0 = Q_2\bar{Q}_1 + \bar{Q}_2Q_1 = Q_2 \oplus Q_1$$

$$J_1 = \bar{Q}_2Q_0$$

$$K_1 = Q_2Q_0$$

$$J_2 = Q_1\bar{Q}_0$$

$$K_2 = \bar{Q}_1\bar{Q}_0$$



# Example: Cont'd

- Step 6: Counter Implementation

$$J_0 = Q_2 Q_1 + \bar{Q}_2 \bar{Q}_1 = \overline{Q_2 \oplus Q_1}$$


$$K_0 = Q_2 \bar{Q}_1 + \bar{Q}_2 Q_1 = Q_2 \oplus Q_1$$

$$J_1 = \bar{Q}_2 Q_0$$


$$K_1 = Q_2 Q_0$$

$$J_2 = Q_1 \bar{Q}_0$$

$$K_2 = \bar{Q}_1 \bar{Q}_0$$

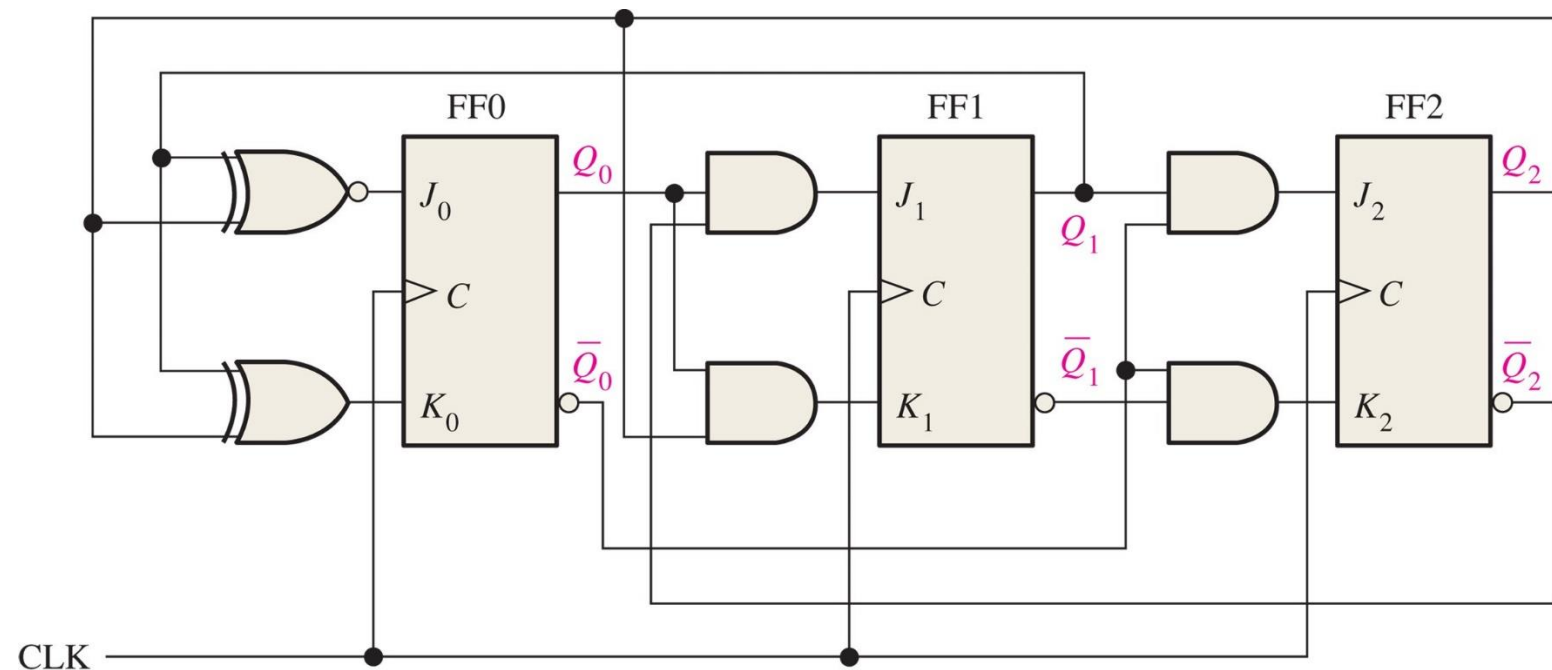

# More Example

 

**Step 2**

Next-state table.


Present State			Next State		
$Q_2$	$Q_1$	$Q_0$	$Q_2$	$Q_1$	$Q_0$
0	0	1	0	1	0
0	1	0	1	0	1
1	0	1	1	1	1
1	1	1	0	0	1

**Step 3**

Transition table for a D flip-flop.

Output Transitions		Flip-Flop Input
$Q_N$	$Q_{N+1}$	$D$
0	0	0
0	1	1
1	0	0
1	1	1

**Step 4**

 


**Step 5**

$$D_0 = \bar{Q}_0 + Q_2$$


$$D_1 = \bar{Q}_1$$

$$D_2 = \bar{Q}_0 + Q_2 \bar{Q}_1$$

**Step 6**

 
 
# Example: Synchronous 3-bit U/D Counters



Step 3  
Transition table for a J-K flip-flop.

Output Transitions		Flip-Flop Inputs	
$Q_N$	$Q_{N+1}$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0


$Q_N$ : present state  
 $Q_{N+1}$ : next state  
 X: "don't care"

Step 2

Next-state table for 3-bit up/down Gray code counter.

Present State			Next State					
			Y = 0 (DOWN)			Y = 1 (UP)		
$Q_2$	$Q_1$	$Q_0$	$Q_2$	$Q_1$	$Q_0$	$Q_2$	$Q_1$	$Q_0$
0	0	0	1	0	0	0	0	1
0	0	1	0	0	0	0	1	1
0	1	1	0	0	1	0	1	0
0	1	0	0	1	1	1	1	0
1	1	0	0	1	0	1	1	1
1	1	1	1	1	0	1	0	1
1	0	1	1	1	1	1	0	0
1	0	0	1	0	1	0	0	0

Y = UP/DOWN control input.

 

- The counter should count up when UP/DOWN is 1 and count down when 0.

$$J_0 = Q_2 Q_1 Y + Q_2 \bar{Q}_1 \bar{Y} + \bar{Q}_2 \bar{Q}_1 Y + \bar{Q}_2 Q_1 \bar{Y}$$

$$J_1 = \bar{Q}_2 Q_0 Y + Q_2 Q_0 \bar{Y}$$

$$J_2 = Q_1 \bar{Q}_0 Y + \bar{Q}_1 \bar{Q}_0 \bar{Y}$$

$$K_0 = \bar{Q}_2 \bar{Q}_1 \bar{Y} + \bar{Q}_2 Q_1 Y + Q_2 \bar{Q}_1 Y + Q_2 Q_1 \bar{Y}$$

$$K_1 = \bar{Q}_2 Q_0 \bar{Y} + Q_2 Q_0 Y$$

$$K_2 = Q_1 \bar{Q}_0 \bar{Y} + \bar{Q}_1 \bar{Q}_0 Y$$



Step 5

# Cascaded Counters



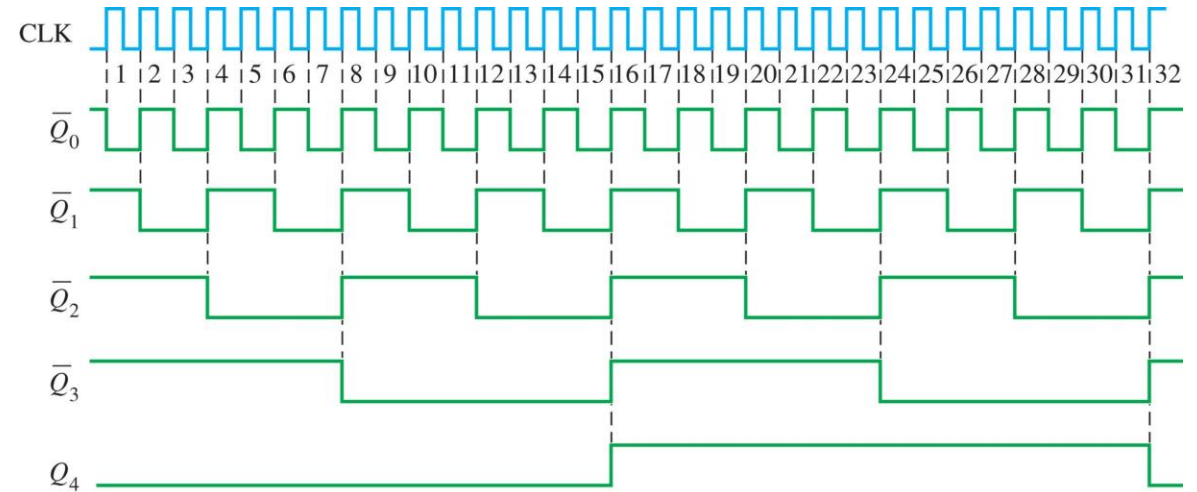
 
# Cascaded Counters: Asynchronous

- The overall modulus of the two cascaded counters is  $4 * 8 = 32$ ; that is, they act as a divide-by-32 counter.


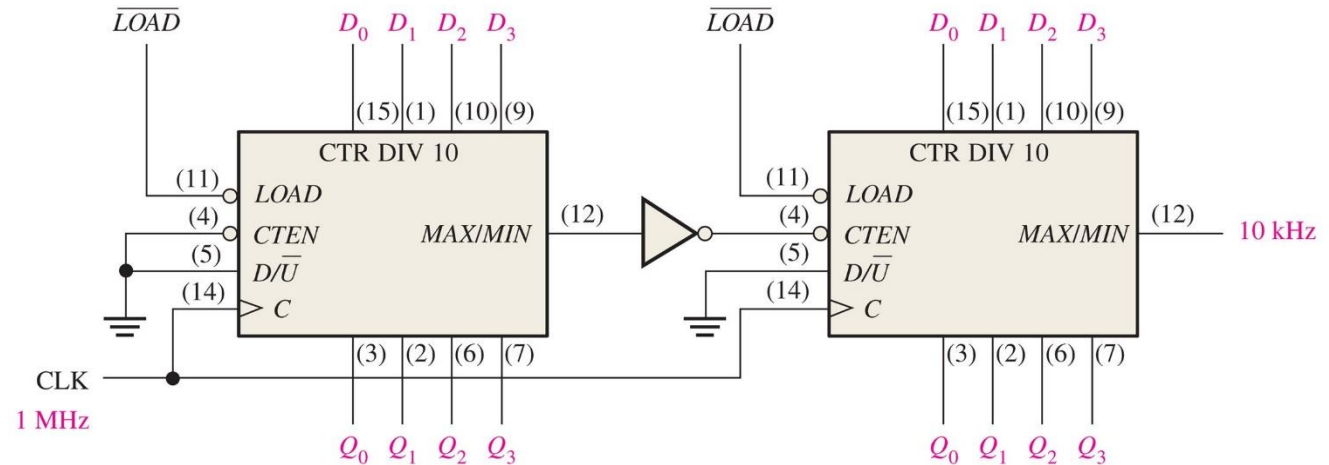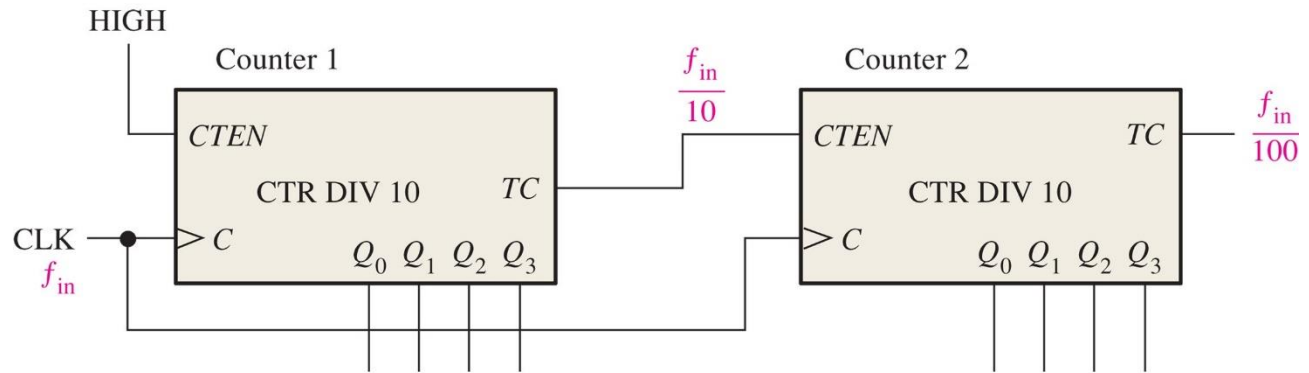
# Cascaded Counters: Synchronous


- The overall modulus of these two cascaded counters is  $10 * 10 = 100$ .
- A divide-by-100 counter using two 74HC190 up/down decade counters connected for the up sequence.



# Cascaded Counters with Truncated Sequences

- Full-modulus cascading: the resulting overall modulus is the product of the individual moduli of all the cascaded counters.
- If the required modulus is less than that achieved by full modulus cascading, a truncated sequence must be implemented with cascaded counters.
- Example: to achieve a modulus-40,000 counter with four cascaded 74HC161s whose full modulus is  $2^{16}=65,536$ , we preset the cascaded counter to 25,536 (63C0 in hexadecimal) each time it recycles.


$$65,536 - 25536 = 40,000$$

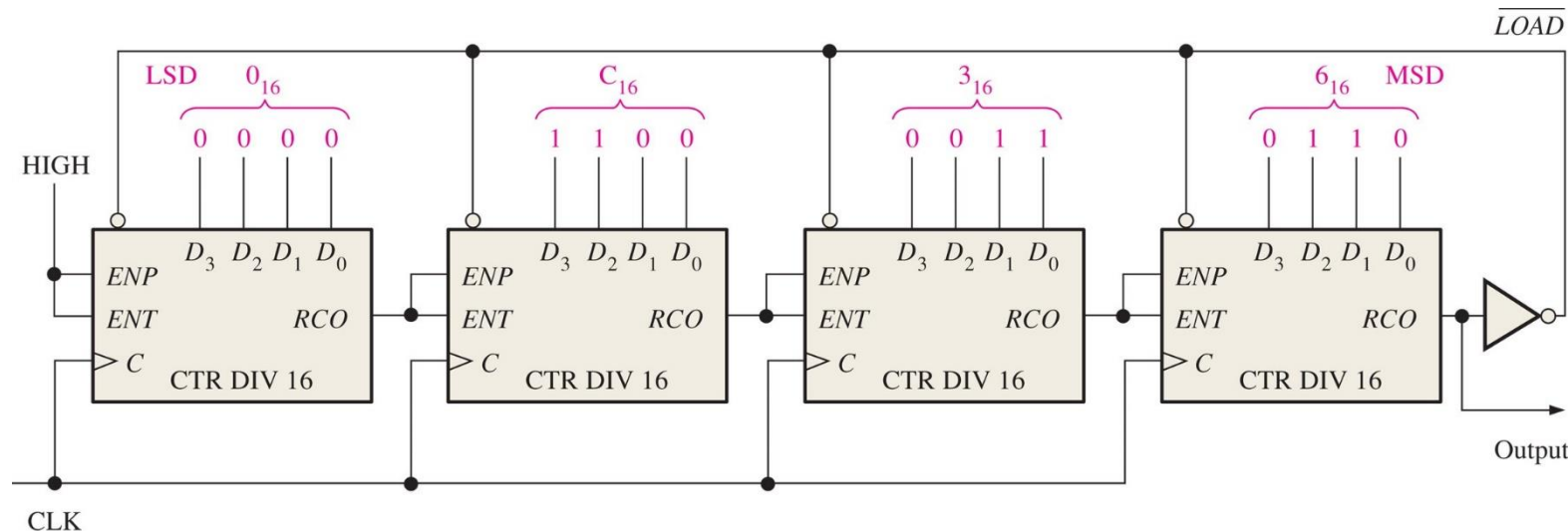


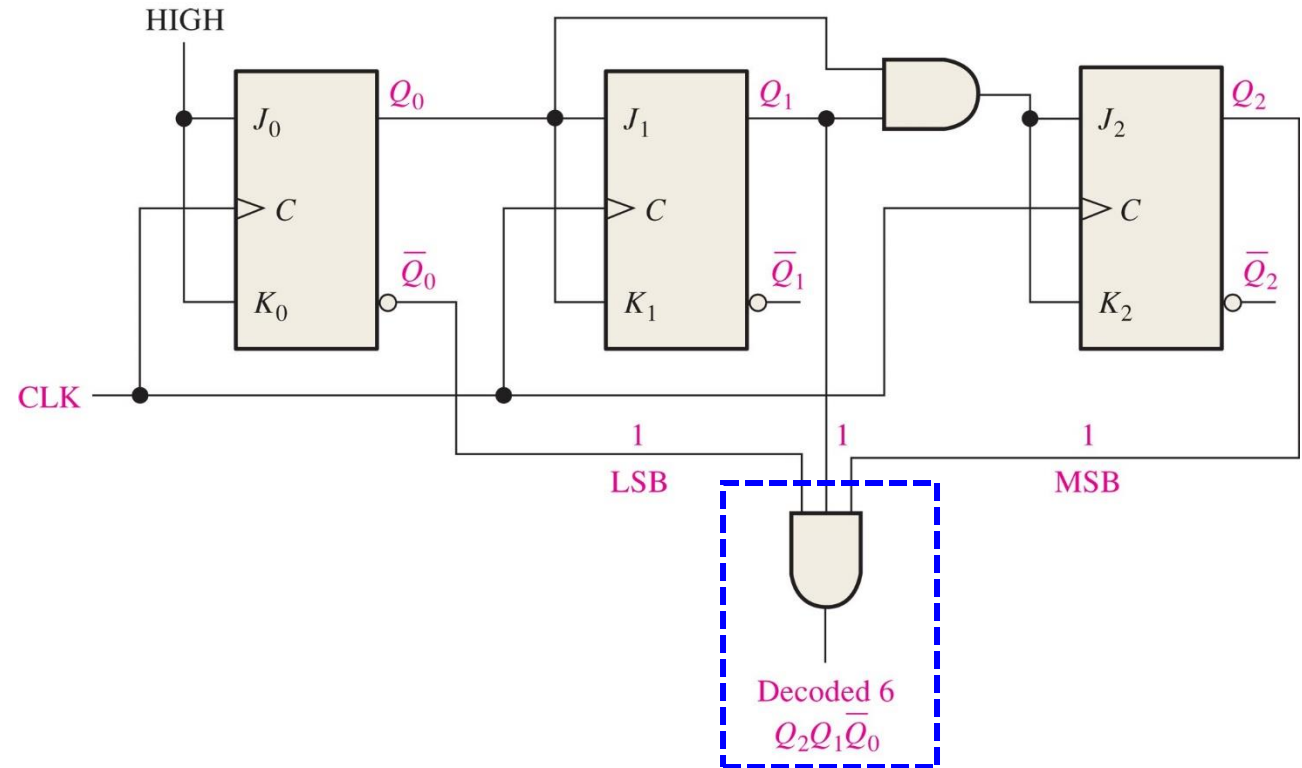
# Counter Decoding


- The decoding of a counter involves using decoders or logic gates to determine when the counter is in a certain binary state in its sequence.
- For example, when  $Q_2 = 1$ ,  $Q_1 = 1$ , and  $Q_0 = 0$ , a HIGH appears on the output of the following decoding gate, indicating that the counter is at state 6.





 
# Decoding Glitches (I)

- The glitch problem can also occur to synchronous counters because the propagation delays from the clock to the Q outputs of each flip-flop in a counter can vary slightly.





Asynchronous BCD decade counter

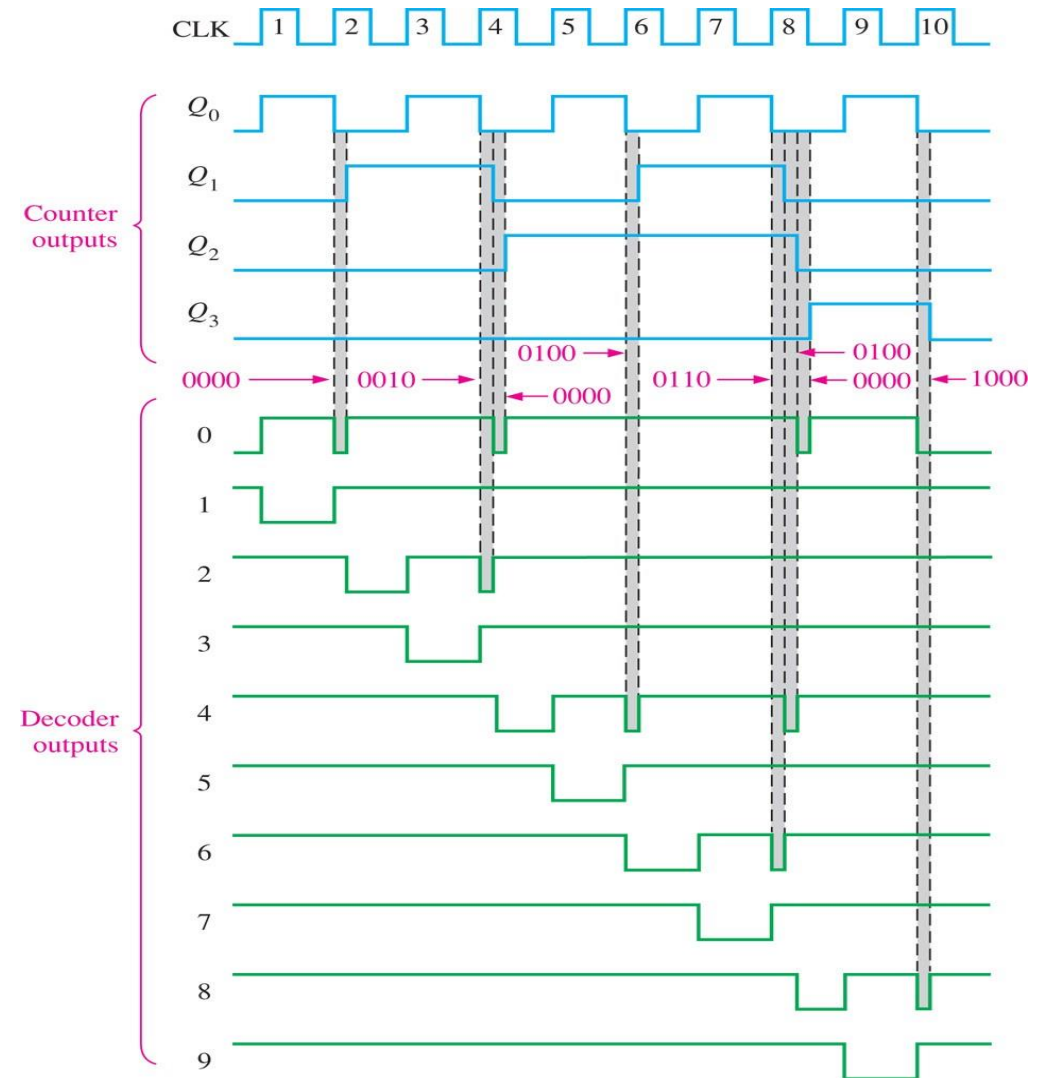
 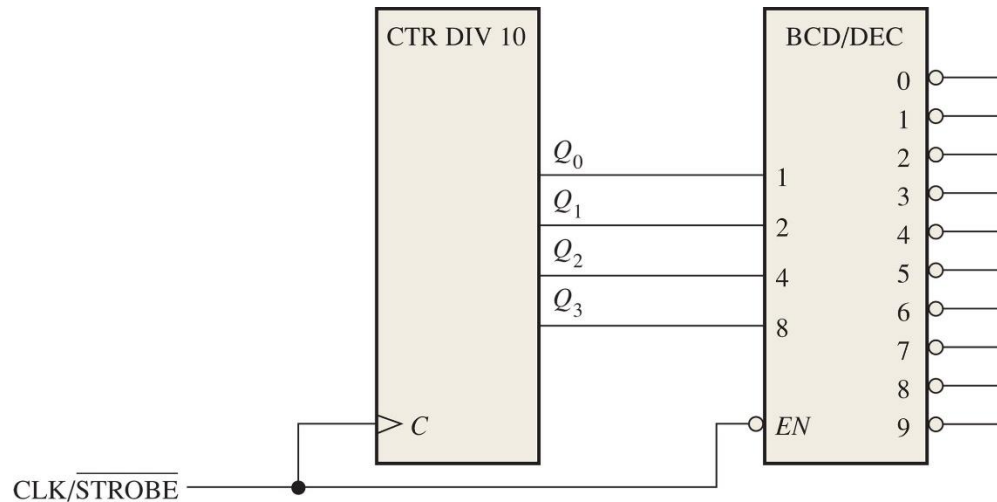
# Decoding Glitches (II)

- For an active-HIGH clock, use the LOW level of the clock to enable the decoder.




# Counter Applications



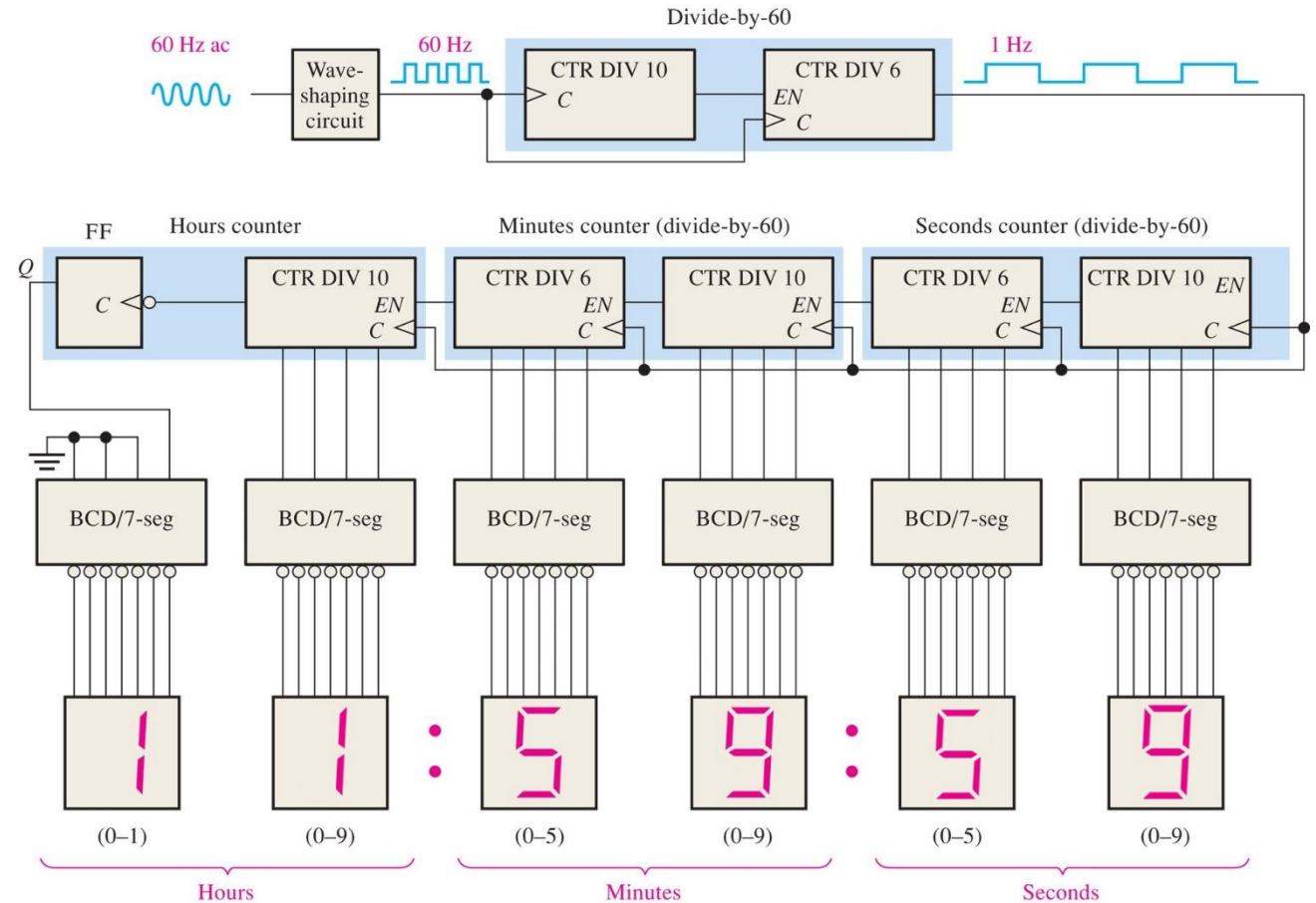
# Example: A Digital Clock

- **Input** : a 60 Hz pulse waveform generated from a 60 Hz sinusoidal ac voltage;
- **Counters for Seconds and Minutes** : count from 0 to 59 and then recycle to 0;
- **The hour counter** : a decade counter and a flip-flop to illuminate a 1 on the tens-of-hours display.




## The Second/Minute/Hour Counter

The right-most bit is the LSB

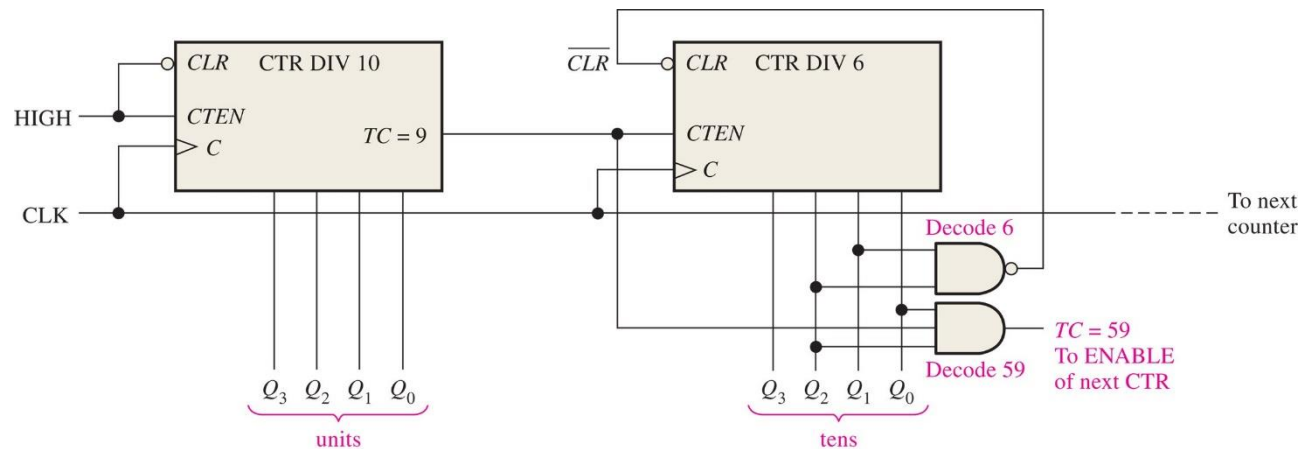



- In state 12, the G2 output is LOW (i.e. Q and Q1 are HIGH) , which activates the LOAD input of the decade counter.
- On the next clock pulse, the decade counter is preset to 0001.

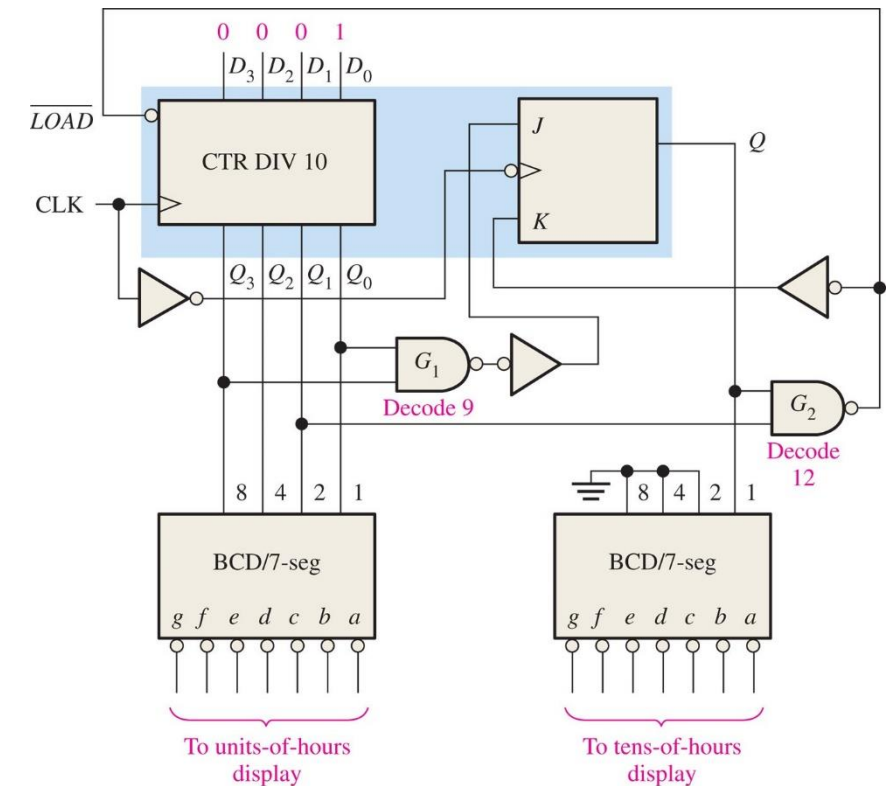- The terminal count, 59, is decoded to enable the next counter in the chain.


 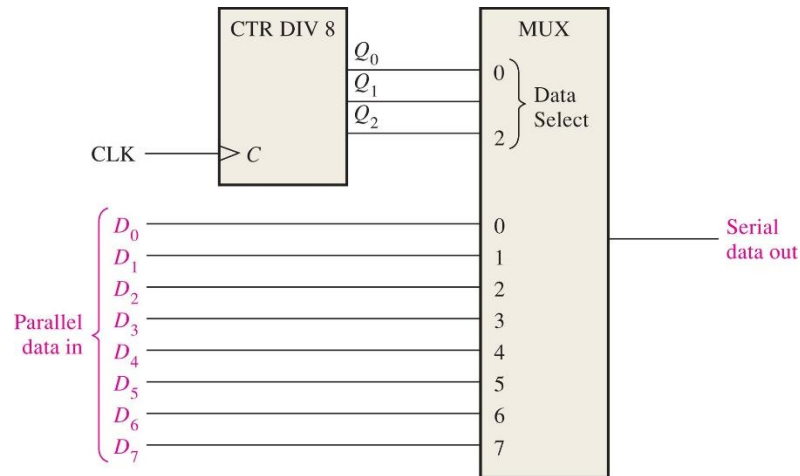
# Example: P/S Data Conversion (Multiplexing)

- The 1<sup>st</sup> byte of parallel data is applied to the multiplexer inputs.
- After 8 clock pulses the data byte has been converted to a serial format and sent out on the transmission line.












# Chapter Review

- ❑ Counters
  - ❑ Asynchronous
  - ❑ Synchronous
- ❑ Up/Down Counters
- ❑ Design of Synchronous Counters
- ❑ Cascaded Counters
- ❑ Counter Decoding



# True/False Quiz

-  Synchronous counters cannot be realized using J-K flip-flops.
-  An asynchronous counter is also known as a ripple counter.
-  A decade counter has twelve states.
-  A counter with four stages has a maximum modulus of sixteen.
-  To achieve a maximum modulus of 32, sixteen stages are required.
-  If the present state is 1000, the next state of a 4-bit up/down counter in the DOWN mode is 0111.
-  Two cascaded decade counters divide the clock frequency by 10.
-  A counter with a truncated sequence has less than its maximum number of states.
-  To achieve a modulus of 100, ten decade counters are required.