

Midterm Test

(Time allowed: 90 minutes)

March 17, 2024

NOTE: Answer ALL 8 questions. Show all intermediate steps, except Question 1 and Question 2.

1. (10 points) Are the following statements necessarily true (Y) or not (N)?

- (1) In positive logic, a HIGH level represents a binary 0.
- (2) The hexadecimal number system is a weighted system with 16 digits.
- (3) The 2's complement of the binary number 1100 is 0011.
- (4) It is possible to build an XOR gate with multiple NAND gates.
- (5) The domain of the expression $ABD + \bar{C}D$ is A, B, C and D .
- (6) In Boolean Algebra, the multiplication of two values is equivalent to the logical OR function.
- (7) The MSB represents the highest-order bit in a binary representation.
- (8) The complement of a sum of variables is equal to the product of the complements of each variable is a statement of Demorgan's theorem.
- (9) A full-adder can be realized using only 2 half-adders.
- (10) The multiplexer is a data distributor while a de-multiplexer is a data selector.

Solution:

- (1) N
- (2) Y
- (3) N
- (4) Y
- (5) Y
- (6) N
- (7) Y
- (8) Y
- (9) N
- (10) N

CONTINUED

2. (10 points) Provide your answers to the following short questions.

- (1) Convert the binary number 101101 to its hex representation;
- (2) Convert the gray code 11010010 to binary;
- (3) How many cells do a 4-variable Karnaugh map have?
- (4) If the inputs to an exclusive-NOR function is A and B , write down the logic expression using And-Or-Invert logic.
- (5) Determine the odd parity bit for the BCD number 00101001.

Solution:

- (1) $2D$;
- (2) 10011100
- (3) 16;
- (4) $AB + \bar{A}\bar{B}$;
- (5) 0.

3. (15 points) Perform each of the following calculations in the 2's complement form.

- (1) $01100101 - 11101000$;
- (2) 01101010×11110001 ;
- (3) $01100110 \div 00100010$.

Solution:

- (1) 01111101 in Figure 1;
- (2) 100111001010 in Figure 2;
- (3) 00000011 in Figure 3.

	01100101	Minuend (101)
+	00011000	2's complement of subtrahend (-24)
	01111101	Difference (125)

Figure 1: Q3-1 solution.

	1101010	Multiplicand (106)
x	0001111	2's complement of multiplier (-15)
	1101010	
	1101010	
	1101010	
	1101010	
+	1101010	
0	11000110110	Final product (1590)
1	00111001010	2's complement (-1590)

Figure 2: Q3-2 solution.

			Add 1 to quotient
	01100110	Dividend (102)	
+	11011110	2's complement of divisor (-34)	
	101000100		Add 1 to quotient
	11011110		
	100100010		Add 1 to quotient
	11011110		
	100000000		Quotient = 3 = 0011

Discard
carry
←
←
←

Figure 3: Q3-3 solution.

4. (15 points)

- (1) Convert the following expression to standard sum-of-product(SOP) forms:
 $(A + C)(BC + AC)$
- (2) Convert the following expression to standard product-of-sum(POS) forms:
 $(A + \bar{C})(A + BC)$
- (3) Convert binary 1101.11 to its decimal representation.

Solution:

(1)

$$\begin{aligned}
 & (A + C)(BC + AC) \\
 &= ABC + AC + BC + AC \\
 &= ABC + A(B + \bar{B})C + (A + \bar{A})BC \\
 &= ABC + ABC + A\bar{B}C + ABC + \bar{A}BC \\
 &= ABC + A\bar{B}C + \bar{A}BC
 \end{aligned}$$

(2)

$$\begin{aligned}
 & (A + \bar{C})(A + BC) \\
 &= (A + \bar{C})(A + B)(A + C) \\
 &= (A + \bar{C} + B\bar{B})(A + B + C\bar{C})(A + C + B\bar{B}) \\
 &= (A + \bar{C} + B)(A + \bar{C} + \bar{B})(A + B + C)(A + B + \bar{C})(A + C + B)(A + C + \bar{B}) \\
 &= (A + B + \bar{C})(A + \bar{B} + \bar{C})(A + B + C)(A + \bar{B} + C)
 \end{aligned}$$

$$(3) \quad 1101.11_2 = 1 \times 2^3 + 1 \times 2^2 + 1 \times 2^0 + 1 \times 2^{-1} + 1 \times 2^{-2} = 13.75$$

5. (12 points) For the logic circuit and the input waveforms shown in Figure. 4, respectively, answer the following questions.

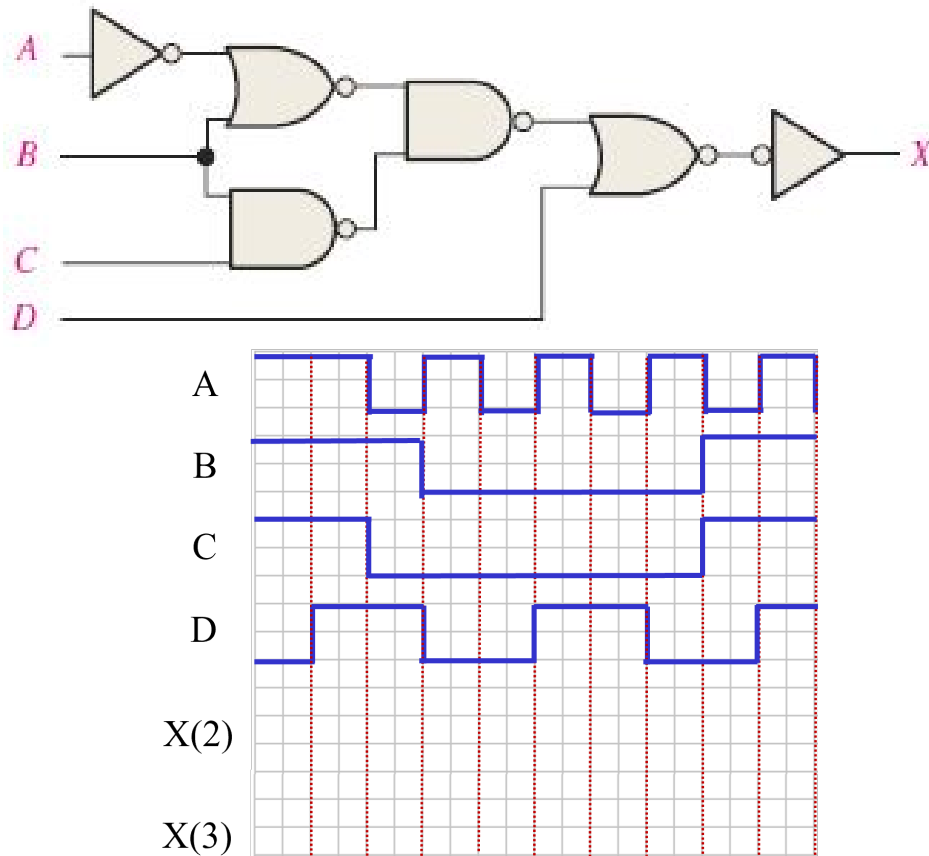


Figure 4: Combinational logic circuit and input waveforms for Q.5.

- (1) (4 points) Derive the expression of the output X and minimize it using the boolean algebra laws and rules, show the intermediate steps;
- (2) (4 points) Draw the output waveform based on the inputs.
- (3) (4 points) Assuming that the input B is shorted to ground, derive the expression of the output X and draw its waveform.

Solution:

$$\begin{aligned}
 X &= \overline{\overline{\overline{\overline{A + B}}(\overline{BC})} + D} = \overline{\overline{\overline{A + B}}(\overline{BC})} + D \\
 &= \overline{A} + B + BC + D = \overline{A} + B + D
 \end{aligned}$$

(1)

 


Figure 5: Output waveform of X for Q.5(1).

(2)

(3) $X = \bar{A} + D$

 


Figure 6: Output waveform of X for Q.5(2).

6. (15 points)

- (1) Derive the minimized SOP expression from the truth table below using K-map (5 points), and implement it using basic gates such as AND, OR, Inverter(5 points). The complementary inputs, if needed, are **NOT** directly available, i.e. $\bar{A}, \bar{B}, \bar{C}, \bar{D}$ are **NOT** available. Same for the question below.
- (2) (5 points) Implement the logic function specified in the truth table by using a 74HC151 8-input data selector/multiplexer.

A	B	C	D	X
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

Table 1: The truth table of Q.6.

 


Figure 7: The 74HC151 8-input multiplexer.

Solution:

- (1) The K-map is shown in Fig. 8.

 


Figure 8: The K-map from the truth table.

The minimized SOP form is:

$$X = ACD + A\bar{B} + \bar{B}C + \bar{A}\bar{B}\bar{C}\bar{D}$$

The logic circuit implemented is shown in Fig. 9.

 


Figure 9: The logic circuit implementation.

(2) The logic function implemented by a 74HC151 is shown in Figure 10.

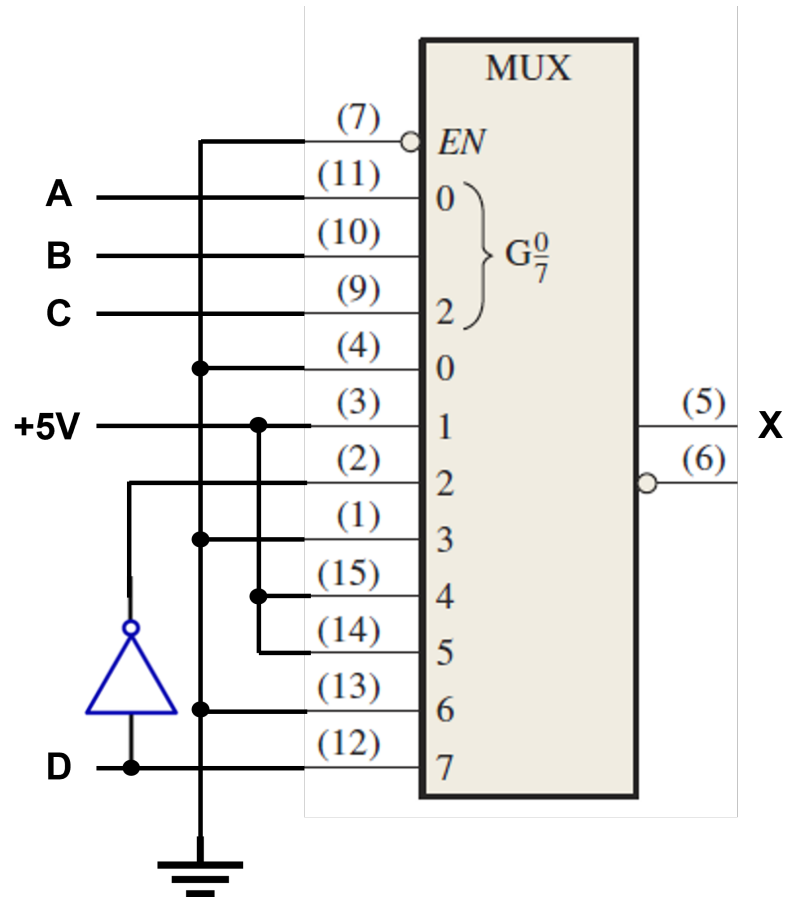


Figure 10: The 74HC151 implemented logic function.

7. (13 points)

- (1) (2 points) For the parallel adder in Fig. 11, determine the complete sum by analyzing the operation of the circuit.

 


Figure 11: The 4-bit ripple carry adder.

- (2) Assume $A = A_1A_0$ and $B = B_1B_0$, and C_0 denotes the initial carry input. If implement the 2-bit addition using the look-ahead carry adder: Firstly, please give the expressions of the carry generation (G_1 and G_0 , respectively), carry propagation (P_1 and P_0 , respectively) and the carry output (C_1 and C_2 , respectively) for each stage (6 points), and draw the logic diagrams inside the block 1 and block 2 of Fig. 12 to show the inside logic circuits using necessary logic gates (5 points).

 


Figure 12: Carry prediction circuits of the 2-bit Look-ahead carry adder.

Solution:

- (1) The complete sum is $\Sigma = \Sigma_5\Sigma_4\Sigma_3\Sigma_2\Sigma_1 = 10001$.

 


Figure 13: The addition of two 4-bit numbers using ripple carry adder.

- (2) The equations and the logic diagrams are shown below (Note: Both “OR” and “XOR” gates can be used to calculate the carry propagation.):

$$G_0 = A_0 B_0$$

$$P_0 = A_0 + B_0$$

$$C_1 = G_0 + P_0 C_0$$

$$G_1 = A_1 B_1$$

$$P_1 = A_1 + B_1$$

$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 (G_0 + P_0 C_0) = G_1 + P_1 G_0 + P_1 P_0 C_0$$

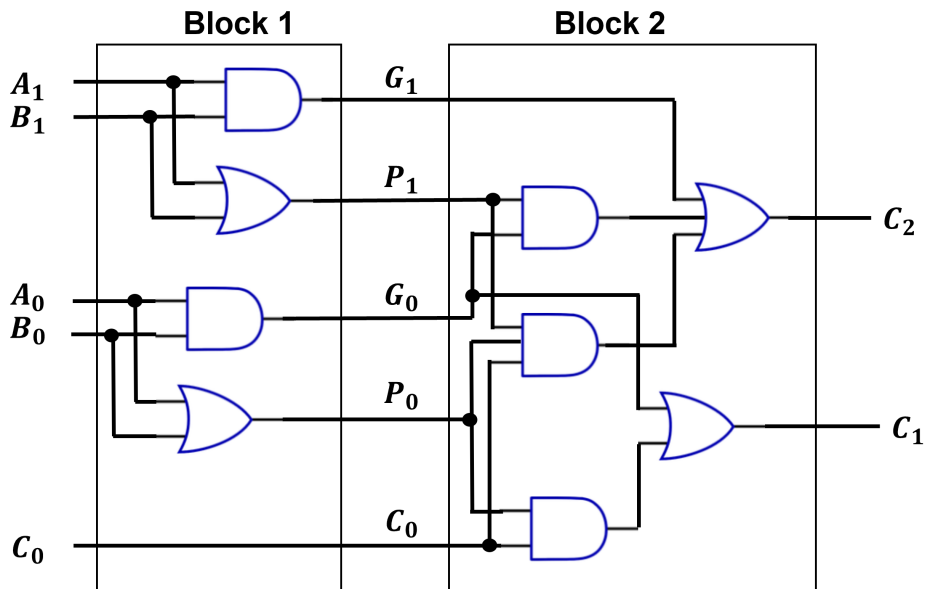


Figure 14: Carry prediction circuits of the 2-bit Look-ahead carry adder.

8. (10 points) Develop a logic circuit with **BCD** inputs that will only produce a 1 output when exactly 2 input variables are 1s.

(1) Please develop the truth table for the above circuit.

(2) Please use K-map to derive the minimized SOP expression for the circuit.

Solution:

(1) The truth table for the circuit is:

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>X</i>
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

(2) $X = AB + AC + AD + B\bar{C}\bar{D} + B\bar{C}D + \bar{B}CD$

 


Figure 15: Solution for Q.8.