

ECE 2050 Digital Logic and Systems

Chapter 11:

Memory & Logic Arrays

Instructor: Tinghuan CHEN, Ph.D.




Chapter Review

- ☐ Counters
 - ☐ Asynchronous
 - ☐ Synchronous
- ☐ Up/Down Counters
- ☐ Design of Synchronous Counters
- ☐ Cascaded Counters
- ☐ Counter Decoding

Memory



Memory Arrays

 - Efficiently store large amounts of data
- M -bit data value read/written at each unique N -bit address
- 3 common types:
 - Dynamic random access memory (DRAM)
 - Static random access memory (SRAM)
 - Read only memory (ROM)



Memory Arrays

  
- 2-dimensional array of bit cells
- Each bit cell stores one bit
- N address bits and M data bits:
 - 2^N rows and M columns
 - **Depth:** number of rows (number of words)
 - **Width:** number of columns (size of word)
 - **Array size:** depth \times width = $2^N \times M$



Address	Data			
11	0	1	0	↑ depth ↓
10	1	0	0	
01	1	1	0	
00	0	1	1	
	↔ width ↔			

Memory Array Example

 - $2^2 \times 3\text{-bit}$ array
- Number of words: 4
- Word size: 3-bits
- For example, the 3-bit word stored at address 10 is 100




Address	Data
11	0 1 0
10	1 0 0
01	1 1 0
00	0 1 1



depth

width

Memory Arrays

 


Memory Array Bit Cells

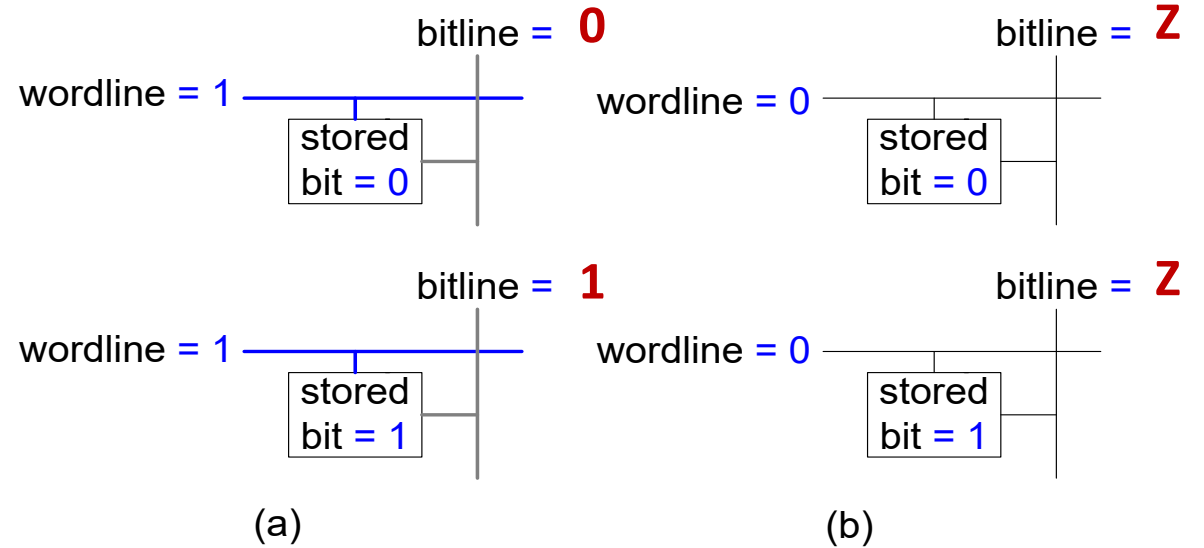 

Memory Array

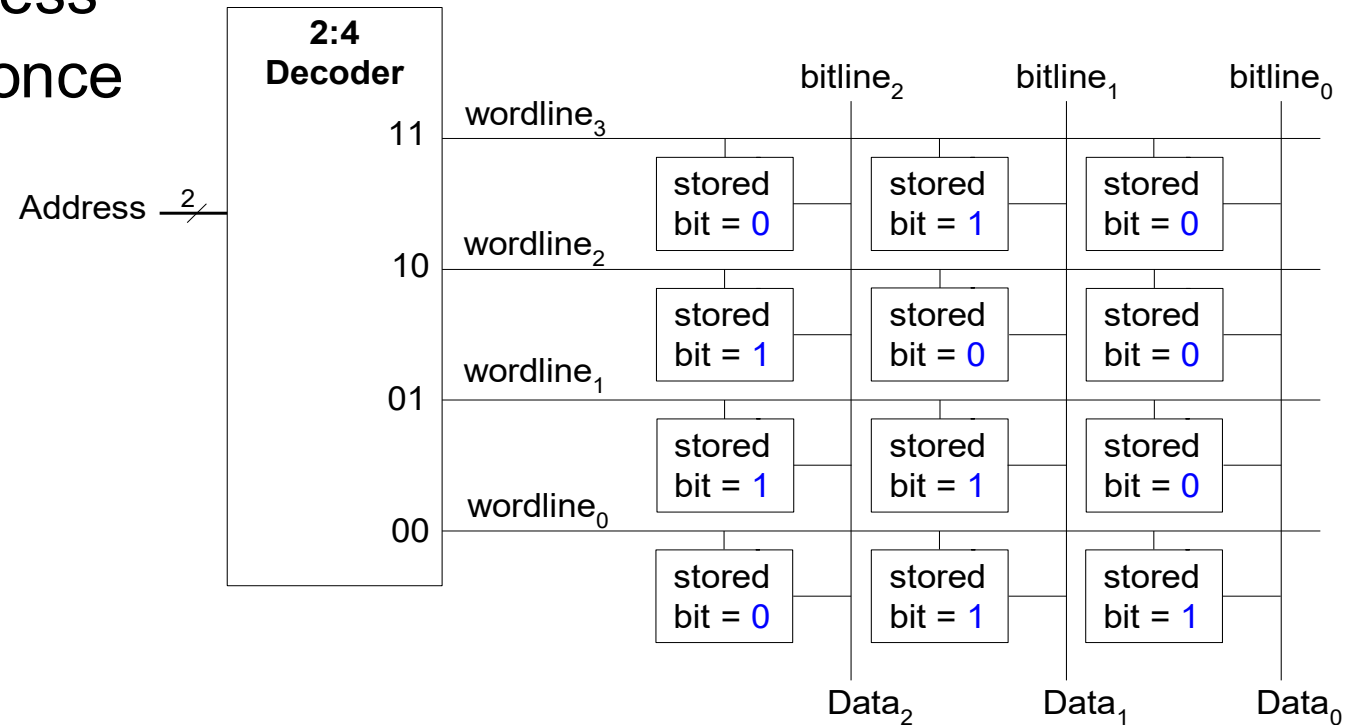- **Wordline:**
 - like an enable
 - single row in memory array read/written
 - corresponds to unique address
 - only one wordline **HIGH** at once



Types of Memory

- Random access memory (RAM): **volatile**
- Read only memory (ROM): **nonvolatile**

RAM: Random Access Memory

- **Volatile:** loses its data when power off
- Read and written quickly
- Main memory in your computer is RAM (DRAM)
- Historically called **random access** memory because any data word accessed as easily as any other (in contrast to sequential access memories such as a tape recorder)

ROM: Read Only Memory

- **Nonvolatile:** retains data when power off
- Read quickly, but writing is impossible or slow
- Flash memory in cameras, thumb drives, and digital cameras are all ROMs
- Historically called **read only** memory because ROMs were written at time of fabrication or by burning fuses. Once a ROM was configured, it could not be written again. This is no longer the case for Flash memory and other types of ROMs.

RAM

Types of RAM

- **DRAM** (Dynamic random access memory)
- **SRAM** (Static random access memory)
- Differ in how they store data:
 - DRAM uses a capacitor
 - SRAM uses cross-coupled inverters



Robert Dennard, 1932 -

- Invented DRAM in 1966 at IBM
- Others were skeptical that the idea would work
- By the mid-1970's DRAM in virtually all computers





DRAM

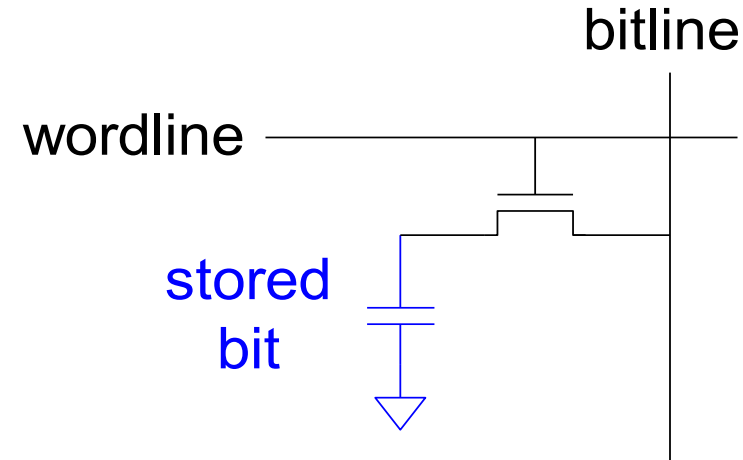
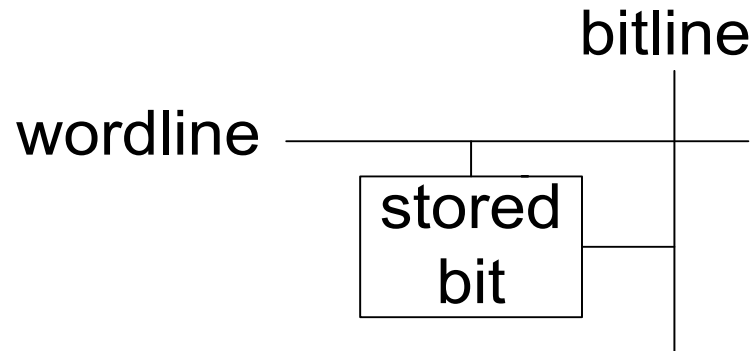
- Data bits stored on **capacitor**
- *Dynamic* because the value needs to be **refreshed** (rewritten) periodically and after read:
 - Charge leakage from the capacitor degrades the value
 - Reading destroys the stored value




DRAM

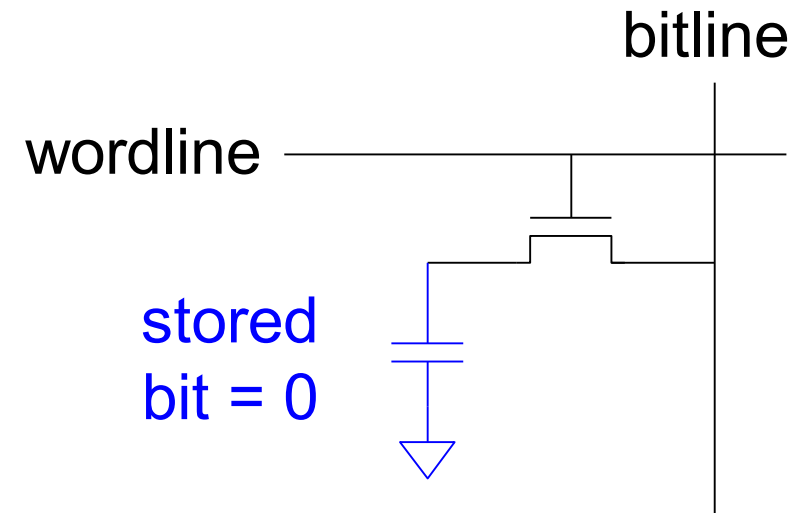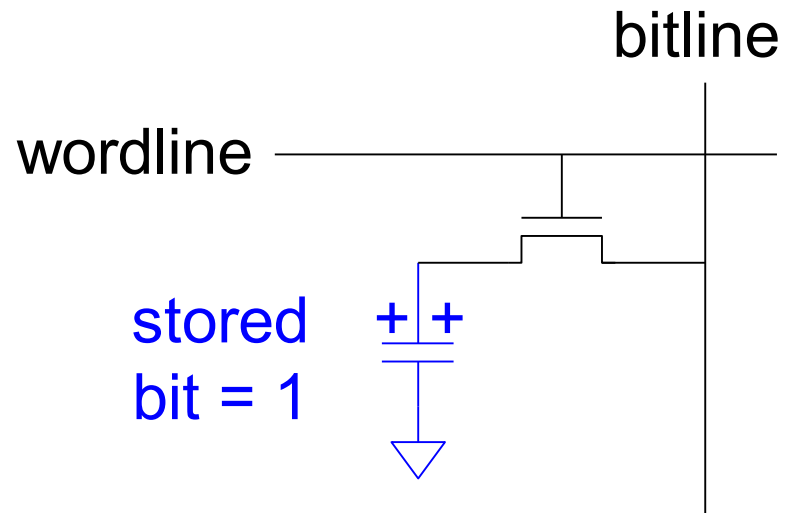


SRAM

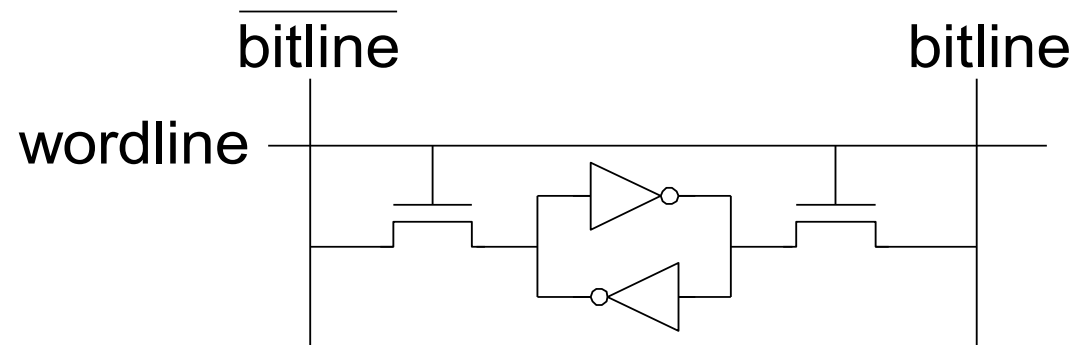 


Memory Arrays Review

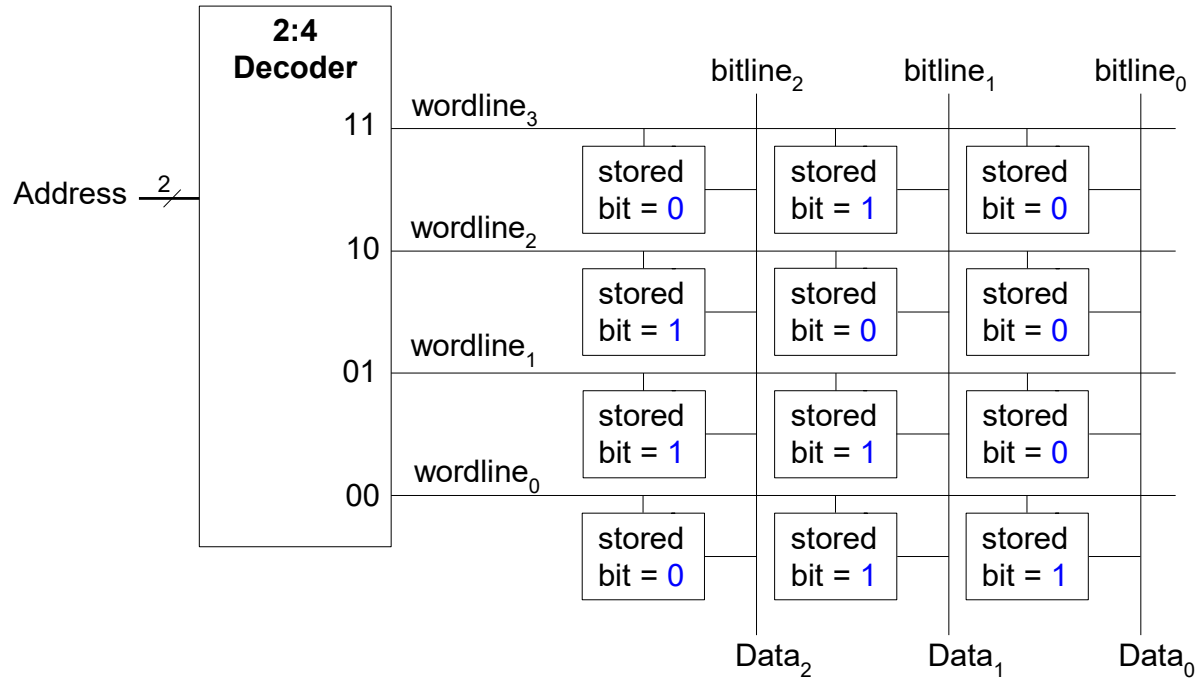

DRAM bit cell:


 


SRAM bit cell:

 


ROM

ROM: Dot Notation

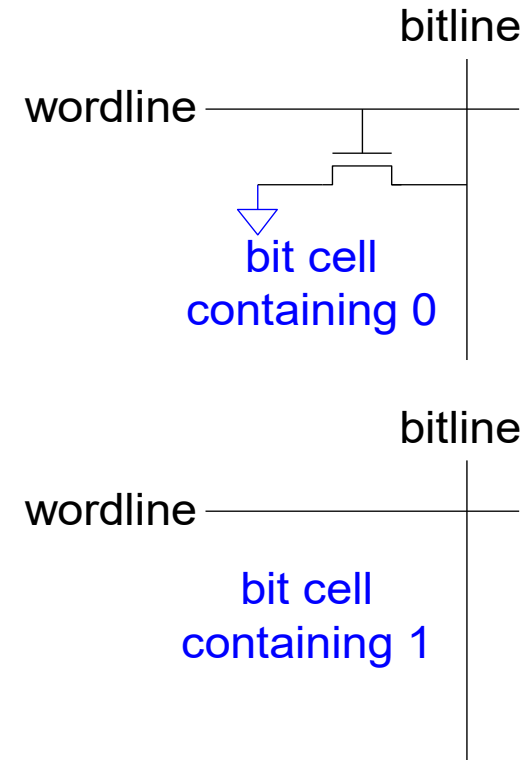 

ROM Storage

 


Address	Data			<div>↑ depth ↓</div>
11	0	1	0	
10	1	0	0	
01	1	1	0	
00	0	1	1	
<div>← width →</div>				

Fujio Masuoka, 1944 -

- Developed memories and high speed circuits at Toshiba, 1971-1994
- Invented Flash memory as an unauthorized project pursued during nights and weekends in the late 1970's
- The process of erasing the memory reminded him of the flash of a camera
- Toshiba slow to commercialize the idea; Intel was first to market in 1988
- Flash has grown into a \$25 billion per year market



ROM Logic

 


$$Data_2 = A_1 \oplus A_0$$

$$Data_1 = \bar{A}_1 + A_0$$


$$Data_0 = \bar{A}_1 \bar{A}_0$$

 Example: Logic with ROMs

- Implement the following logic functions using a $2^2 \times 3$ -bit ROM:
 - $X = AB$
 - $Y = A + B$
 - $Z = A \bar{B}$



Logic with Any Memory Array

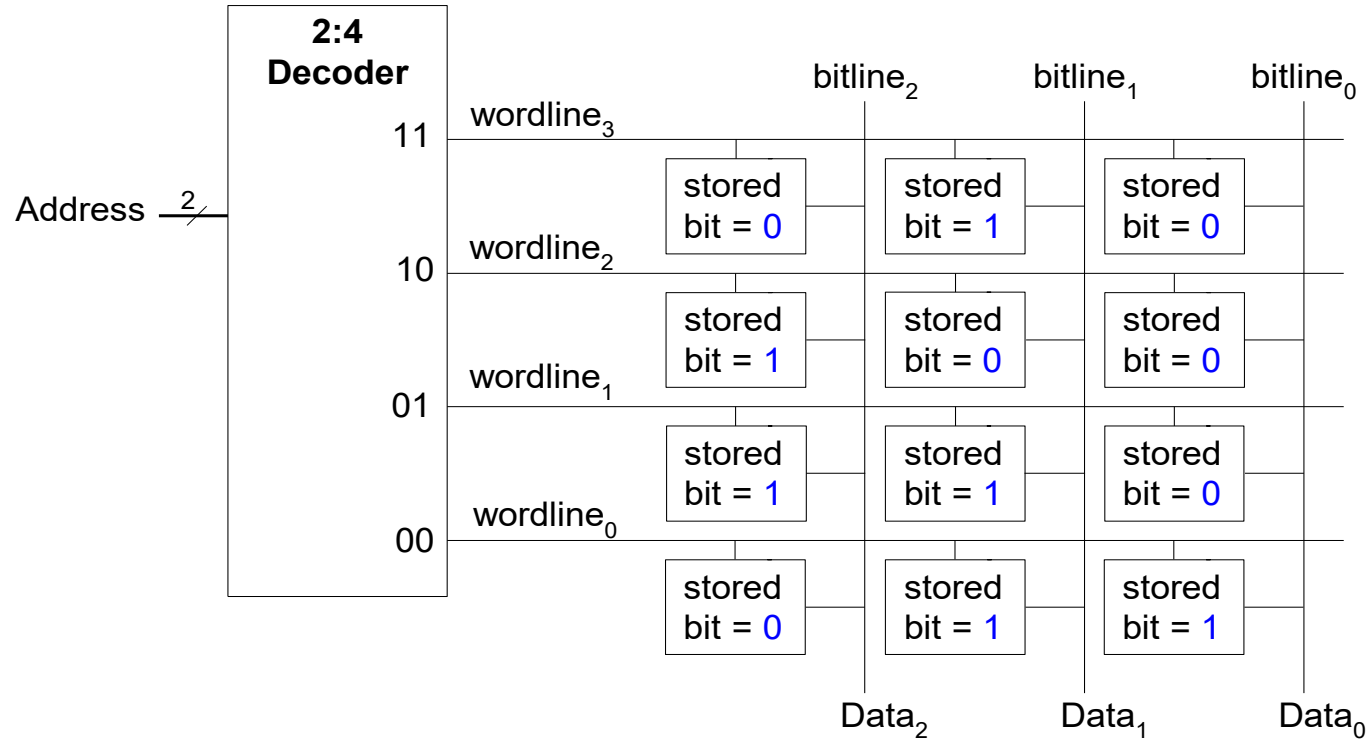

$Data_2 =$

$Data_1 =$

$Data_0 =$


Logic with Memory Arrays

- Implement the following logic functions using a $2^2 \times 3$ -bit memory array:

– $X = AB$

– $Y = A + B$


– $Z = A \overline{B}$

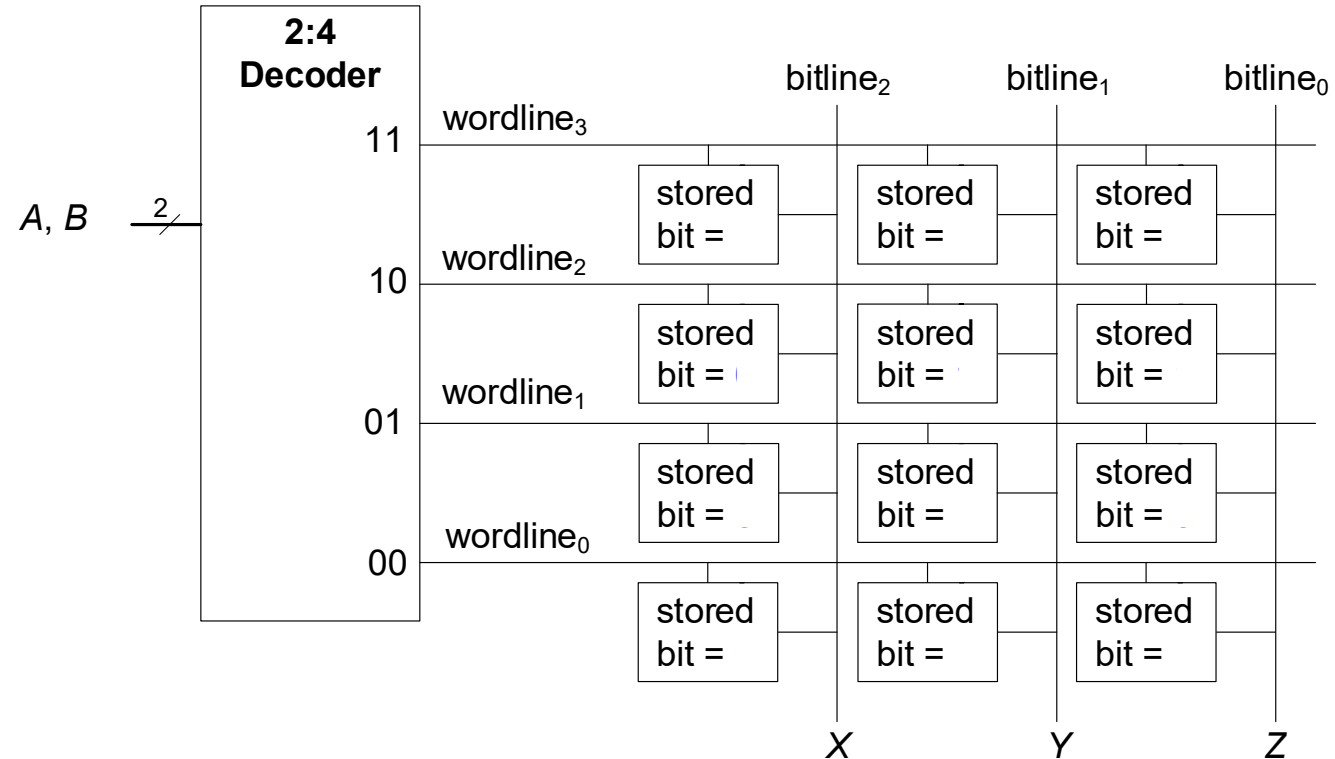

Logic with Memory Arrays

- Called **lookup tables (LUTs)**: look up output at each input combination (address)

Truth Table		
A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1


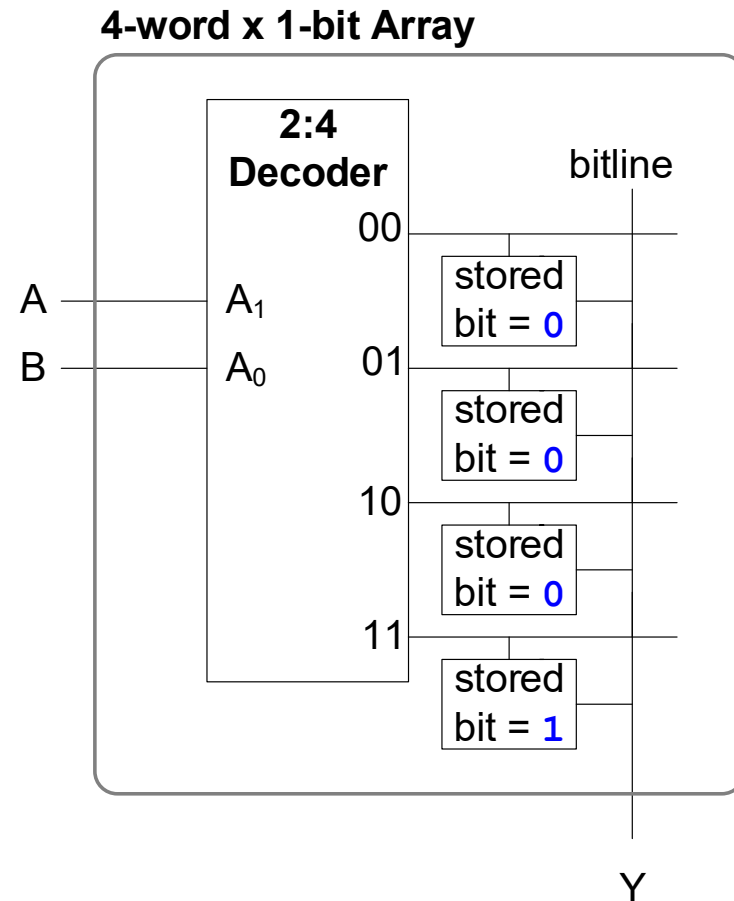


Logic Arrays: PLAs & FPGAs

- **PLAs** (Programmable logic arrays)
 - AND array followed by OR array
 - Combinational logic only
 - Fixed internal connections
- **FPGAs** (Field programmable gate arrays)
 - Array of Logic Elements (LEs)
 - Combinational and sequential logic
 - Programmable internal connections



PLAs: Programmable Logic Arrays

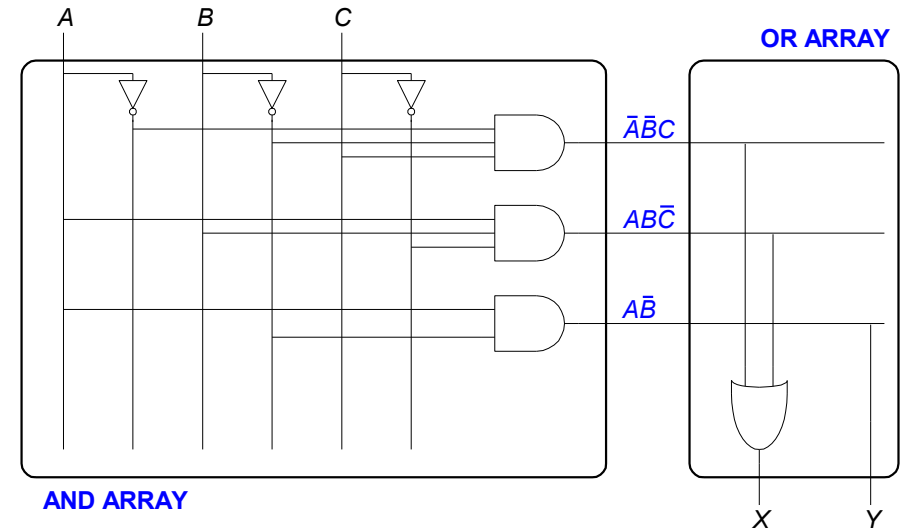 - $X = \bar{A}\bar{B}C + AB\bar{C}$
- $Y = A\bar{B}$




PLAs: Dot Notation

  - $X = \bar{A}\bar{B}C + AB\bar{C}$
- $Y = A\bar{B}$



FPGAs: Field Programmable Gate Arrays

 - Composed of:
 - **LEs** (Logic elements): perform logic
 - **IOEs** (Input/output elements): interface with outside world
 - **Programmable interconnection:** connect LEs and IOEs
 - Some FPGAs include other building blocks such as multipliers and RAMs




General FPGA Layout

LE: Logic Element

- Composed of:
 - **LUTs** (lookup tables): perform combinational logic
 - **Flip-flops**: perform sequential logic
 - **Multiplexers**: connect LUTs and flip-flops

Altera Cyclone IV LE

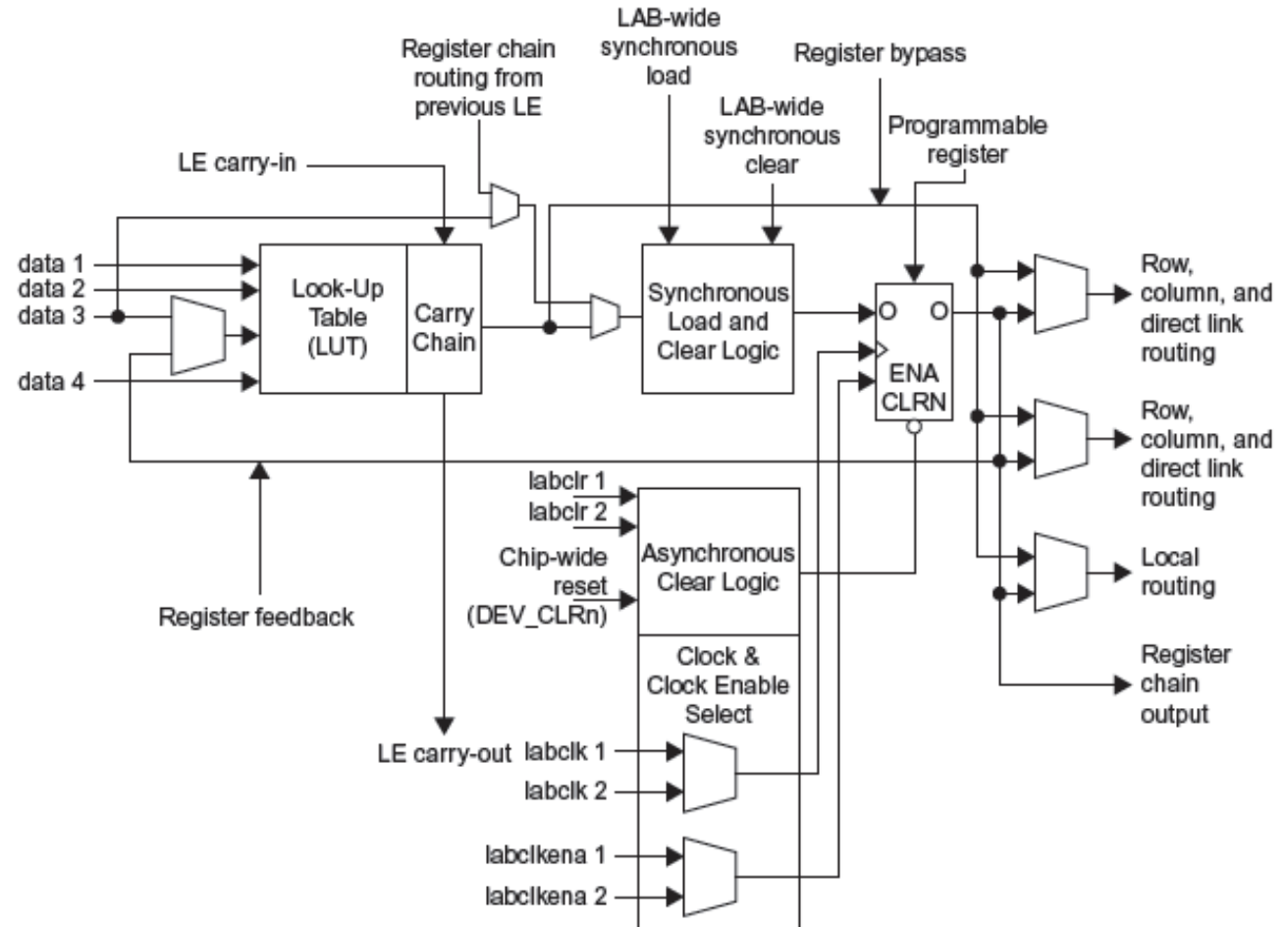- The Altera Cyclone IV LE has:
 - 1 four-input **LUT**
 - 1 **registered output**
 - 1 **combinational output**



- *From Cyclone IV datasheet*

FPGA Design Flow

- Using a CAD tool (such as Altera's Quartus II)
 - **Enter the design** using schematic entry or an HDL
 - **Simulate** the design
 - **Synthesize** design and map it onto FPGA
 - **Download the configuration** onto the FPGA
 - **Test** the design