



香港中文大學(深圳)
The Chinese University of Hong Kong, Shenzhen

ECE2050 Digital Logic and Systems

Tutorial 7: Sequential Logic Design

Yiyang Li

Contact: 222010039@link.cuhk.edu.cn


Office Hour: 11:00-12:00 Tuesday, Zhixin 107

Review: S-R Latch

■ Bistable Storage device (SET & RESET)

✓ S-R Latch

➤ Two cross-coupled NAND (NOR) gates

 

Active-LOW input \bar{S} - \bar{R} latch

➤ Truth Table

TABLE 7-1

Truth table for an active-LOW input \bar{S} - \bar{R} latch.

| Inputs | | Outputs | | Comments |
|-----------|-----------|---------|-----------|--|
| \bar{S} | \bar{R} | Q | \bar{Q} | |
| 1 | 1 | NC | NC | No change. Latch remains in present state. |
| 0 | 1 | 1 | 0 | Latch SET. |
| 1 | 0 | 0 | 1 | Latch RESET. |
| 0 | 0 | 1 | 1 | Invalid condition |

$\left\{ \begin{array}{l} Q \text{ is HIGH, the latch is in the SET state} \\ Q \text{ is LOW, the latch is in the RESET state} \end{array} \right.$




Review: S-R Latch

■ Bistable Storage device (SET & RESET)

✓ S-R Latch (**Application**)

➤ Latch as a Contact-Bounce Eliminator

 


Review: The Gated S-R Latch


■ Bistable Storage device (SET & RESET)

✓ The Gated S-R Latch

➤ S-R latch + EN (input)

 

(a) Logic diagram

 

(b) Logic symbol

➤ Input-Output Relationship

- When enabled, the NAND gates outputs are \bar{S} and \bar{R} , respectively.
- The output is similar to S-R latches




Review: The Gated D Latch

■ Bistable Storage device (**SET & RESET**)


✓ The Gated D Latch

➤ D (Input) + EN (Input)

➤ Input-Output Relationship

 

(a) Logic diagram

 


(b) Logic symbol

- When D and EN are HIGH, Q is HIGH
- When D is LOW and EN is HIGH, Q is LOW



 Question 1

■ Q1: Determine the output of a **gated D latch** for the inputs in the figure below.



Review: Flip-Flops

■ Synchronous Bistable Devices

- ✓ Output changes state at a leading or trailing edge on the **triggering** input called **CLK**
- ✓ Two types of edge-triggered flip-flops

➤ The D Flip-Flop

 


TABLE 7-2

Truth table for a positive edge-triggered D flip-flop.

| Inputs | | Outputs | | Comments |
|--------|-----|---------|-----------|----------|
| D | CLK | Q | \bar{Q} | |
| 0 | ↑ | 0 | 1 | RESET |
| 1 | ↑ | 1 | 0 | SET |

↑ = clock transition LOW to HIGH

➤ The J-K Flip-Flop

 


TABLE 7-3

Truth table for a positive edge-triggered J-K flip-flop.

| Inputs | | | Outputs | | Comments |
|--------|---|-----|-------------|-------------|-----------|
| J | K | CLK | Q | \bar{Q} | |
| 0 | 0 | ↑ | Q_0 | \bar{Q}_0 | No change |
| 0 | 1 | ↑ | 0 | 1 | RESET |
| 1 | 0 | ↑ | 1 | 0 | SET |
| 1 | 1 | ↑ | \bar{Q}_0 | Q_0 | Toggle |


↑ = clock transition LOW to HIGH

Q_0 = output level prior to clock transition



Question 2

- For a negative edge-triggered J-K flip-flop with the inputs in Figure below, develop the Q output waveform relative to the clock. Assume that Q is initially LOW.

 

Question 4

■ What is the difference between a latch and a flip flop?

- Latch is a **level-sensitive** device (outputs can change as soon as the inputs changes), No CLK.
- Flip-Flop is an **edge-sensitive** device (only changes state when a CLK signal goes from high to low or low to high).
- Latch cannot filter **glitches** (when the enable signal is valid, the output state may change multiple times with the input). This is extremely dangerous to the next-level circuit, so the flip-flop can be used


■ What are the applications of flip flop?

- Counters
- Frequency dividers
- ...



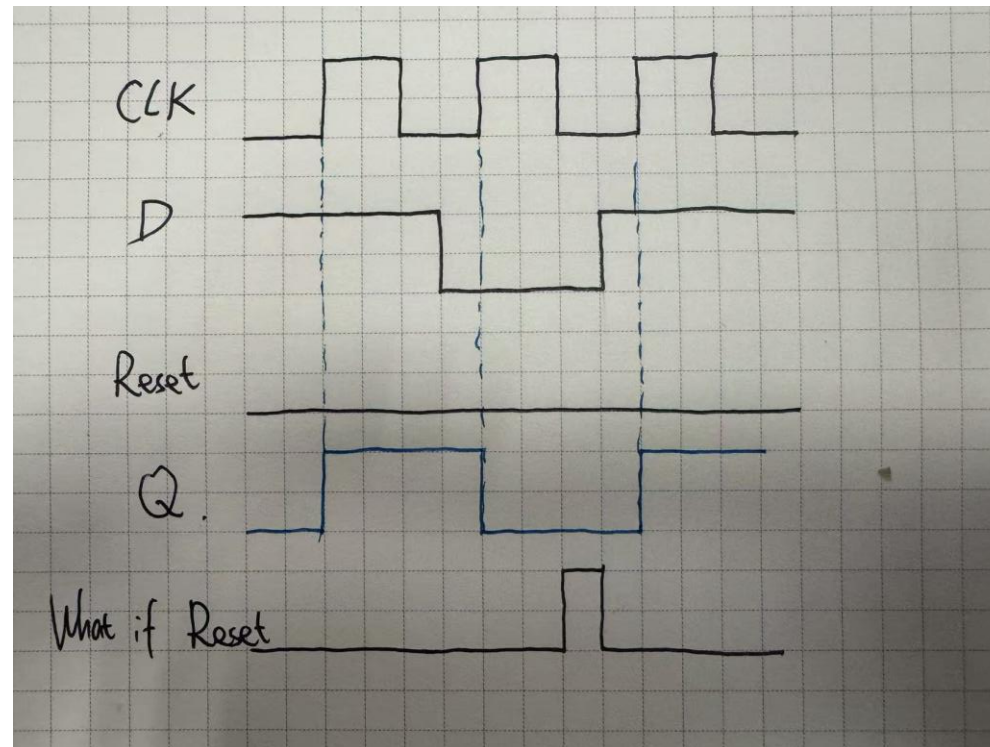Question 5

- For a positive edge-triggered D Flip-Flop with the inputs in Figure below, develop the Q output waveform relative to the clock. Assume that Q is initially LOW.





香港中文大學(深圳)
The Chinese University of Hong Kong, Shenzhen

Thank You!