


# ECE2050 Digital Logic and Systems

## Project: Bidirectional Shift Registers


### ■ Objectives and Aims:

- Get familiar with the hardware programming language VHDL
- Study the use of different architectural design methods
- Study the use of combinational and sequential logics

 
### ■ Exercise: In this project, you need to implement a **Bidirectional Shift Register**, which is composed of 4 D-Flip-Flops (D-FF) and some basic logic gates as follows:



 - $RIGHT/LEFT$  controls data bits inside the register to be shifted left or right.
- When  $RIGHT/LEFT$  is HIGH,  $G_1 \sim G_4$  are enabled, and the state of the  $Q$  output of each flip-flop is passed through to the  $D$  input of the **following** flip-flop.



 - When  $\overline{\text{RIGHT/LEFT}}$  is LOW,  $G_5 \sim G_8$  are enabled, and the Q output of each flip-flop is passed through to the D input of the **preceding** flip-flop.



## ■ Requirements:

- Implement a Bidirectional Shift Register, which is composed of 4 D-Flip-Flops (D-FF) using the **structural design (port map)** and some basic logic gates.
  - That is, implement the D-Flip-Flop first, and then use D-Flip-Flop and basic logic gates to implement the Bidirectional Shift Register.
  - Write down a testbench to verify the Bidirectional Shift Register function (timing diagram).
  - You can use Verilog HDL if you are familiar with it.
- Submission Rule:

- Submit your (1) source code(s) (.vhd), (2) testbench (.vhd), and (3) the behavior simulation result (a screen shot) to BB.
- If using Verilog HDL, submit your (1) source code(s) (.v), (2) testbench (.v), and (3) the behavior simulation result (a screen shot) to BB.
- Deadline: May 5, 2025.