

Midterm Test

(Time allowed: 90 minutes)

March 19, 2023

NOTE: Answer ALL 8 questions. Show all intermediate steps, except Question 1 and Question 2.

1. (10 points) Are the following statements necessarily true (Y) or not (N)?

- (1) An XNOR gate output is LOW if both its inputs is HIGH.
- (2) Minimization with a K-map may result in multiple possible solutions.
- (3) Decoders are logic circuits with many outputs and inputs that convert coded inputs into coded outputs.
- (4) It is possible to build an AND gate with multiple NOR gates.
- (5) The dual symbol for a NAND gate is a negative-OR symbol.
- (6) In Boolean Algebra, the addition of two values is equivalent to the logical OR function.
- (7) The right-most bit in a signed binary number is the sign bit.
- (8) Fan-out is the minimum number of similar gates that a given gate can drive.
- (9) When a Boolean variable is multiplied by its complement, the result is 0.
- (10) A parity generator can be implemented using exclusive-OR gates.

Solution:

- (1) N
- (2) Y
- (3) N
- (4) Y
- (5) Y
- (6) Y
- (7) N
- (8) N
- (9) Y
- (10) Y

2. (10 points) Provide your answers to the following short questions.

- (1) For a periodic digital waveform with $20ms$ period and $5ms$ pulse width, write down its frequency and duty cycle;
- (2) Determine the even parity bit for the BCD number 00010100;
- (3) Subtract 173_{16} from BCD_{16} , write down the result;
- (4) Convert binary 101101 to Gray code;
- (5) A ternary numeral system (also called base 3 or trinary) has three as its base. Analogous to a bit, a ternary digit is a trit (trinary digit). Ternary most often refers to a system in which the three digits are all non-negative numbers; specifically 0, 1, and 2. Convert the fractional ternary number 10.2 to decimal (round to the nearest hundredth).

Solution:

- (1) 50Hz, 25%;
- (2) 0;
- (3) $A5A_{16}$;
- (4) 111011;
- (5) 3.67.

3. (15 points) Perform each of the following calculations of the signed numbers. Show your work.

- (1) $00001001 - 00000010$;
- (2) 01010010×11111110 ;
- (3) $01001011 \div 00011001$.

Solution:

- (1) 00000111 in Figure 1;
- (2) 101011100 in Figure 2;
- (3) 00000011 in Figure 3.

00001001	Minuend (+9)
+ 11111110	2's complement of subtrahend (-2)
100000111	Difference (+7)

Discard carry

Figure 1: Q3-1 solution.

01010010	
X 00000010	
00000000	
+ 01010010	
010100100	
101011100	2's complement

Figure 2: Q3-2 solution.

00011001	2's complement	11100111
	→	

01001011	
+ 11100111	Add 1 to quotient
00110010	
+ 11100111	Add 1 to quotient
00111001	
+ 11100111	Add 1 to quotient
00000000	Quotient=3=0011

Figure 3: Q3-3 solution.

4. (10 points) For the logic circuit and the input waveforms shown in Figure. 4, respectively, answer the following questions.

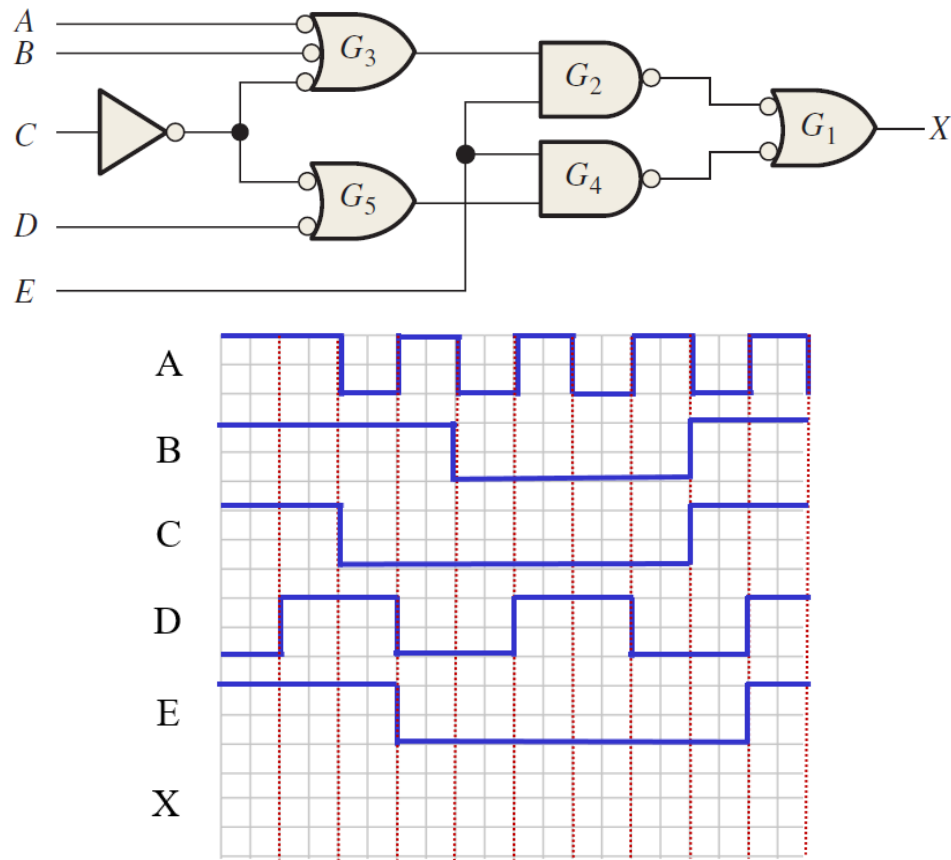


Figure 4: Combinational logic circuit and input waveform for Q.4.

- (1) (5 points) Derive the expression of the output X and draw its waveform;
- (2) (5 points) Assuming that the output of gate G_3 is open, derive the expression of the output X and draw its waveform.

Solution:

(1) $X = \bar{A}E + \bar{B}E + CE + \bar{D}E$

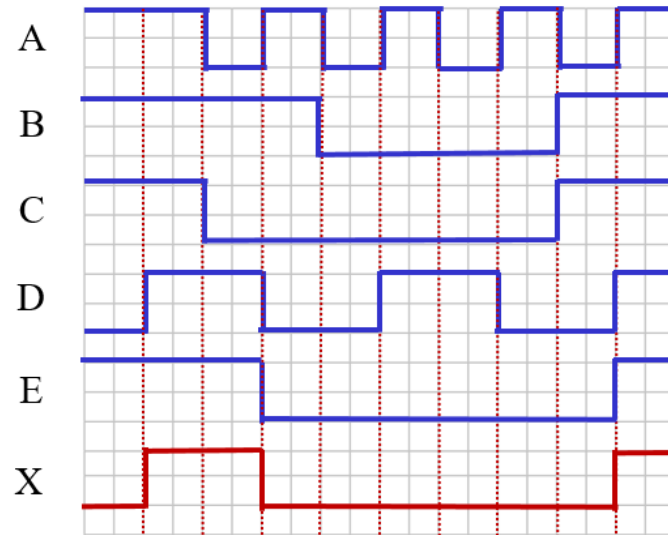


Figure 5: Output waveform of X for Q.4(1).

(2) $X = E$

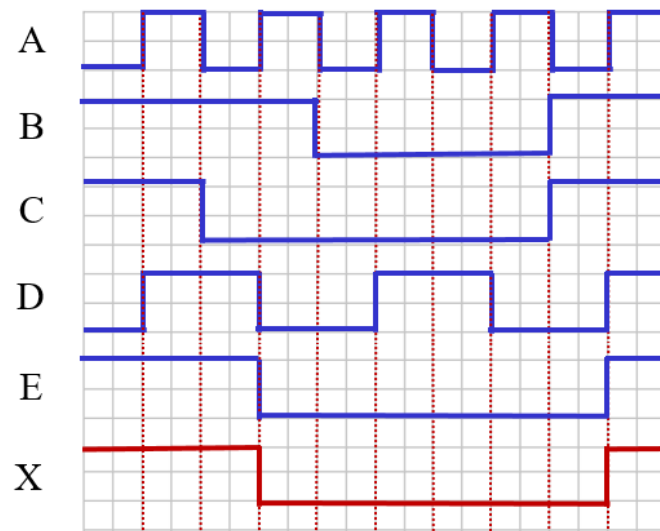


Figure 6: Output waveform of X for Q.4(2).

5. (20 points) A circuit that compares two 2-bit numbers, $A = \{A_1, A_0\}$ and $B = \{B_1, B_0\}$, and produces the output $C = \{C_1, C_0\}$ as follows:

- C equals to the lowest input (for example if $A = 11$ and $B = 10$, then $C = 10$);
- C is a don't care if $A = B$.

- (1) (5 points) Write down the truth table;
- (2) (5 points) Use Karnaugh Map to simplify the Boolean expression of the outputs C_1 and C_0 , show your work step by step;
- (3) (5 points) Sketch the C_1 logic diagram of the circuit, using **NAND** gates only (You **CANNOT** assume that complementary inputs are directly available, i.e. $\bar{A}_1, \bar{A}_0, \bar{B}_1, \bar{B}_0$ are NOT available);
- (4) (5 points) Given the input waveforms as shown in Figure 7, draw the output C_1 waveform for your design circuit in (3).

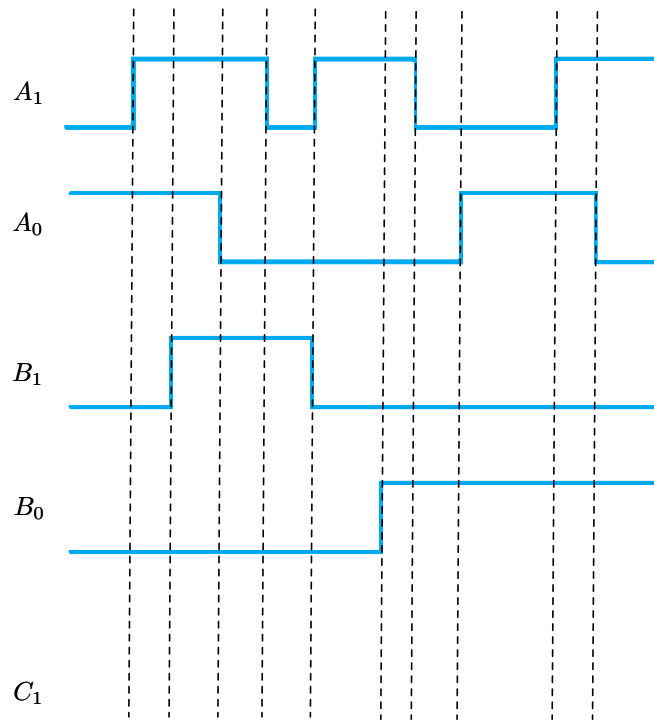


Figure 7: The input waveforms for Q.5.

Solution:

- (1) The solution is shown in Table 1.
- (2) The Karnaugh Map is shown in Figure 8.

$$C_1 = \bar{A}_1 \bar{A}_0 \bar{B}_1 \bar{B}_0 + \bar{A}_1 A_0 \bar{B}_1 B_0 + A_1 B_1;$$

$$C_0 = \bar{A}_1 \bar{A}_0 \bar{B}_1 \bar{B}_0 + A_1 \bar{A}_0 B_1 \bar{B}_0 + A_0 B_0 + \bar{A}_1 A_0 B_1 + A_1 \bar{B}_1 B_0.$$
- (3) The C_1 logic diagram of the circuit is shown in Figure 9.
- (4) The output C_1 waveform is shown in in Figure 10.

A_1	A_0	B_1	B_0	C_1	C_0
0	0	0	0	X	X
0	0	0	1	0	0
0	0	1	0	0	0
0	0	1	1	0	0
0	1	0	0	0	0
0	1	0	1	X	X
0	1	1	0	0	1
0	1	1	1	0	1
1	0	0	0	0	0
1	0	0	1	0	1
1	0	1	0	X	X
1	0	1	1	1	0
1	1	0	0	0	0
1	1	0	1	0	1
1	1	1	0	1	0
1	1	1	1	X	X

Table 1: The truth table.

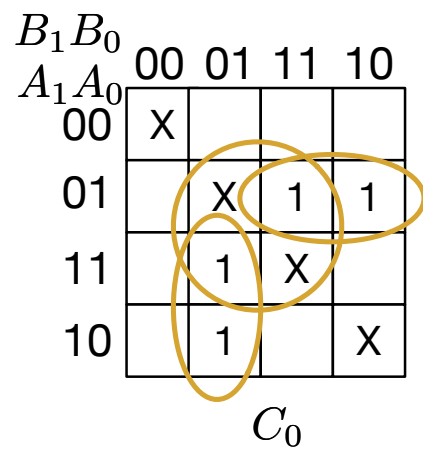
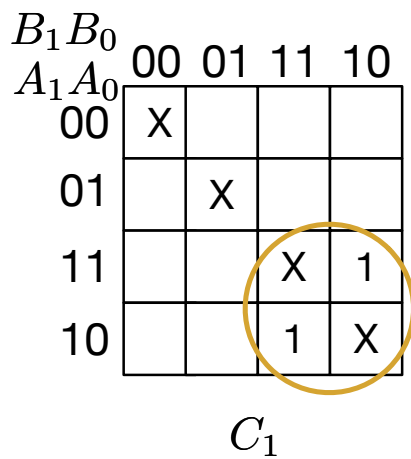


Figure 8: The Karnaugh Map.

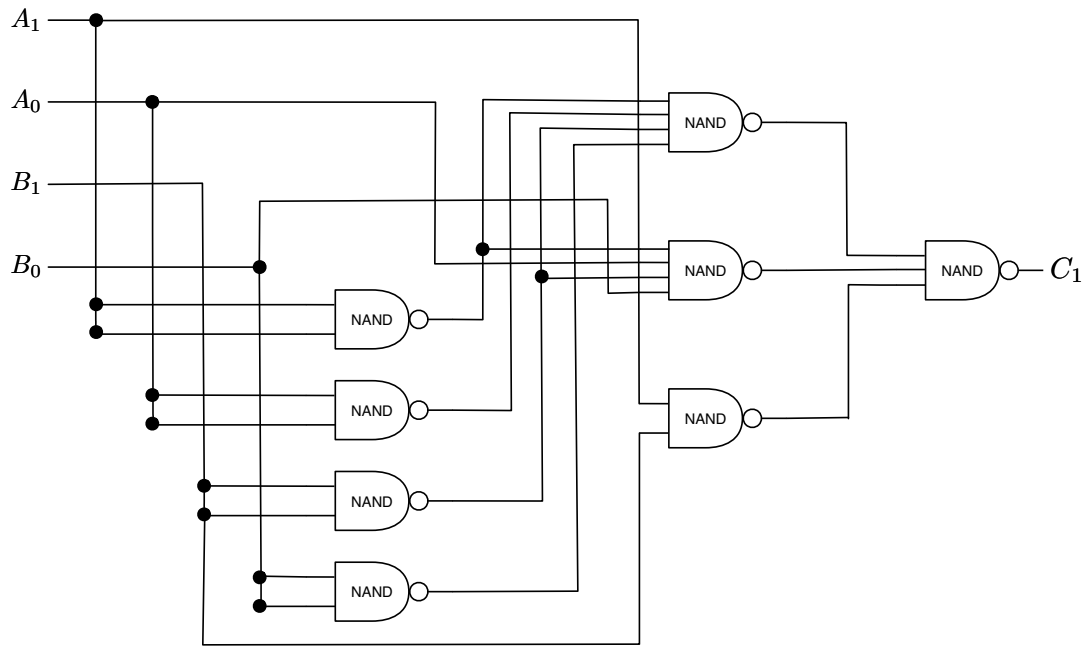


Figure 9: The C_1 logic diagram of the circuit.

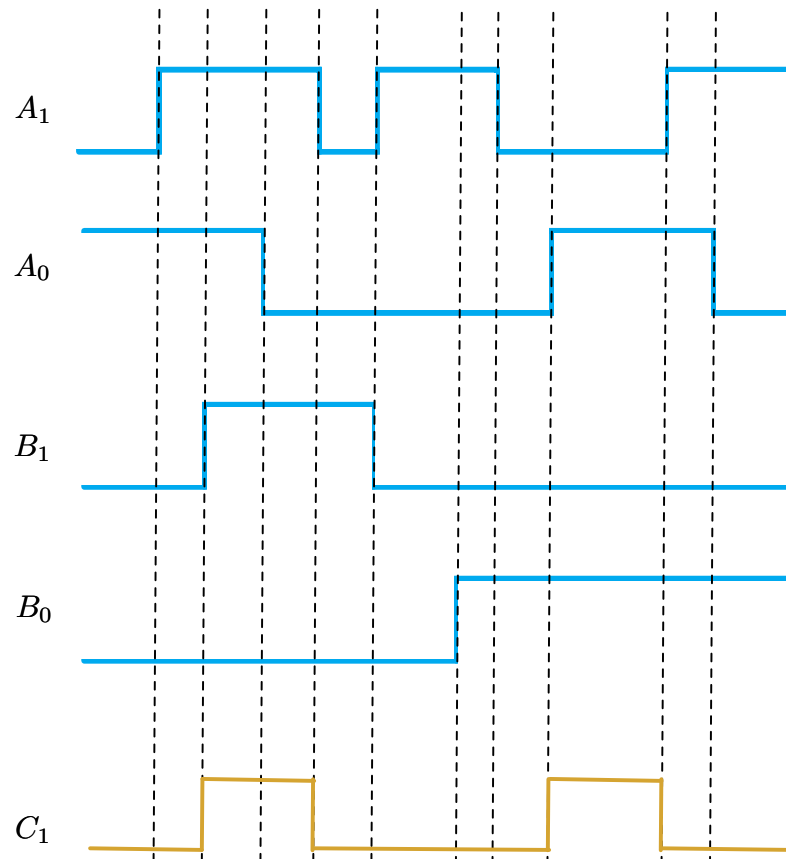


Figure 10: The output C_1 waveform.

6. (15 points) Design a magnitude comparator circuit for 2-bit binary numbers $A = \{A_1, A_0\}$ and $B = \{B_1, B_0\}$. The outputs are X , Y , and Z , where $X = 1$ if $A > B$; $X = 0$ otherwise. $Y = 1$ if $A < B$; $Y = 0$ otherwise. $Z = 1$ if $A = B$; $Z = 0$ otherwise.

- (1) (9 points) Fill in the truth table in Table 2 for the three outputs of the comparator and write down the standard SOP forms for X , Y and Z ;

A_1	A_0	B_1	B_0	$X(A > B)$	$Y(A < B)$	$Z(A = B)$
0	0	0	0			
0	0	0	1			
0	0	1	0			
0	0	1	1			
0	1	0	0			
0	1	0	1			
0	1	1	0			
0	1	1	1			
1	0	0	0			
1	0	0	1			
1	0	1	0			
1	0	1	1			
1	1	0	0			
1	1	0	1			
1	1	1	0			
1	1	1	1			

Table 2: The truth table of a magnitude comparator circuit for 2-bit binary numbers

- (2) (6 points) Implement Z logic diagram of the circuit using a 74HC154 decoder as shown in Figure 11 and one or several NAND gates (Connect ALL input pins as needed; You may assume that complementary inputs, if needed, are directly available, i.e. $\bar{A}_1, \bar{A}_0, \bar{B}_1, \bar{B}_0$ are available).

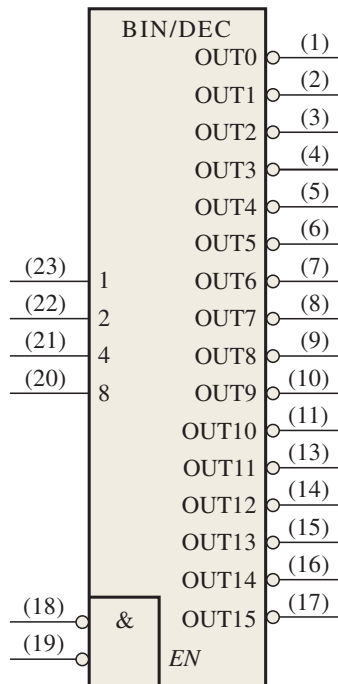


Figure 11: The 74HC154 decoder.

Solution:

(1) The truth table is shown in Table 3. The standard SOP forms are

$$X = \bar{A}_1 A_0 \bar{B}_1 \bar{B}_0 + A_1 \bar{A}_0 \bar{B}_1 \bar{B}_0 + A_1 \bar{A}_0 \bar{B}_1 B_0 + A_1 A_0 \bar{B}_1 \bar{B}_0 + A_1 A_0 \bar{B}_1 B_0 + A_1 A_0 B_1 \bar{B}_0$$

$$Y = \bar{A}_1 \bar{A}_0 \bar{B}_1 B_0 + \bar{A}_1 \bar{A}_0 B_1 \bar{B}_0 + \bar{A}_1 \bar{A}_0 B_1 B_0 + \bar{A}_1 A_0 B_1 \bar{B}_0 + \bar{A}_1 A_0 B_1 B_0 + A_1 \bar{A}_0 B_1 B_0$$

$$Z = \bar{A}_1 \bar{A}_0 \bar{B}_1 \bar{B}_0 + \bar{A}_1 A_0 \bar{B}_1 B_0 + A_1 \bar{A}_0 B_1 \bar{B}_0 + A_1 A_0 B_1 B_0$$

(2) The Z logic diagram of the circuit is shown in Figure 12.

A_1	A_0	B_1	B_0	$X(A > B)$	$Y(A < B)$	$Z(A = B)$
0	0	0	0	0	0	1
0	0	0	1	0	1	0
0	0	1	0	0	1	0
0	0	1	1	0	1	0
0	1	0	0	1	0	0
0	1	0	1	0	0	1
0	1	1	0	0	1	0
0	1	1	1	0	1	0
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	0	1
1	0	1	1	0	1	0
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	0	1

Table 3: The truth table of a magnitude comparator circuit for 2-bit binary numbers

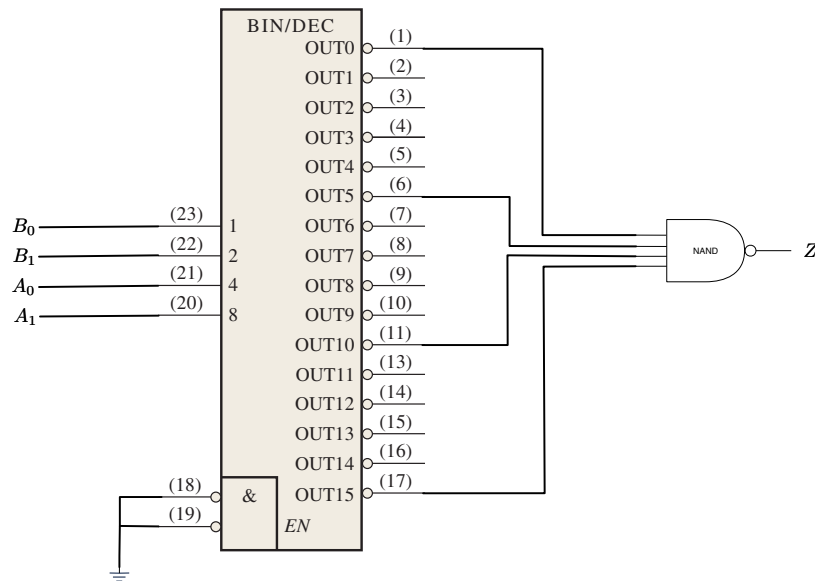


Figure 12: The Z logic diagram of the circuit.

7. (10 points) Consider the boolean expressions as follows,

$$D_0 = X\bar{S}_1\bar{S}_0 + YS_1\bar{S}_0$$

$$D_1 = X\bar{S}_1S_0 + YS_1S_0$$

$$D_2 = XS_1\bar{S}_0 + Y\bar{S}_1\bar{S}_0$$

$$D_3 = XS_1S_0 + Y\bar{S}_1S_0$$

Design a circuit to implement the boolean expressions using 1-of-4 decoders as shown in Figure 13 and NAND gates, where the truth table of 1-of-4 decoder is shown in Table 4. (Connect ALL input pins as needed. You may assume that complementary inputs, if needed, are directly available - e.g., both A_0 and \bar{A}_0 are available).

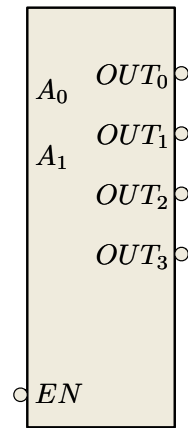


Figure 13: A 2-line-to-4-line (1-of-4) decoder.

EN	A_1	A_0	OUT_0	OUT_1	OUT_2	OUT_3
0	X	X	1	1	1	1
1	0	0	0	1	1	1
1	0	1	1	0	1	1
1	1	0	1	1	0	1
1	1	1	1	1	1	0

Table 4: The truth table of 2-line-to-4-line (1-of-4) decoder

Solution: The designed circuit is shown in Figure 14.

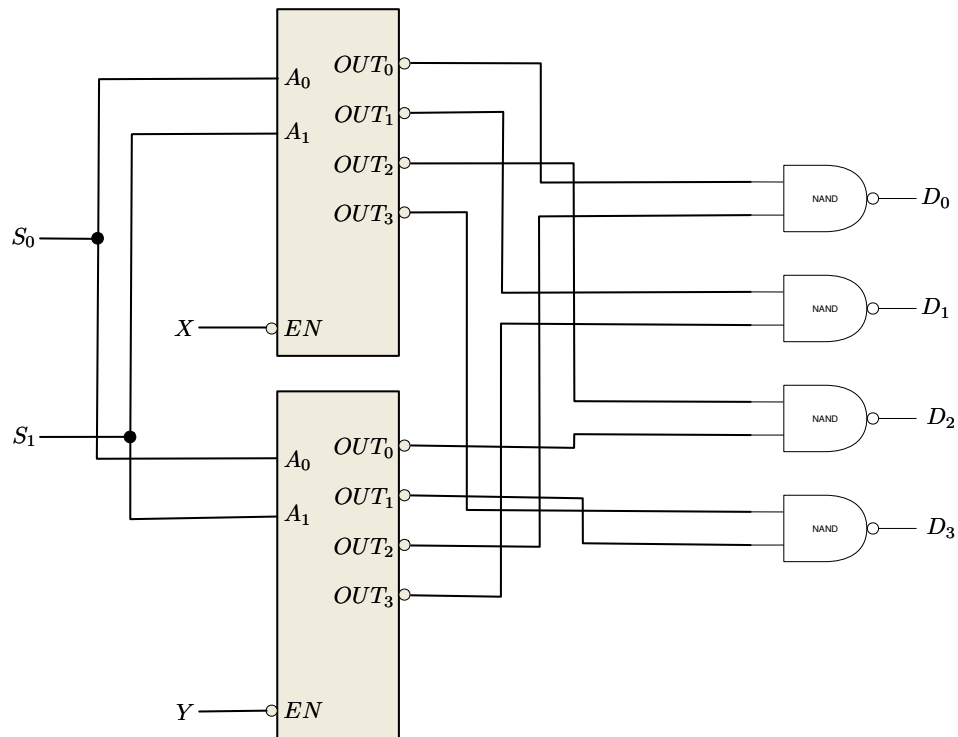


Figure 14: Q7 solution.

8. (10 points) In Chapter 6, we have studied a simplified method of multiplexing two four-bit BCD numbers to a single BCD-to-7-segment decoder as shown in Figure 15. Note that the 74HC157 is a quad 2-input multiplexer. If the data-select line is LOW, the multiplex passes A bits (A_3, A_2, A_1, A_0) to the BCD-to-7-segment decoder. In contrast, if the data-select line is HIGH, the multiplex passes B bits (B_3, B_2, B_1, B_0) to the BCD-to-7-segment decoder.

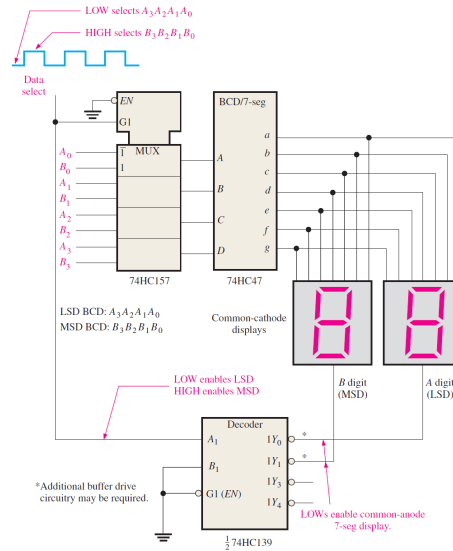


Figure 15: Simplified 7-segment display multiplexing logic from the textbook.

Now, we would like to extend this design to multiplexing THREE four-bit BCD numbers with only ONE additional multiplexer and one additional data-select line.

- (1) (5 points) Design and draw the data-select input waveform for both S_1 and S_2 ;
- (2) (5 points) Complete the circuit shown in Figure 16 by properly connecting all the components, assuming that the third BCD C is represented by (C_3, C_2, C_1, C_0)

S_1 ?

S_2 ?

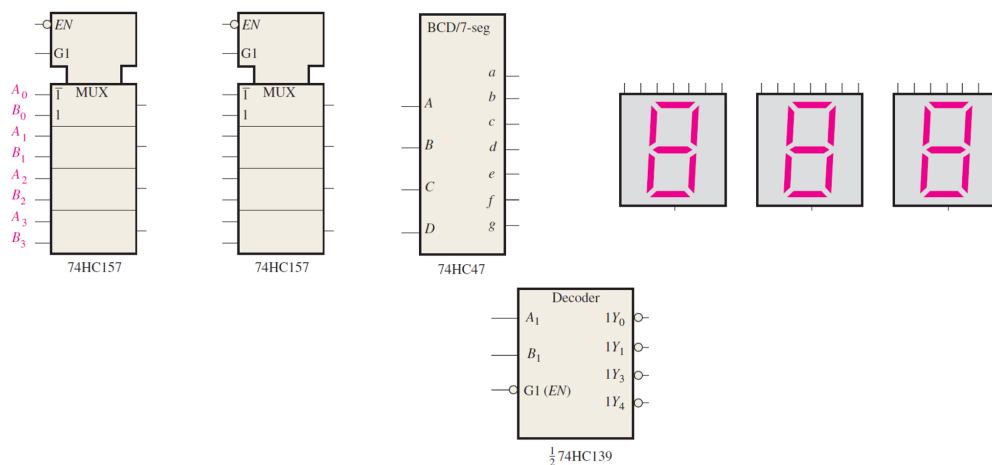


Figure 16: Multiplexing three four-bit BCD numbers.

Solution:

CONTINUED

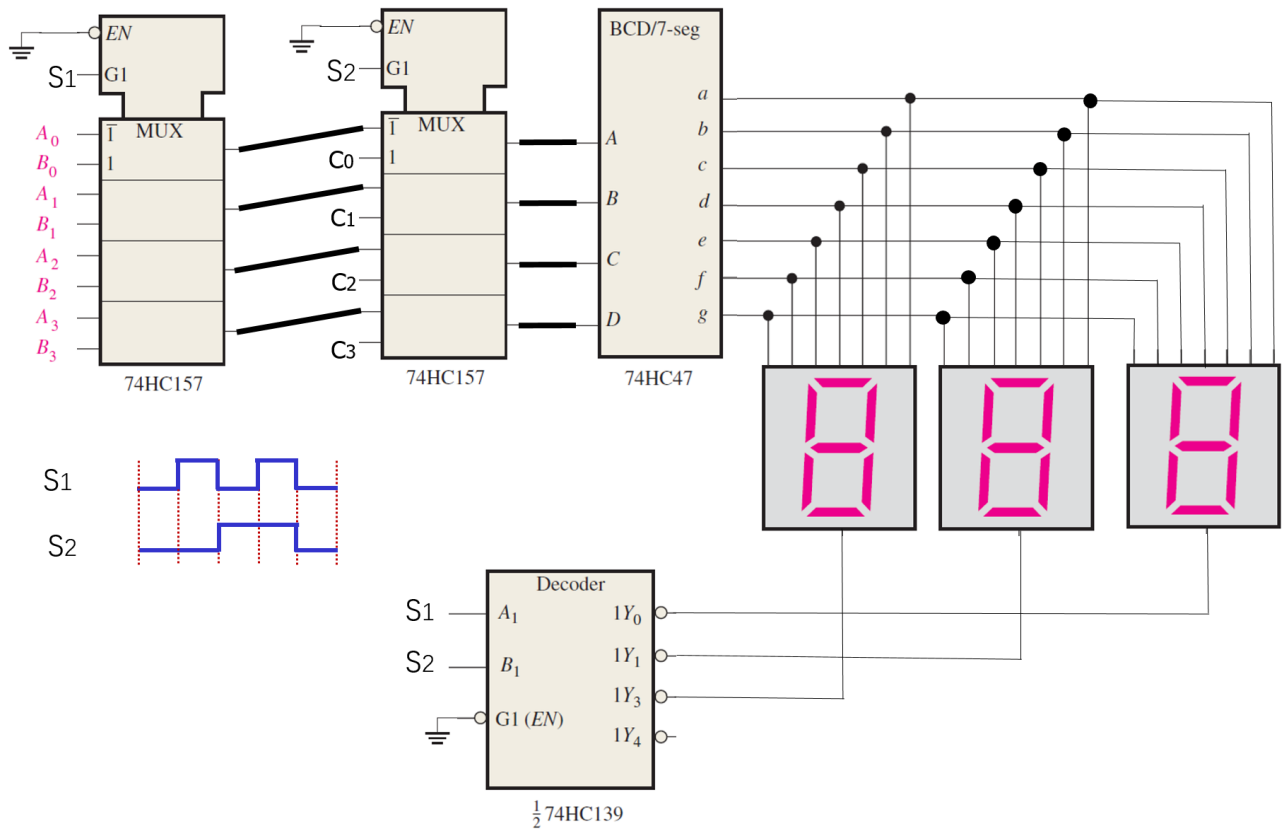


Figure 17: Solution for Q.8.